

EE3235 Analog Integrated Circuit Analysis and Design I

Homework 4 Ideal OP circuit

Due date: 2021.11.24 (Wed.) 13:20 (upload to eeclass system)

Suppose $V_{DD}=1.8V$, temperature= $25^{\circ}C$, TT corner in this homework.

Please note that:

1. **No delay allowed.**
2. Please hand in your report using eeclass system.
3. Please generate your report with **pdf** format, name your report as [HWX_studentID_name.pdf](#).
4. Please hand in the spice code file (.sp) for each work. Do not include output file.
5. Please print waveform with [white background](#), and make sure the X, and Y labels are clear.
6. Please do not zip your report.

1. Unity – gain Amplifier

(a) DC sweep



(b) TF analysis

```
**** small-signal transfer characteristics  
  
v(vout)/vin = 999.0010m  
input resistance at vin = 1.000e+20  
output resistance at v(vout) = 0.
```


DC gain calculation

$$\frac{V_{out}}{V_{IN}} = \frac{A_0}{1 + A_0} = \frac{1000}{1 + 1000} = 0.999000999 \left(\frac{V}{V} \right)$$

The simulation is exactly the same except the rounding figures, this simulation is based on considering finite gain with ideal op.

2. Noninverting amplifier

(a) DC Sweep

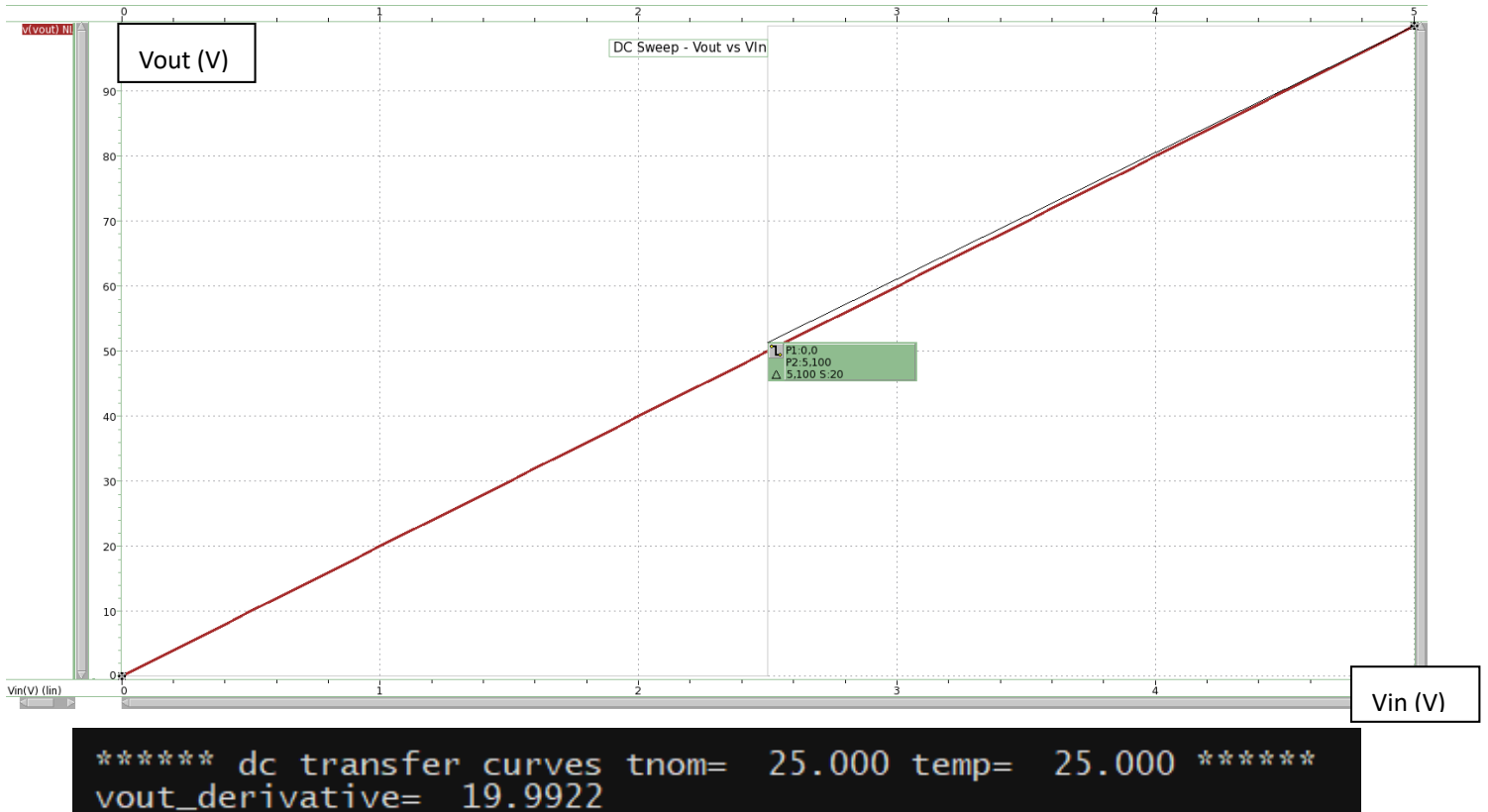

(b) TF analysis

```

***      small-signal transfer characteristics

v(vout)/vin                      = 19.9922
input resistance at vin           = 1.000e+20
output resistance at v(vout)      = 0.

```

(c) Design Consideration

The gain of non-inverting amplifier without considering finite gain is $\frac{R_1+R_2}{R_2}$, and considering finite gain is

$\frac{R_1+R_2}{R_2} \left(\frac{1}{1+\frac{R_1+R_2}{R_2 A_0}} \right)$, so if merely considering the infinite gain model, then the ratio between R_1 and R_2 is 19:1. Then,

with the consideration of finite gain, I observe that increasing R_1 by small figure increases the $\frac{R_1+R_2}{R_2}$ term but

decreases $\left(\frac{1}{1+\frac{R_1+R_2}{R_2 A_0}} \right)$, so with this relationship, I increases 0.2k Ω to R_1 every time to approach to the projected

gain. Another consideration on the resistor is that courses from electric circuit says op amp usually work with resistors of k Ω , so I choose $R_1 = 38 \text{ k}\Omega$ and $R_2 = 2 \text{ k}\Omega$ originally and set for 38.8 k Ω and 2 k Ω . The reason of not using $R_1 = 19 \text{ k}\Omega$ and $R_2 = 1 \text{ k}\Omega$, is that every 0.2k Ω increment on R_1 has much more impact if using smaller R_2 .

The hand calculated gain of using the selected resistor is $\frac{R_1+R_2}{R_2} \left(\frac{1}{1+\frac{R_1+R_2}{R_2 A_0}} \right) = \frac{38.8\text{k}\Omega+2\text{k}\Omega}{2\text{k}\Omega} \left(\frac{1}{1+\frac{38.8\text{k}\Omega+2\text{k}\Omega}{2\text{k}\Omega \times 1000}} \right) =$

19.99215994 $\left(\frac{\text{V}}{\text{V}} \right)$, this is exactly the same with the simulation except the rounding figures.

**** resistors

subckt

element 0:r1 0:r2

r value	38.8000k	2.0000k
---------	----------	---------


v drop	19.0122	980.0078m
--------	---------	-----------

current	490.0039u	490.0039u
---------	-----------	-----------

power	9.3160m	480.2077u
-------	---------	-----------

3. Inverting amplifier

(a) DC Sweep

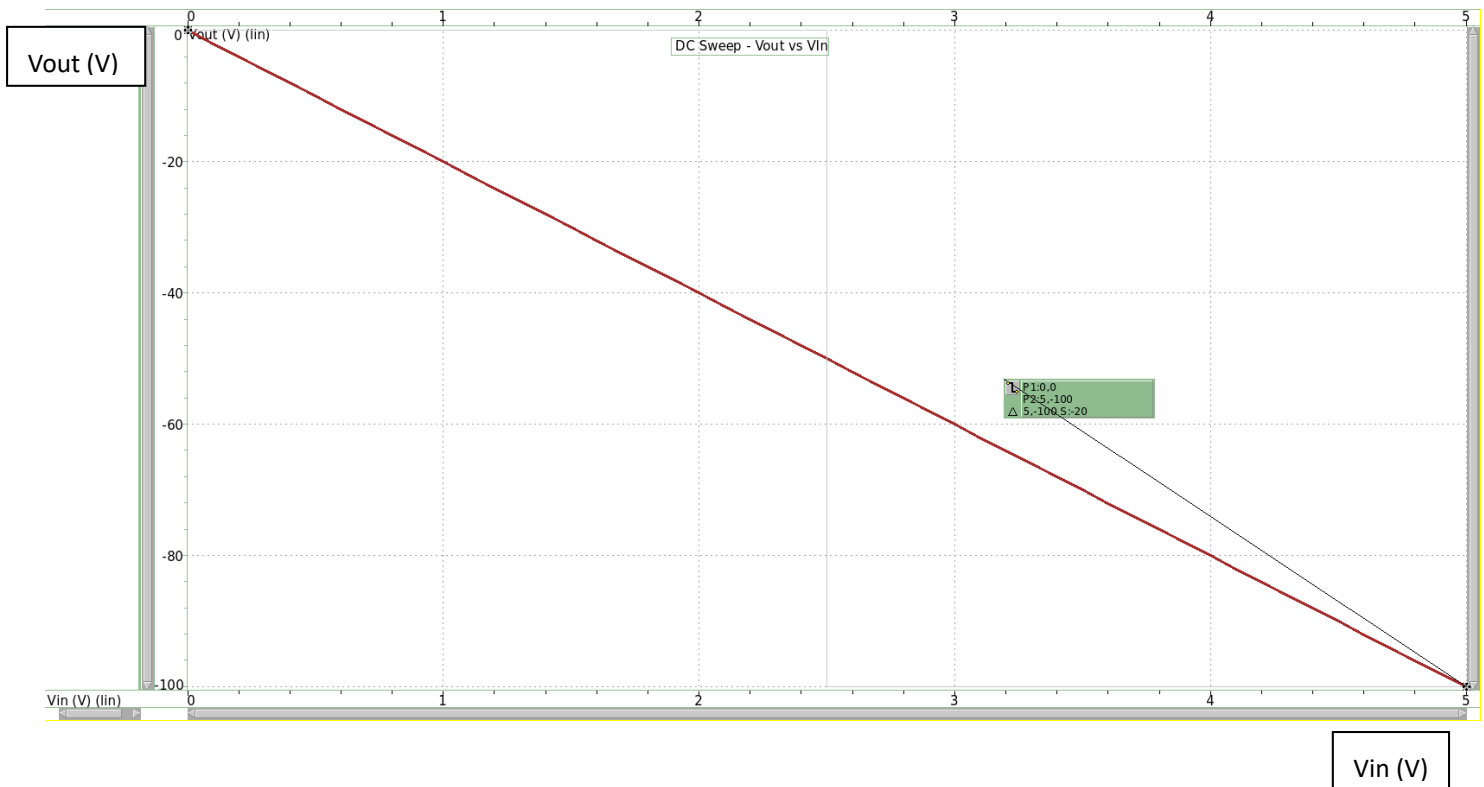

(b) TF Analysis

```
***** dc transfer curves tnom= 25.000 temp= 25.000 *****
vout derivative= -20.0206
```

```
**** small-signal transfer characteristics
v(vout)/vin          = -20.0206
input resistance at   vin    = 4.0817k
output resistance at  v(vout) = 0.
```

(c) Design Consideration

The gain of inverting amp without considering finite gain is $\frac{-R_1}{R_2}$, and the gain of considering finite gain is $\frac{-R_1}{R_2} \frac{1}{1 + \frac{1}{A_0}(\frac{R_1}{R_2} + 1)}$.

The absolute value of $\frac{-R_1}{R_2}$ increases when R_1 increases, but $\frac{1}{1 + \frac{1}{A_0}(\frac{R_1}{R_2} + 1)}$ decreases when R_1 increases.

With similar approach on last part, First choose ratio of $\frac{R_1}{R_2} = 20$ as a design start point and resistor of $k\Omega$ level. Then increases R_1 by $0.2 k\Omega$ to observe the gain. I choose $R_2 = 4 k\Omega$ and $R_1 = 80 k\Omega$ as starting point, I use 4:80 instead of 1:20 because larger R_2 is less sensitive to every $0.2 k\Omega$ increment on R_1 . Eventually, I set for $R_1 = 81.8 k\Omega$ and $R_2 = 4 k\Omega$.

The hand calculated gain is $\frac{-R_1}{R_2} \frac{1}{1 + \frac{1}{A_0}(\frac{R_1}{R_2} + 1)} = \frac{-81.8k}{4k} \frac{1}{1 + \frac{1}{1000}(\frac{81.8k}{4k})} = -20.02055901(\frac{V}{V})$

The hand calculated value is exactly the same with the simulated result except the rounding figures.


```
*** resistors
```

```
subckt
```

element	0:r2	0:r1
r value	4.0000k	81.8000k
v drop	0.	0.
current	0.	0.
power	0.	0.


4. Voltage adder

(a) DC Sweep

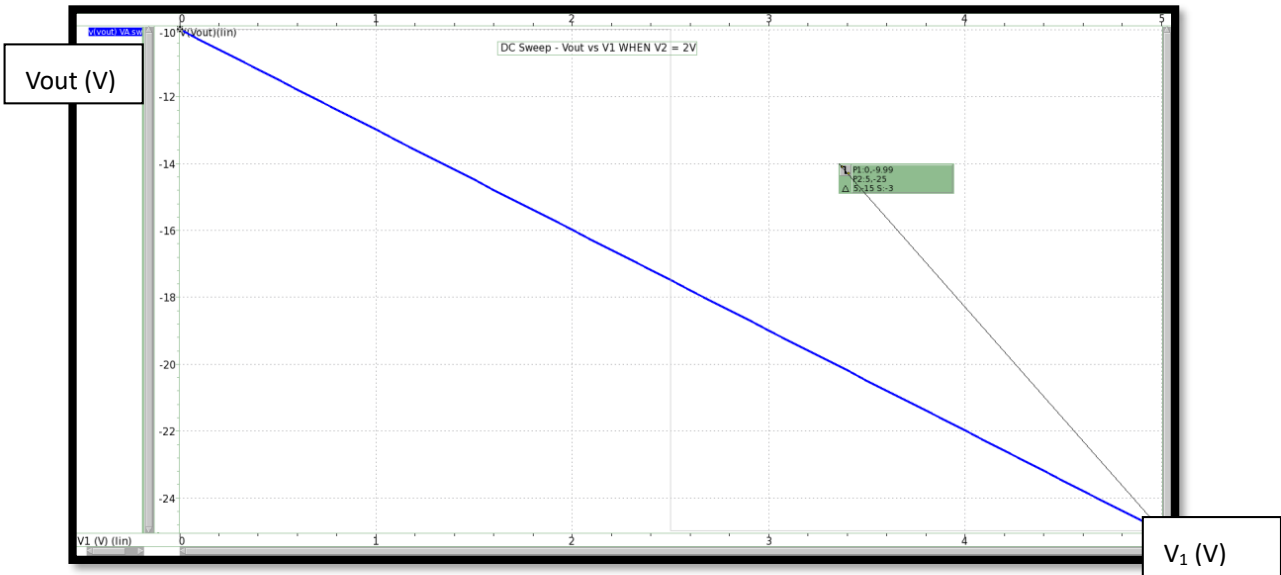

	X1	Y1	X2	Y2	DeltaX	DeltaY	Slope	Show
1	0	-9.99	5	-25	5	-15	-3	<input checked="" type="checkbox"/>
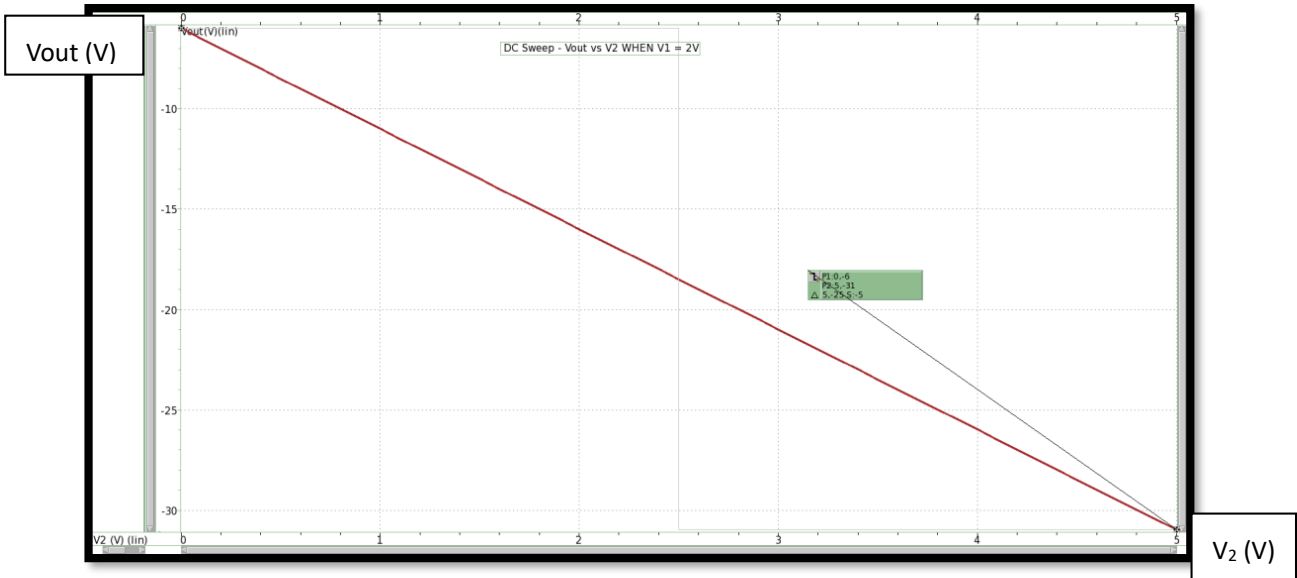
```
***** dc transfer curves tnom= 25.000 temp= 25.000 *****
slope1= -2.9978
*****
```



	X1	Y1	X2	Y2	DeltaX	DeltaY	Slope	Show
1	0	-6	5	-31	5	-25	-5	<input checked="" type="checkbox"/>

```
***** dc transfer curves tnom= 25.000 temp= 25.000 *****
slope2= -4.9964
```

The reason of using derivative of V_{out} at 2.5V instead of average of derivative of V_{out} from 0V to 5V in part(a) is because the derivative at boundary point (0V to be specific) doesn't follow the rest of the points on the straight slope which diluted the real slope.

(b)

Comments:

The relation is between slope1/slope2 and the function is that when V_2 is fixed then the slope1 simply approaches to the negative value of the coefficient of V_1 for the given function, and it goes the same for slope 2 and V_2 when V_1 being fixed.

$$\frac{V_1 - V_X}{R_1} + \frac{V_2 - V_X}{R_2} = \frac{V_X - V_{out}}{R_F}$$

$$V_{out} = A_0(0 - V_X) = -A_0 V_X$$

With above relation, we can get
$$\frac{V_1 + \frac{V_{out}}{A_0}}{R_1} + \frac{V_2 + \frac{V_{out}}{A_0}}{R_2} = \frac{\frac{-V_{out}}{A_0} - V_{out}}{R_F}$$

$$\Rightarrow -V_{out} = \frac{A_0 R_2 R_F}{(R_1 + R_2) R_F + (1 + A_0) R_1 R_2} V_1 + \frac{A_0 R_1 R_F}{(R_1 + R_2) R_F + (1 + A_0) R_1 R_2} V_2$$

For My design, I select $R_1 = 20 \text{ k}\Omega$, $R_2 = 12 \text{ k}\Omega$, $R_F = 60.5 \text{ k}\Omega$

For slope 1, since V_2 is fixed, the slope is simply the term
$$\frac{A_0 R_2 R_F}{(R_1 + R_2) R_F + (1 + A_0) R_1 R_2} = \frac{1000 \times 12k \times 60.5k}{(20k + 12k) \times 60.5k + (1 + 1000) 12k \times 20k} = 2.9978$$

For slope 2, since V_1 is fixed, the slope is simply the term
$$\frac{A_0 R_1 R_F}{(R_1 + R_2) R_F + (1 + A_0) R_1 R_2} = \frac{1000 \times 20k \times 60.5k}{(20k + 12k) \times 60.5k + (1 + 1000) 12k \times 20k} = 4.9964$$

The hand calculated value is identical to the simulation result except for a negative sign needed to be add in front, since the device is an inverting summer.

(c) design consideration

Although the above equations relation gives an exact approach of getting the desired R_F value for setting R_1 and R_2 constant ratio (e.g. $R_1 = 5x$, $R_2 = 3x$). But since it only has two voltage input, so I can view it as two inverting amplifiers with linear addition

without huge difference to the simulation result. The function without considering finite gain is $-R_F(\frac{V_1}{R_1} + \frac{V_2}{R_2})$

So, I first considered the case of $R_1 = 20 \text{ k}\Omega$, $R_2 = 12 \text{ k}\Omega$, $R_F = 60 \text{ k}\Omega$ where 60 is the lcm of 12 and 20 and $\frac{60}{20} = 3$, $\frac{60}{12} = 5$

Then combining the experience from the inverting amplifier, having a small amount of increment to R_F will make the gain value (considering finite gain) approaches to the requested value. So, I set $R_1 = 20 \text{ k}\Omega$, $R_2 = 12 \text{ k}\Omega$, $R_F = 60.5 \text{ k}\Omega$ and gets the result that I wanted with slope error $< 1\%$.

**** resistors			
subckt	0:r1	0:r2	0:rf
element	20.0000k	12.0000k	60.5000k
r value	20.0000k	12.0000k	60.5000k
v drop	1.9840	1.9840	16.0044
current	99.2006u	165.3343u	264.5349u
power	196.8151u	328.0252u	4.2337m

5. Square-Root Amplifier

(a) DC sweep



(b)

Vin	Simulation Vov (mV)	Calculation Vov(mV)	error	error square	ERR
1	189.6916	189.6916	0	0	0.02103
2	280.3825	268.2644334	0.04517	0.002040518	2.10%
3	350.1854	328.555489	0.06583	0.004334031	
4	409.5455	379.3832	0.0795	0.00632081	
5	462.8839	424.1633124	0.09129	0.008333313	

(c) design consideration

The first thought of setting the W/L value is that since the ideal formula discard the effect of channel length modulation, so for the neglection of channel length modulation, I set $\frac{W}{L} = \frac{2\mu m}{1\mu m}$ a common ratio with micrometer level of channel length.

Then, considering the NMOS in saturation and finite gain is put into consideration. The equation

considering finite gain should look like $\frac{V_{in} + \frac{V_{out}}{A_0}}{R_1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (-V_{out} - V_{TH})^2$, neglecting channel length modulation when in saturation.

There are plenty to notice, the LHS of the equation tells that if V_{out} is large due to amplification then the device won't be close to a square root amplifier, since the original design taught on course didn't consider the term $\frac{V_{out}}{A_0}$. Making R_1 larger has same concepts of dropping the gain on output side of the inverting

amplifier case. Consider that the MOSFETS in previous homework usually operates in microamps,

combining that I want to make $\frac{V_{out}}{A_0}$ neglectable and the LHS can be simply viewed as $\frac{V_{in}}{R_1}$ by making R_1

large, so I set the starting R_1 to 50k Ω . The small signal parameters then can be found for detailed calculation.

But, at 50k Ω , the overdrive voltage doesn't follow the square root growth when the input voltage is at 5V, this indicates that the source voltage is amplified negative to an extend that the drain current doesn't grow in square order, so Resistance had to be increased.

Then few more increment on R_1 to make the overdrive voltage stays in square root growth and also making

$\frac{V_{in}}{R_1}$ approaches close to the drain current for 1~5 V respectively. Eventually I stick for $R_1 = 98k\Omega$ and the

ERR is 2.1%.

Another perspective provided by classmates is that increasing resistance also increases the voltage drop across R_1 , this then makes V_X approximately become a virtual short.

```
**** resistors
subckt
element 0:r1
r value 98.0000k
v drop 4.9993
current 51.0128u
power 255.0256u
```

M1 operating point from 1V – 5V

**** mosfets

```
subckt
element 0:m1
model 0:n_18.1
region Saturation
id 10.1990u
ibs 66.8439n
ibd -1.052e-19
vgs 502.5534m
vds 503.0559m
vbs 502.5534m
vth 312.8618m
vdsat 168.4131m
vod 189.6916m
beta 615.8308u
gam eff 496.4716m
gm 93.5025u
gds 1.1099u
gmb 9.6448u
cdtot 3.2826f
cgtot 14.0742f
cstot 15.1596f
cbtot 7.0839f
cgs 12.9658f
cgd 738.6390a
```

**** mosfets

```
subckt
element 0:m1
model 0:n_18.1
region Saturation
id 20.4022u
ibs 1.5676u
ibd -1.203e-19
vgs 583.6221m
vds 584.2057m
vbs 583.6221m
vth 303.2395m
vdsat 228.5102m
vod 280.3825m
beta 616.9924u
gam eff 495.1403m
gm 133.2467u
gds 1.7331u
gmb 11.8240u
cdtot 3.2874f
cgtot 14.1024f
cstot 15.1584f
cbtot 6.9936f
cgs 13.0651f
cgd 743.4892a
```

**** mosfets

```
subckt
element 0:m1
model 0:n_18.1
region Saturation
id 30.6056u
ibs 18.1212u
ibd -1.314e-19
vgs 646.5314m
vds 647.1779m
vbs 646.5314m
vth 296.3460m
vdsat 274.4311m
vod 350.1854m
beta 617.3257u
gam eff 494.1689m
gm 162.4146u
gds 2.2364u
gmb 12.7946u
cdtot 3.2891f
cgtot 14.1159f
cstot 15.1532f
cbtot 6.9382f
cgs 13.1258f
cgd 746.4820a
```

**** mosfets


```
subckt
element 0:m1
model 0:n_18.1
region Saturation
id 40.8092u
ibs 146.5039u
ibd -1.407e-19
vgs 700.3707m
vds 701.0710m
vbs 700.3707m
vth 290.8252m
vdsat 313.0758m
vod 409.5455m
beta 617.1953u
gam eff 493.3787m
gm 186.5183u
gds 2.6710u
gmb 13.2540u
cdtot 3.2896f
cgtot 14.1272f
cstot 15.1523f
cbtot 6.8995f
cgs 13.1733f
cgd 748.6610a
```

**** mosfets


```
subckt
element 0:m1
model 0:n_18.1
region Saturation
id 51.0128u
ibs 943.2844u
ibd -1.488e-19
vgs 749.0563m
vds 749.8053m
vbs 749.0563m
vth 286.1723m
vdsat 347.1276m
vod 462.8839m
beta 616.7504u
gam eff 492.7028m
gm 207.4606u
gds 3.0575u
gmb 13.4340u
cdtot 3.2894f
cgtot 14.1374f
cstot 15.1543f
cbtot 6.8712f
cgs 13.2131f
cgd 750.3939a
```

Observation after design

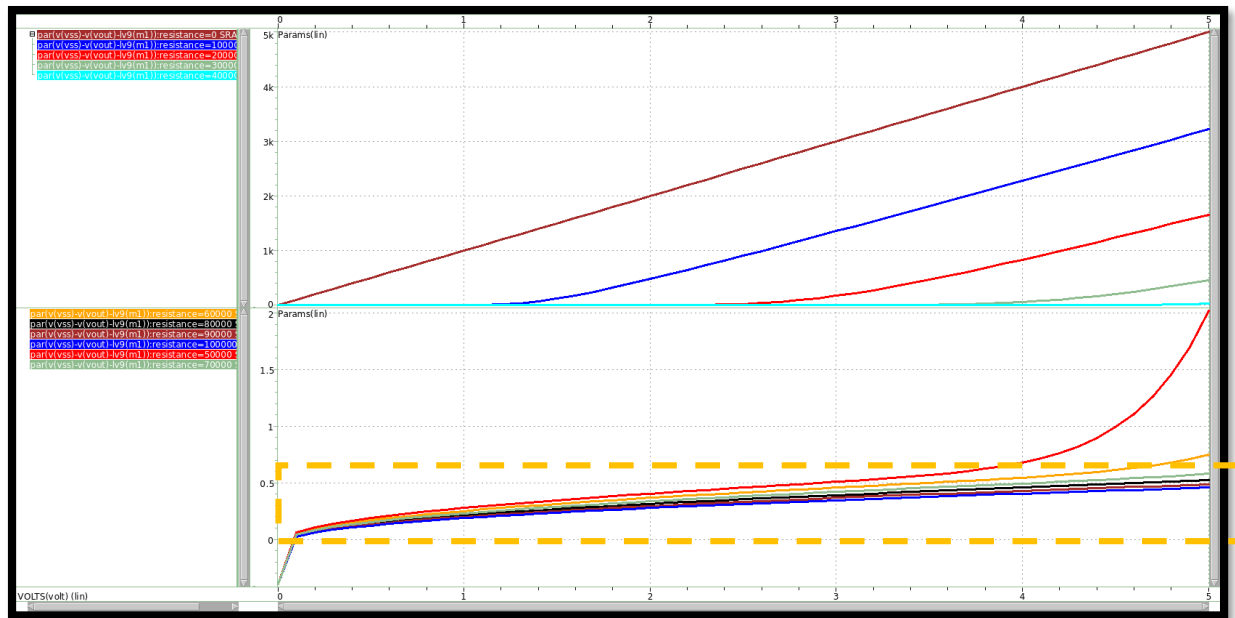Overdrive voltage DC sweep for $R_1 = 0\text{k}\Omega$ to $100\text{k}\Omega$ with fixed $\frac{W}{L}$



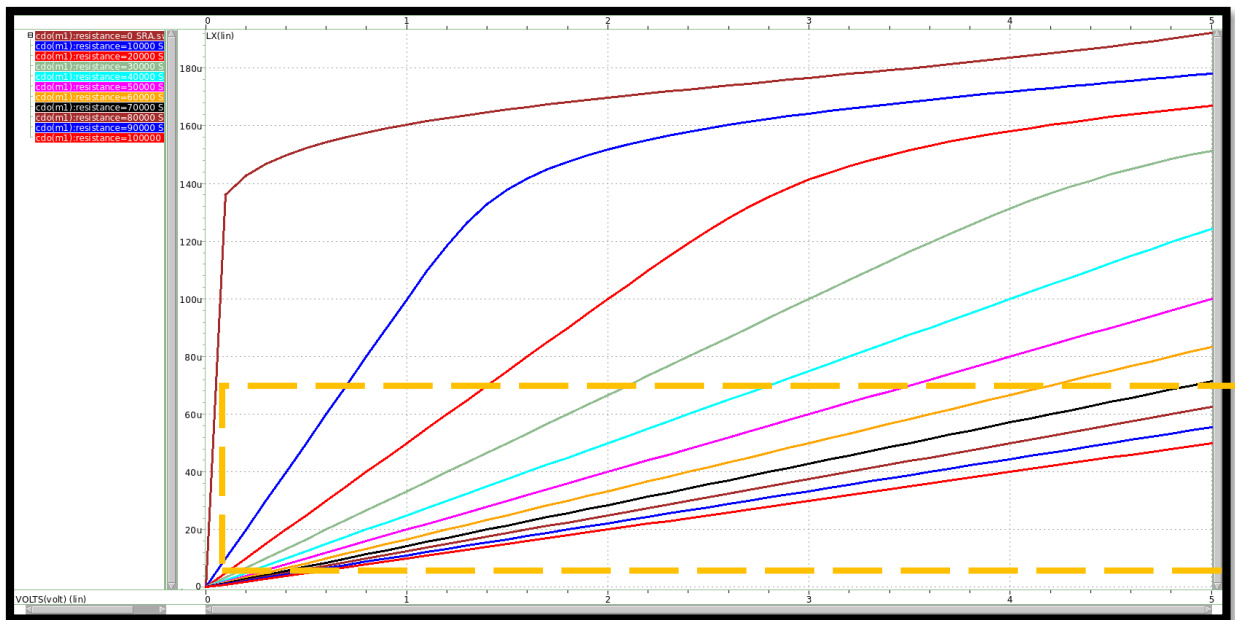
Drain current DC sweep for $R_1 = 0\text{k}\Omega$ to $100\text{k}\Omega$ with fixed $\frac{W}{L}$



The overdrive drive voltage and drain current that I boxed in yellow dashed line is the curve we are looking for to design a square root amplifier. First for my $\frac{W}{L}$ fixed, if the drain current is too high, it then grows in a flat curve, and the corresponding overdrive voltage blows up instead of growing in square root order.

This also occurs to me that when the source side is too negative, then the body diode is turned on. This causes leakage current which makes the overdrive voltage grows larger than normal. So using higher resistance also prevents this from happening.

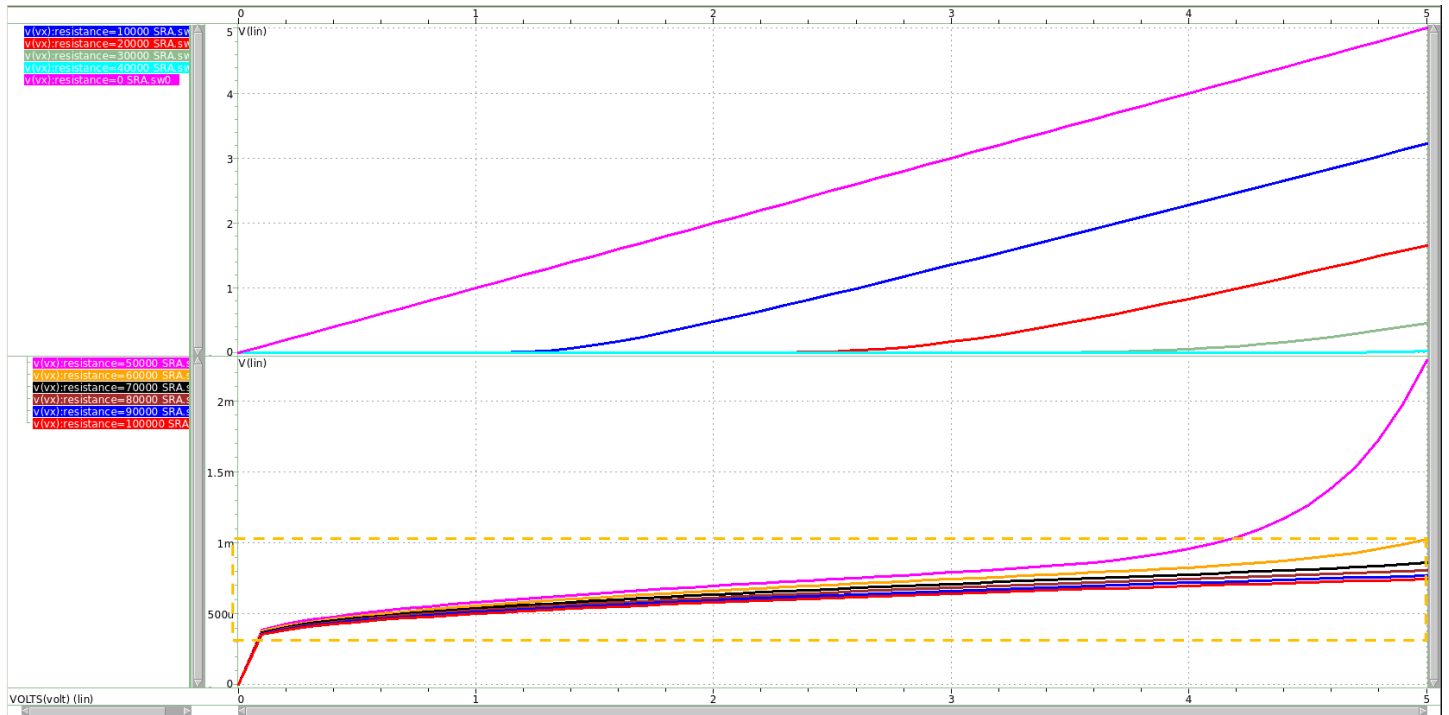V_X DC sweep for or $R_1 = 0k\Omega$ to $100k\Omega$ with fixed $\frac{W}{L}$



Having a small resistance also causes V_X to be large through feedback where the negative input port cannot approach to a virtual short. The region where the yellow dashed line boxed has small V_X and doesn't vary much for increasing V_{in} .