

EE3235 Analog Integrated Circuit Analysis and Design I

Homework 3

Cascade Amplifier

Due date: 2021.11.10 (Wed.) 13:20 (upload to eeclass system)

Suppose $V_{DD}=1.8V$, temperature=25°C, TT corner in this homework.

Please note that:

1. **No delay allowed.**
2. Please hand in your report using eeclass system.
3. Please generate your report with **pdf** format, name your report as **HWX_studentID_name.pdf**.
4. Please hand in the spice code file (.sp) for each work. Do not include output file.
5. Please print waveform with **white background**, and make sure the X, and Y labels are clear.
6. Please do not zip your report.

Part I – Cascode Amplifier**(a) Design Process**

The common source cascode amplifier is strongly dominated by the output resistance of the PMOS and NMOS, since the gain can be approximated by $A_v = -g_{m,n} (r_{o1} || r_{o2})$. The output resistance is calculated by $r_o = \frac{1}{\lambda I_D}$. From the 2 above formula, there are 2 approaches to acquire high gain, the first is to boost up the transconductance of the NMOS, but raising up the transconductance makes the drain current larger which inversely drops the output resistance lower. This leads to the second approach, use larger channel length, which diminishes the channel length modulation effect on the transistor. This will increase the output resistance when the transistors are in saturation region. A tradeoff between device size and gain can be observed from here.

From above I start from using $1\mu m$ as channel length. Courses from microelectronics reminds me that the mobility of electron is about twice larger than hole, I then set the W/L of PMOS to 2 and W/L of NMOS, and sweeps for the V_{in} and V_{b1} relation for given V_{b1} when V_{out} is at 0.5V. I then also reversed the ratio of NMOS and PMOS to observe if higher gain can be achieved, with surprising result, it actually does. With some few trials of increasing channel length and the fixed ratio relation

($\frac{W}{L_{NMOS}} : \frac{W}{L_{PMOS}} = 2 : 1$), I achieved the SPEC goals by setting $\frac{W}{L_{NMOS}} = \frac{3.82\mu m}{1.91\mu m}$ $\frac{W}{L_{PMOS}} =$

$\frac{1.91\mu m}{1.91\mu m}$ and $V_{in} = 0.4V, V_{b1} = 1.1V$. During design, I found out that with small changes on device such as gate voltage or channel width and length can drastically affect the performance.

(b)

.tf

```

****      small-signal transfer characteristics

v(vout)/vin      = -107.7740
input resistance at vin      = 1.000e+20
output resistance at v(vout) = 3.8525x

```

.op

```

***** option summary *****
runlvl = 5      bypass = 2.0000
****info** dc convergence successful at Newton-Raphson method
1***** PrimeSim HSPICE -- R-2020.12-SP2 linux64 (May 24 2021 7074677) *****
*****
**** protect ****

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0. *****
node      =voltage      node      =voltage      node      =voltage
+0:vb1     = 1.1000  0:vdd     = 1.8000  0:vin     = 400.0000m
+0:vout     = 498.4701m 0:vss     = 0.

maximum nodal capacitance= 6.613E-14      on node      0:vss

nodal capacitance table
node      = cap      node      = cap      node      = cap
+0:vb1     = 23.3468f 0:vdd     = 37.7989f 0:vin     = 43.7248f
+0:vout     = 7.4827f 0:vss     = 66.1338f

**** voltage sources ****
subckt
element 0:vin      0:vb1      0:vdd      0:vss
volts    400.0000m 1.1000    1.8000    0.
current  0.         0.         -1.5238u  49.4473a
power    0.         0.         2.7428u   0.

total voltage source power dissipation= 2.7428u      watts

***** mosfets *****
subckt
element 0:mp1      0:mn1
model   0:p_18.1   0:n_18.1
region  Saturation Saturation
id       -1.5238u   1.5238u
ibs      2.115e-22 -2.839e-22
ibd      165.9053a -170.5694a
vgs      -700.0000m 400.0000m
vds      -1.3015   498.4701m
vbs      0.         0.
vth      -486.4380m 354.6310m
vdsat    -206.6975m 80.2505m
vod      -213.5620m 45.3690m
beta     67.2814u   606.2986u
gam eff  557.0846m  507.4459m
gm        12.3797u   27.9754u
gds       25.0682n   234.5027n
gmb       3.8440u    5.7626u
cddtot    2.1140f    5.3687f
cgtot     23.3468f   43.7248f
cstot     26.9468f   45.4175f
cbtot     10.8522f   20.7163f
cgs       20.8850f   37.1248f
cgd       686.3449a   1.3439f

```


From part (a) with known formula $A_v = -g_{m,NMOS}(r_{o,N} || r_{o,P})$, from above operating point information,

transconductance of the NMOS is $g_{m,NMOS} = 27.9754 \mu S$, $r_{o,N} = \frac{1}{g_{ds,NMOS}} = \frac{1}{234.5027 \times 10^{-9}} \Omega$,

$$r_{o,P} = \frac{1}{g_{ds,PMOS}} = \frac{1}{25.0682 \times 10^{-9}} \Omega$$

This leads to $A_v = -27.9754 \times 10^{-6} \times \left(\frac{1}{234.5027 \times 10^{-9} + 25.0682 \times 10^{-9}} \right) = -107.7756 V/V$

The relative error rate is $\left| \frac{-107.7756 + 107.774}{107.774} \right| = 1.48 \times 10^{-3} \%$, which is almost identical between simulation value and hand calculate value.

 

$$g_{m1} = 27.9754 \mu S$$

$$g_{ds,n} = 234.5027 nS$$

$$g_{ds,p} = 25.0682 nS$$

$$A_v = - 27.9754 \times 10^{-6} \times \left(\frac{1}{234.5027 \times 10^{-9}} \parallel \frac{1}{25.0682 \times 10^{-9}} \right)$$

$$= - 107.7756 \text{ } v/v$$

(c) (d)

I choose $W/L = \frac{1.5 \mu m}{0.35 \mu m}$ and V_{b2} to 1.16 V to achieved the spec

.tf

```
**** small-signal transfer characteristics
v(vout)/vin = 10.2693
input resistance at vin = 9.7378k
output resistance at v(vout) = 65.8648k
```

.op

```
***** option summary *****
runlv1 = 5 bypass = 2.0000
**info** dc convergence successful at Newton-Raphson method
***** PrimeSim HSPICE -- R-2020.12-SP2 linux64 (May 24 2021 7074677) *****
*****
.protect

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node =voltage node =voltage node =voltage
+0:vb2 = 1.1600 0:vdd = 1.8000 0:vin = 500.0000m
+0:vout = 796.1436m 0:vss = 0.

maximum nodal capacitance= 4.887E-15 on node 0:vin
nodal capacitance table
node = cap node = cap node = cap
+0:vb2 = 4.0128f 0:vdd = 0. 0:vin = 4.8867f
+0:vout = 2.0725f 0:vss = 0.

**** voltage sources
subckt
element 0:vin 0:vb2 0:vdd 0:vss
volts 500.0000m 1.1600 1.8000 0.
current 10.0386u 0. -10.0386u -1.2964p
power -5.0193u 0. 18.0694u 0.
total voltage source power dissipation= 13.0501u watts

**** resistors
subckt
element 0:rd
r value 100.0000k
v drop 1.0039
current 10.0386u
power 10.0773u

**** mosfets
subckt
element 0:mn2
model 0:n_18.1
region Saturation
id 10.0386u
ibs -89.2925a
ibd -142.1728a
vgs 660.0000m
vds 296.1436m
vbs -500.0000m
vth 566.5795m
vdsat 131.5512m
vod 93.4205m
beta 1.4275m
gam eff 519.9009m
gm 134.0418u
gds 5.1838u
gmb 16.7241u
cdtot 2.0725f
cgtot 4.0128f
cstot 4.8867f
cbtot 3.6991f
cgs 3.1457f
cgd 543.6366a
```


From small signal model of common gate amplifier considering body conductance is

$$A_V = \left(g_m + g_{mb} + \frac{1}{r_o} \right) (r_D \parallel r_o), \text{ from above operating point information, } g_m = 134.0318 \times 10^{-6} S$$

$$g_{mb} = 16.7241 \times 10^{-6} S, \quad \frac{1}{r_o} = g_{ds} = 5.1838 \times 10^{-6} S, \quad r_o = \frac{1}{5.1838 \times 10^{-6}} \Omega$$

$$A_V = \left(g_m + g_{mb} + \frac{1}{r_o} \right) (r_D \parallel r_o) = (155.9497 \times 10^{-6}) \times 65859.6662 = 10.2708 V/V$$

The relative error rate is $\left| \frac{10.2708 - 10.2693}{10.2693} \right| = 0.015\%$, which is almost identical between simulation value and hand calculate value.

 

$$A_v = \left[g_m + g_{mb} + \frac{1}{r_o} \right] (r_D \parallel r_o)$$

$$= \left[134.0418 \times 10^{-6} + 16.7241 \times 10^{-6} + 5.1838 \times 10^{-6} \right]$$

$$\times \left[100 \times 10^3 \parallel \frac{1}{5.1838 \times 10^{-6}} \right]$$

$$= (155.9497 \times 10^{-6}) \times 65859.6662$$

$$= 10.2708 \text{ V/V}$$

(e)

```
***** option summary *****
runlvl = 5          bypass = 2.0000
****info**** dc convergence successful at Newton-Raphson method
***** Primesim HSPICE -- R-2020.12-SP2 linux64 (May 24 2021 7074677) *****
*****
.proteect

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vb1    = 1.1000 0:vb2    = 1.1600 0:vdd     = 1.8000
+0:vin    = 400.0000m 0:vout  = 799.9505m 0:vss     = 0.
+0:vx     = 500.3702m

maximum nodal capacitance= 6.613E-14      on node 0:vss

nodal capacitance table
node      = cap      node      = cap      node      = cap
+0:vb1    = 23.3469f 0:vb2    = 4.0115f 0:vdd     = 37.7994f
+0:vin    = 43.7262f 0:vout  = 2.0707f 0:vss     = 66.1339f
+0:vx     = 12.3664f
```

```
**** current sources
subckt
element 0:i1
volts 500.3702m
current 10.0000u
power -5.0037u

total current source power dissipation= -5.0037u watts

**** resistors
subckt
element 0:rd
r value 100.0000k
v drop 1.0000
current 10.0005u
power 10.0010u
```

```
**** mosfets
subckt
element 0:mp1 0:mn1 0:mn2
model 0:p_18.1 0:n_18.1 0:n_18.1
region Saturation Saturation Saturation
id -1.5237u 1.5242u 10.0005u
ibs 2.115e-22 -2.840e-22 -89.3586a
ibd 165.6631a -171.2196a -142.8527a
vgs -700.0000m 400.0000m 659.6298m
vds -1.2996 500.3702m 299.5803m
vbs 0. 0. -500.3702m
vth -486.4380m 354.6215m 566.5581m
vdsat -206.6975m 80.2555m 131.3200m
vod -213.5620m 45.3785m 93.0716m
beta 67.2814u 606.2981u 1.4275m
gam eff 557.0846m 507.4459m 519.9092m
gm 12.3793u 27.9820u 133.8095u
gds 25.0914n 234.4641n 5.1114u
gmb 3.8439u 5.7637u 16.6901u
cdtot 2.1145f 5.3665f 2.0707f
cgtot 23.3469f 43.7262f 4.0115f
cstot 26.9468f 45.4197f 4.8854f
cbtot 10.8526f 20.7142f 3.6976f
cgs 20.8850f 37.1263f 3.1444f
cgd 686.3508a 1.3438f 543.4210a
```

```
**** voltage sources
subckt
element 0:vin 0:vb1 0:vb2 0:vdd 0:vss
volts 400.0000m 1.1000 1.1600 1.8000 0.
current 0. 0. 0. -11.5242u -1.3008p
power 0. 0. 0. 20.7436u 0.

total voltage source power dissipation= 20.7436u watts
```

Comment:

(i)

V_x has slight changes comparing to common source stage (which is 498.4701 mV) and the common gate stage (which is fixed at 0.5V), V_x is biased at 500.3702 mV, which is biased at a neglectable small increase voltage comparing to the 2 previous case.

(ii)

```
**** small-signal transfer characteristics
v(vout)/vin = -2.7911
input resistance at vin = 1.000e+20
output resistance at v(vout) = 99.9149k
```

Comment:

The gain from the transfer function is -2.7911 V/V, whereas the value acquired from multiplying the gain from individual gain stage is $A_1 \times A_2 = -107.7740 \times 10.2693 = -1106.7635 \text{ V/V}$

The reason for this significant drop is because simply multiplying both values hasn't taken the effect of the input impedance from the common gate amplifier to the common source amplifier into account.

The gain of common source amplifier should be adjusted from $-g_{m,MN1} \times (r_{o,MN1} \parallel r_{o,MP1})$ into $-g_{m,MN1} \times (r_{o,MN1} \parallel r_{o,MP1} \parallel (\frac{1}{g_{m,MN2}}) \parallel R_{current\ source})$, consider that the current source is ideal, so it's resistance is close to infinite. The gain can be calculated as $A_1 = -27.9820 \times 10^{-6} \times \frac{1}{25.0914 \times 10^{-9} + 234.4641 \times 10^{-9} + 133.8095 \times 10^{-6}} = -0.2087\ V/V$
Then the overall gain should be $A_{V,overall} = -0.2087 \times 10.2693 = 2.1432\ V/V$

The value still varies a bit from the acquired gain, so I decided to probe the gain at Vx.

```
****      small-signal transfer characteristics
v(vx)/vin
input resistance at vin      = -271.0849m
output resistance at v(vx)   = 1.000e+20
                             = 9.6880k
```

The value above shows that the gain I calculated was undervalued. With the result from above, $A_{V,overall} = -271.0849 \times 10^{-3} \times 10.2693 = -2.7839\ V/V$, which is very close to $-2.7911\ V/V$.

Then I decided to use the input impedance from part (c) (d)

```
input resistance at vin      = 9.7378k
to calculate the gain
```

$$A_V = -27.9820 \times 10^{-6} \times \frac{1}{25.0914 \times 10^{-9} + 234.4641 \times 10^{-9} + \frac{1}{9.7378 \times 10^3}} \times 10.2693$$

$$= -27.9820 \times 10^{-6} \times 9713.2498 \times 10.2693$$

$$= -2.7912\ V/V \Rightarrow \text{which is identical to the simulation}$$

This once again reminds me that when there is voltage difference between source and bulk, I must always taken body conductance into account.

(f)



```
*****
***** pole/zero analysis
*****

input = 0:vin          output = v(vout)

      poles (rad/sec)          poles ( hertz)
real      imag      real      imag
-3.87643g      0.      -616.953x      0.
-15.7140g      0.      -2.50096g      0.

      zeros (rad/sec)          zeros ( hertz)
real      imag      real      imag
17.8238g      0.      2.83675g      0.

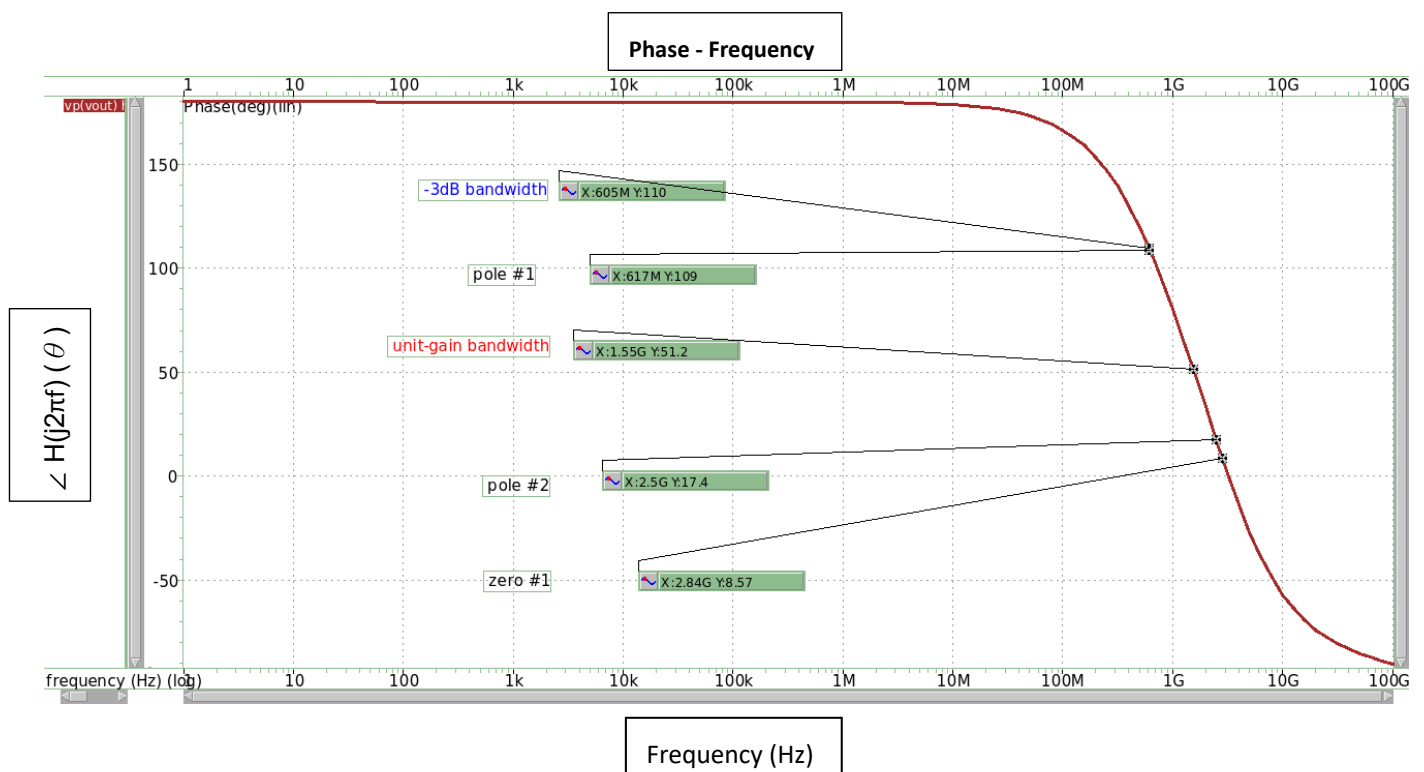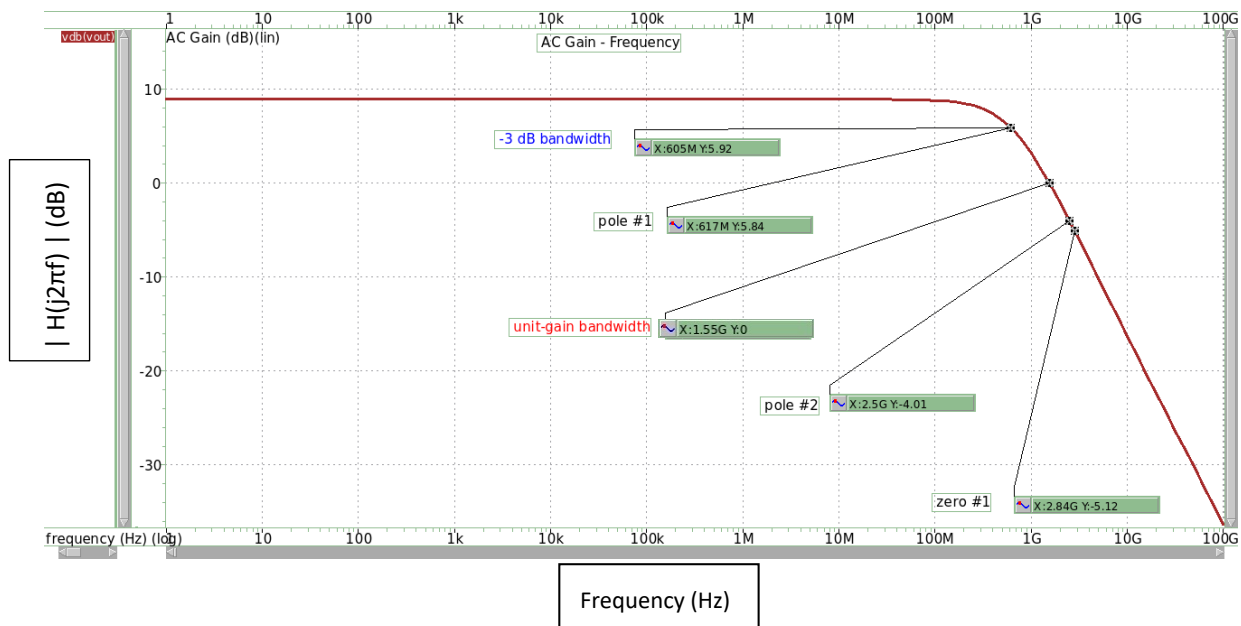***** constant factor = 9.53881g
*****
.protect
***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgain_in_db= 8.9155      at= 6.3096
      from= 1.0000      to= 100.0000g
bw= 607.6032x
ugb= 1.5519g
```



(g)

```
*****
***** pole/zero analysis

input = 0:vin          output = v(vout)

      poles (rad/sec)          poles ( hertz)
real      imag      real      imag
-3.87643g    0.      -616.953x    0.
-15.7140g    0.      -2.50096g    0.



      zeros (rad/sec)          zeros ( hertz)
real      imag      real      imag
17.8238g    0.      2.83675g    0.

*****
```


| element | 0:mp1 | 0:mn1 | 0:mn2 |
|---------|----------|----------|----------|
| model | 0:p_18.1 | 0:n_18.1 | 0:n_18.1 |

| | gm | gds | gmb | cdtot | cgtot | cstot | cbtot | cgs | cgd |
|-----------|-----------|-----------|-----|-------|-------|-------|-------|-----|-----|
| 12.3793u | 27.9820u | 133.8095u | | | | | | | |
| 25.0914n | 234.4641n | 5.1114u | | | | | | | |
| 3.8439u | 5.7637u | 16.6901u | | | | | | | |
| 2.1145f | 5.3665f | 2.0707f | | | | | | | |
| 23.3469f | 43.7262f | 4.0115f | | | | | | | |
| 26.9468f | 45.4197f | 4.8854f | | | | | | | |
| 10.8526f | 20.7142f | 3.6976f | | | | | | | |
| 20.8850f | 37.1263f | 3.1444f | | | | | | | |
| 686.3508a | 1.3438f | 543.4210a | | | | | | | |

| maximum nodal capacitance= | | 6.613E-14 | | on node | | 0:vss | | |
|----------------------------|---|-----------|--------|---------|---------|-------|---|----------|
| nodal capacitance table | | | | | | | | |
| node | = | cap | node | = | cap | node | = | cap |
| +0:vb1 | = | 23.3469f | 0:vb2 | = | 4.0115f | 0:vdd | = | 37.7994f |
| +0:vin | = | 43.7262f | 0:vout | = | 2.0707f | 0:vss | = | 66.1339f |
| +0:vx | = | 12.3664f | | | | | | |

 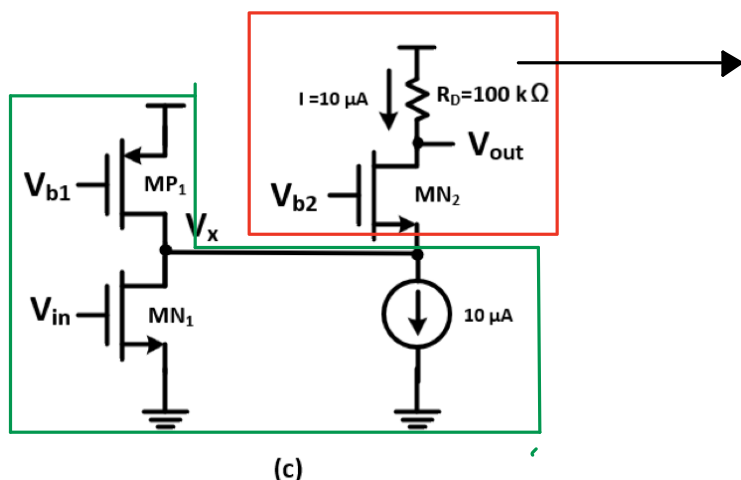

 the resistance is significant larger , so this is clear to be the dominant. pole



$$\begin{aligned} |\omega_{p, out}| &= \frac{1}{R_D \times C_{Dtot, MN2}} \\ &= \frac{1}{100 \text{ k} \times 2.0707 \text{ f}} \\ &= 4829.28 \times 10^6 \text{ (rad/s)} \\ &= 768.6 \text{ MHz} \end{aligned}$$

$$\begin{aligned} &(\gamma_{o, MN1} \parallel \gamma_{o, MP1} \parallel \gamma_{in, MN2}) \\ &= \frac{1}{25 \times 10^{-9} + 234.46 \times 10^{-9} + 9737.8} \\ &= 9713.258 \Omega \end{aligned}$$

For the pole at V_x , since the drain capacitance of MN1 floats from V_{in} to V_x , to avoid the error from miller approximation, I will use

$$+0:vx = 12.3664f$$

$$\Rightarrow |\omega_{p,x}| = \frac{1}{9713.258 \times 12.3664 \times 10^{-15}} = 8.325 \times 10^9 \text{ rad/s}$$

$$= 1.325 \text{ GHz}$$

Comment:

The dominant pole calculated has a certain amount of difference. Comparing to classmates with the same approach of calculating it, they all have a close hand calculation value compare to the simulation value. I notice that the differences between our design is the size of MN2, my channel length of MN2 is $0.35\mu\text{m}$, the neglection of drain-source capacitance will cause larger error because the drain and source are closer in my design, so my speculation would be that the realistic node capacitance would be higher. Without the consideration of drain source capacitance, the equivalence capacitance at node V_{out} is smaller, which causes the pole to be larger, which corresponds to the larger value I acquired from hand calculation.

The second pole isn't close either, the courses from past weeks have taught us that to get the actual transfer function, the direct analysis using KCL and KVL must be done. But if we are simply looking both poles in terms of order, then it is still a good approximation.

There are more to be observed, I found out that with a smaller size of my channel length of MN2, this causes my dominate pole to be 10 times larger compared to my classmates. Meanwhile, the gain is $1.5 \sim 2$ times smaller compared to my classmates. There is a trade-off between gain and bandwidth in this cascade design. I personally think that having larger bandwidth is a better design, because courses of communication system, the need of implementing communication is highspeed circuit.

(h)

Table I Performamance Table

| Work Item | Unit | Specification | Simulation | Calculation |
|-----------------------------|-------------------------|---------------|-----------------|--------------|
| Vdd | V | 1.8 | | |
| | Common Source Amplifier | | | |
| Vin | V | - | 0.4 V | |
| Vb1 | V | - | 1.1 V | |
| Vx | V | 0.5 | 498.4701 mV | |
| Gain($ A_1 $) | V/V | > 90 | 107.774 V/V | 107.7756 V/V |
| | Common Gate Amplifier | | | |
| Vin | V | 0.5 | 0.5 V | |
| Vo | V | - | 796.1436 mV | |
| I | μ A | 10 | 10.0386 μ A | |
| Gain($ A_2 $) | V/V | > 10 | 10.2693 V/V | 10.2708 V/V |
| | Cascade Amplifier | | | |
| Vin | V | - | 0.4 V | |
| Vx | V | 0.5 | 500.3702 mV | |
| Vo | V | - | 799.9505 mV | |
| Gain ($ A_1 \times A_2 $) | V/V | > 1 | 2.7911 V/V | |
| Dominate Pole | MHz | > 55 | 616.953 MHz | 768.6 MHz |
| Unit Gain Bandwidth | MHz | > 70 | 1.5519 GHz | |