

EE3235 Analog Integrated Circuit Analysis and Design I

Homework 2

Elementary Gain Stages

Due date: 2021.10.27 (Wed.) 13:20 (upload to eeclass system)



Suppose $V_{DD}=1.8V$, temperature= $25^{\circ}C$, TT corner in this homework.

Please note that:

1. **No delay allowed.**
2. Please hand in your report using eeclass system.
3. Please generate your report with **pdf** format, name your report as [HWX_studentID_name.pdf](#).
4. Please hand in the spice code file (.sp) for each work. Do not include output file.
5. Please print waveform with [white background](#), and make sure the X, and Y labels are clear.
6. Please do not zip your report.

Part 1 – Common Source Amplifier

(1) DC sweep

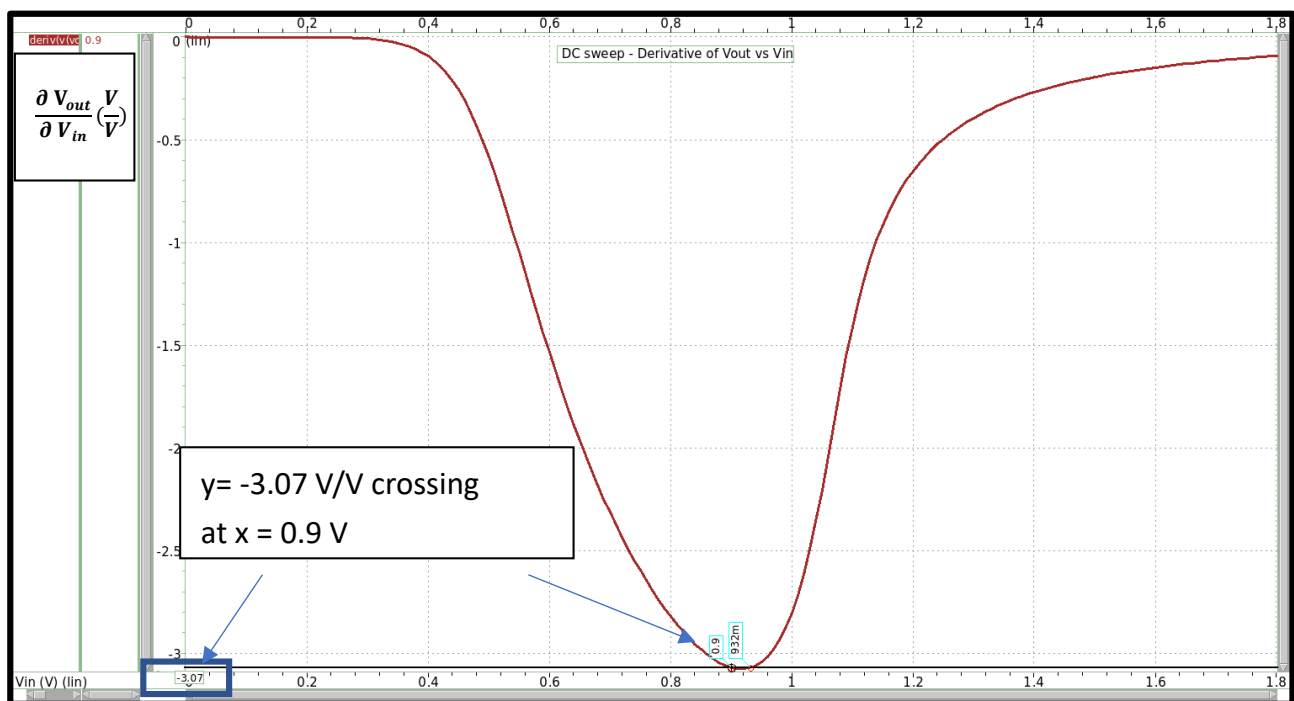 

```
***** dc transfer curves tnom= 25.000 temp= 25.000 *****
vout_derivative= -3.0694
**info** dc convergence successful at Newton-Raphson method
1***** PrimeSim HSPICE -- R-2020.12-SP2 linux64 (May 24 2021 7074677) *****
*****
```

Comment:

I acquired the derivative of V_{out} with respect to V_{in} where $V_{in} = 0.9$ V is -3.07 from the probe and -3.0694 from the .lis file, this is because the cursor from custom waveview rounds it to less decimal place.

(2) TF Analysis

```
****      small-signal transfer characteristics
v(vout)/vin      =      -3.0731
input resistance at      vin      =      1.000e+20
output resistance at v(vout)      =      16.3742k
```

Comment:

The values are close where the relative error is $\left| \frac{-3.0731 - (-3.0694)}{-3.0694} \right| = 0.12\%$, the reason that the results are similar is because the biased voltage is close to the probing voltage. Also, the meaning of derivative of V_{out} with respect to V_{in} is for given small input change at bias point, the value indicates how output change respond to the small change, which is the definition of gain.

(3) Hand Calculation and Discussion

**** mosfets

```
subckt
element 0:ms
model 0:n_18.1
region Saturation
id 48.8227u
ibs -1.948e-20
ibd -103.2106a
vgs 900.0000m
vds 896.7792m
vbs 0.
vth 490.0856m
vdsat 326.7695m
vod 409.9144m
beta 658.9948u
gam_eff 507.4507m
gm 187.8304u
gds 7.0231u
gmb 29.1442u
cdtot 878.3203a
cgtot 1.4683f
cstot 2.0675f
cbtot 1.7458f
cgs 1.1263f
cgd 217.6025a
```

**** resistors

```
subckt
element 0:rd
r value 18.5000k
v drop 903.2208m
current 48.8227u
power 44.0977u
```

TABLE I

COMMON SOURCE PERFORMANCE TABLE

| Working Item | SPEC | Your Design | Hand Calculation |
|--------------|-----------------|---------------------------------------|------------------|
| V_{DD} | 1.8V | 1.8V | 1.8V |
| $V_{in,DC}$ | 0.9V | 0.9V | 0.9V |
| $V_{out,DC}$ | 0.9V | 0.8968 V | 0.89678 V |
| Gain A_v | > 2.8 (V/V) | 3.0731 V/V | 3.07529 V/V |
| R_D | < 100K Ω | 18.5 k Ω | - |
| I_D | < 50 μ A | 48.8227 μ A | - |
| M_S W/L, m | - | $\frac{0.6\mu m}{0.3\mu m}$, $m = 1$ | - |

From .lis file, $g_{ds} = 7.0231 \mu S$ indicating that $r_o = \frac{1}{7.0231 \times 10^{-6}} = 142387.2649 \Omega$

DC Gain

DC Gain for common source amplifier is $A_v = -g_m(r_o || R_D)$
 $= 187.8304 \times 10^{-6}(18500 || 142387.2649) = -3.07529 V/V$

The relative error of DC gain between hand calculation and design is

$$\left| \frac{-3.07529 - (-3.0731)}{-3.0731} \right| = 0.07\% \text{ which is almost identical.}$$

$V_{out,DC}$

The Drain-Source Voltage is

$$V_{DS} = V_{DD} - I_D R_D = 1.8 - 48.8227 \times 10^{-6} \times 18500 = 0.89678 V$$

The relative error of $V_{out,DC}$ between hand calculation and design is

$$\left| \frac{0.89678 - 0.8967792}{0.8967792} \right| = 8.921 \times 10^{-5} \% \text{ which is almost identical.}$$

Output resistance

The output resistance from the transfer function is 16.3742 k Ω

And the hand calculate value is $(18500 || 142387.2649) = 16.37273 k\Omega$

The relative error of Output resistance between hand calculation and design is

$$\left| \frac{16.3727 k - 16.3742 k}{16.3742 k} \right| = 9.16075 \times 10^{-5} \% \text{ which is almost identical.}$$

Other operating point information

```
***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vdd    = 1.8000  0:vin    = 900.0000m  0:vout    = 896.7792m
+0:vss    = 0.

maximum nodal capacitance= 3.813E-15      on node      0:vss

nodal capacitance table
node      = cap      node      = cap      node      = cap
+0:vdd    = 0.      0:vin    = 1.4683f  0:vout    = 878.3203a
+0:vss    = 3.8132f

**** voltage sources

subckt
element 0:vin      0:vdd      0:vss
volts   900.0000m  1.8000  0.
current 0.      -48.8227u  -6.1093a
power   0.      87.8809u  0.

total voltage source power dissipation= 87.8809u      watts
```

Comment:

The relative error of all kinds of variables are negligible for the common source amplifier, this indicates that the small signal model of the common source amplifier from the textbook is a great approximation for the real situation.

(設計過程在下一頁)

Comment and Discussion:

First, I need to know what goals and what condition I need to meet the SPEC.

From formula: $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$

$$V_{out} = 1.8 - I_D R_D \quad \text{and} \quad \text{gain} \cong g_m (r_o \parallel R_D)$$

I supposed that when drain current is precisely $50\mu A$ and V_{out} is biased at $0.9 V$, then I got $R_D = 18 k\Omega$, considering that the drain current should be smaller, so I set $R_D = 18.5 k\Omega$.

Then I use $\frac{5\mu m}{0.18\mu m}$ a common value seen in textbook as testing aspect ratio to test the $\mu_n C_{ox} \frac{W}{L}$, I acquired $\beta = 9.7885 \times 10^{-3}$, and drain current equals to $597.8761 \mu A$.

Then I have to lower the aspect ratio, to neglect channel length modulation, I make the length larger approaching to width while adjusting the aspect ratio, so I make $L = 0.18 \times 15 = 2.7 \mu m$ where I projected the $I_D = \frac{597.8761}{15} = 39.85 \mu A$, but the value is $63.505 \mu A$ causing the NMOS in linear region and doesn't meet the SPEC.

Then, the previous homework reminded me that with longer channel length there exists RSCE, so the threshold voltage drops, therefore the drain current still increases because V_{TH} is in the parentheses of a square order. From previous homework, SCE exists in channel lengths from $180nm$ to $300nm$ so I select $300nm$ as my channel length and channel width to be $\frac{5\mu m}{2.7\mu m} \times 300nm = 556 nm$, so I select $600nm$ to make the aspect ratio equals to 2, an integer value. Then it meets the SPEC where

$$|A_V| = |-3.0731| = 3.0731 \frac{V}{V}, I_D = 48.8227 \mu A, R_D = 18.5 k\Omega, V_{DS} = 896.7792 mV$$



Since the drain current is a little close to the limit, so I try to lower the aspect ratio, so I set the W to $550 nm$ and the drain current drops to $45.2094 \mu A$, so I set $R_D = 20 k\Omega$. But the gain then drops to $3.0583 V/V$, I then again set $W = 500 nm$ and $R_D = 21.5 k\Omega$. The current then drops to $41.7170 \mu A$ and the gain drops to $3.0146 V/V$.

(Both adjustments meet the SPEC)

Trade-offs can be observed throughout the simulation, first I have to decrease my size to make the device in the RCE region. This needs to be supported by advanced technology. And then to achieve smaller drain current, it would impact my gain. So that the tradeoffs of power consumption and gain performance is then observed. If the company is asking for stable and limited power consumption, I would choose the latter case. But since there is no special notification on this design, so I will stick to the original design where a better gain performance is acquired.

Part 2 – Common gate

(1) DC sweep

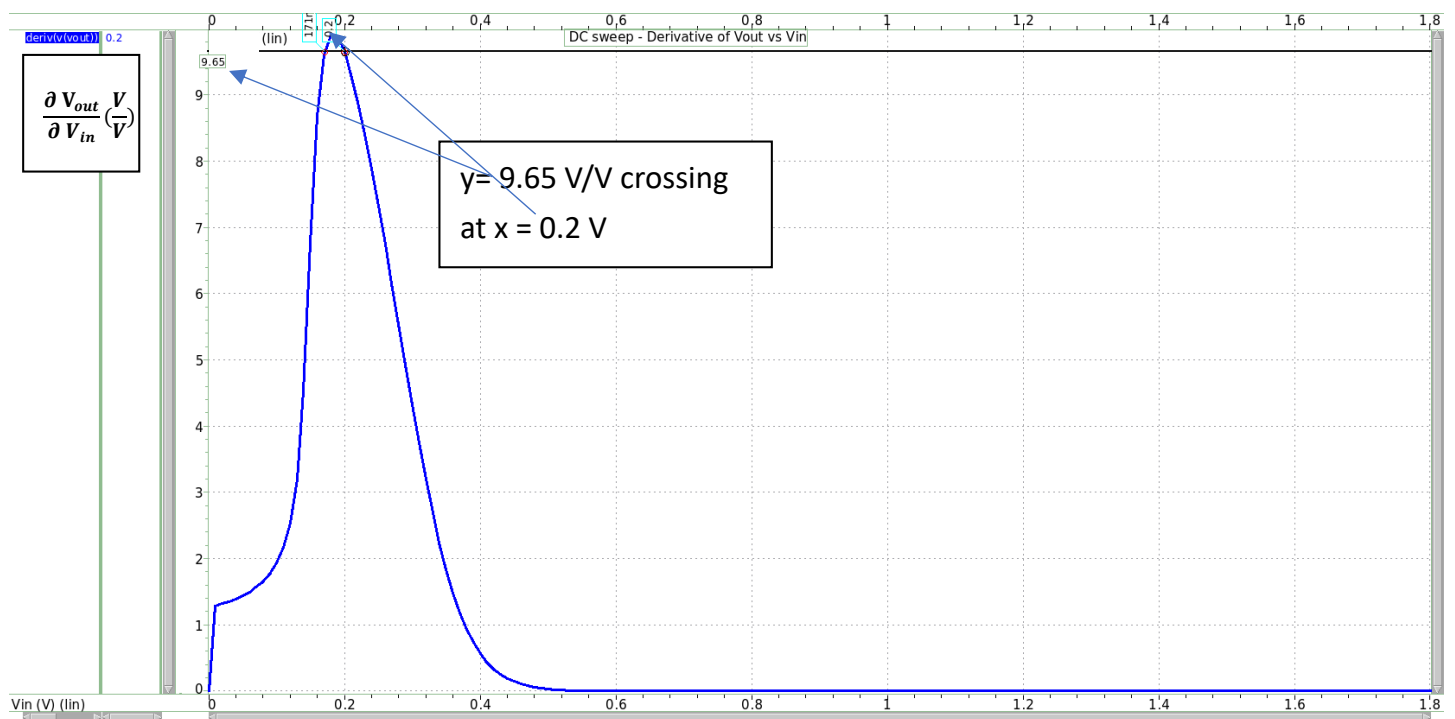 

```
***** dc transfer curves tnom= 25.000 temp= 25.000 *****
vout_derivate= 9.6509
**info** dc convergence successful at Newton-Raphson method
***** PrimeSim HSPICE -- R-2020.12-SP2 linux64 (May 24 2021 7074677) *****
*****
```

Comment:

The derivative I acquired from probing and .lis file are almost the same, the only difference is the rounding figures, same as last part.

(2) TF Analysis

```
****      small-signal transfer characteristics

v(vout)/vin      =      9.4951
input resistance at      vin      =      10.3737k
output resistance at v(vout)      =      81.4848k
```

Comment:

The values are close where the relative error is $\left| \frac{-9.4951 - (-9.6509)}{-9.6509} \right| = 1.61\%$, the reason that the results are similar is because the biased voltage is close to the probing voltage. Also, the meaning of derivative of V_{out} with respect to V_{in} is for given small input change at bias point, the value indicates how output change respond to the small change, which is the definition of gain.

(3) Hand Calculation and Discussion

**** mosfets

```
subckt
element 0:mb
model 0:n_18.1
region Saturation
id 9.1196u
ibs -27.2565a
ibd -122.8729a
vgs 650.0000m
vds 701.7212m
vbs -200.0000m
vth 510.7269m
vdsat 159.5498m
vod 139.2731m
beta 737.1800u
gam eff 512.7680m
gm 99.2682u
gds 2.1205u
gmb 15.1695u
cdtot 1.2603f
cgtot 2.7191f
cstot 3.4299f
cbtot 2.4985f
cgs 2.1761f
cgd 323.8626a
```

**** resistors

```
subckt
element 0:rd
r value 98.5000k
v drop 898.2788m
current 9.1196u
power 8.1919u
```

TABLE II

COMMON GATE PERFORMANCE TABLE

| Working Item | SPEC | Your Design | Hand Calculation |
|--------------|-----------------|----------------------------------|------------------|
| V_{DD} | 1.8V | 1.8V | 1.8V |
| $V_{in,DC}$ | 0.2V | 0.2V | 0.2V |
| $V_{out,DC}$ | 0.9V | 0.90172 V | 0.90172 V |
| Gain A_v | > 8.5 (V/V) | 9.4951 V/V | 8.0885 V/V |
| R_D | < 100K Ω | 98.5 k Ω | - |
| I_D | < 50 μ A | 9.1196 μ A | - |
| V_b | - | 0.85 V | - |
| M_b W/L, m | - | $\frac{0.9\mu m}{0.4\mu m}, m=1$ | - |

From .lis file, $g_{ds} = 2.1205 \mu S$ indicating that $r_o = \frac{1}{2.1205 \times 10^{-6}}$
 $= 471586.89 \Omega$

DC Gain

DC Gain for common gate amplifier is $A_v = g_m(r_o || R_D)$
 $= 99.2682 \times 10^{-6} (471586.89 || 98500) \cong 8.0885 V/V$

The relative error of the DC gain between hand calculation and design is

$$\left| \frac{8.0885 - 9.4951}{9.4951} \right| = 14.81\% , \text{ which a significant difference can be noticed.}$$

$V_{out,DC}$

$$V_{out,DC} = V_{DD} - I_D R_D = 1.8 - 9.1196 \times 10^{-6} \times 98500 \\ = 0.90172 V$$

$$\text{The relative error of } V_{out,DC} \text{ is } \left| \frac{0.90172 - (0.2 + 0.7017212)}{(0.2 + 0.7017212)} \right| = 1.3 \times 10^{-4} \%,$$

which is almost identical between both values.

I/O impedance

$$R_{in} = \frac{r_o + R_D}{1 + g_m r_o} = \frac{471586.89 + 98500}{1 + 99.2682 \times 10^{-6} \times 471586.89} \\ = 11923.12 \Omega$$

$$R_{out} = (r_o || R_D) = 81481.1 \Omega$$

$$\text{The relative error of } R_{in} = \left| \frac{11923.12 - 10373.7}{10373.7} \right| = 14.94\%$$

$$\text{And the relative error of } R_{out} = \left| \frac{81481.1 - 81484.8}{81484.8} \right| = 4.537 \times 10^{-3} \%$$

The input impedance like the DC gain has a relative error around 15%, while the output impedances are almost identical for both value.

With body voltage connected to source voltage (一開始做錯)

**** mosfets

```
subckt
element 0:mb
model 0:n_18.1
region Saturation
id 9.3793u
ibs -2.667e-21
ibd -105.1954a
vgs 600.0000m
vds 699.5858m
vbs 0.
vth 474.4421m
vdsat 147.0031m
vod 125.5579m
beta 902.9562u
gam eff 507.4464m
gm 109.5748u
gds 2.1864u
gmb 19.8498u
cdtot 1.5667f
cgtot 3.3342f
cstot 4.3200f
cbtot 3.2210f
cgs 2.6664f
cgd 398.1024a
```

**** resistors

```
subckt
element 0:rd
r value 96.0000k
v drop 900.4142m
current 9.3793u
power 8.4453u
```

TABLE II

COMMON GATE PERFORMANCE TABLE

| Working Item | SPEC | Your Design | Hand Calculation |
|--------------|-----------------|-------------------------------------|------------------|
| V_{DD} | 1.8V | 1.8V | 1.8V |
| $V_{in,DC}$ | 0.2V | 0.2V | 0.2V |
| $V_{out,DC}$ | 0.9V | 0.89959 V | 0.89959 V |
| Gain A_v | > 8.5 (V/V) | 8.8659 V/V | 8.6943 V/V |
| R_D | < 100K Ω | 96 k Ω | - |
| I_D | < 50 μ A | 9.3799 μ A | - |
| V_b | - | 0.8 V | - |
| M_b W/L, m | - | $\frac{1.1\mu m}{0.4\mu m}$, $m=1$ | - |

From .lis file, $g_{ds} = 2.1864 \mu S$ indicating that $r_o = \frac{1}{2.1864 \times 10^{-6}}$

$$= 457372.8503 \Omega$$

DC Gain

DC Gain for common gate amplifier is $A_v = g_m(r_o || R_D)$

$$= 109.5748 \times 10^{-6} (457372.8503 || 96000) \cong 8.6943 V/V$$

The relative error of the DC gain between hand calculation and design is

$$\left| \frac{8.6943 - 8.8659}{8.8659} \right| = 1.93\% , \text{ which a small difference can be noticed.}$$

$V_{out,DC}$

$$V_{out,DC} = V_{DD} - I_D R_D = 1.8 - 9.3793 \times 10^{-6} \times 9600$$

$$= 0.8995872 V$$

The relative error of $V_{out,DC}$ is $\left| \frac{0.8995872 - (0.2 + 0.6995858)}{(0.2 + 0.6995858)} \right| = 1.556 \times$

$10^{-4} \%$, which is almost identical between both values.

I/O impedance

$$R_{in} = \frac{r_o + R_D}{1 + g_m r_o} = \frac{457372.8503 + 96000}{1 + 109.5748 \times 10^{-6} \times 457372.8503}$$

$$= 10825.71 \Omega$$

$$R_{out} = (r_o || R_D) = 79345.7677 \Omega$$

The relative error of $R_{in} = \left| \frac{10825.71 - 10828}{10828} \right| = 0.02\%$

And the relative error of $R_{out} = \left| \frac{79345.76677 - 79349.2}{79349.2} \right| = 4.326 \times 10^{-3} \%$

The I/O impedance between both values are almost identical

Other operating point information

```

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vb      = 850.0000m 0:vdd      = 1.8000 0:vin      = 200.0000m
+0:vout     = 901.7212m 0:vss      = 0.
maximum nodal capacitance= 3.430E-15 on node 0:vin
nodal capacitance table
node      = cap      node      = cap      node      = cap
+0:vb      = 2.7191f 0:vdd      = 0. 0:vin      = 3.4299f
+0:vout     = 1.2603f 0:vss      = 0.
**** voltage sources
subckt
element 0:vin 0:vb 0:vdd 0:vss
volts 200.0000m 850.0000m 1.8000 0.
current 9.1196u 0. -9.1196u -1.1020p
power -1.8239u 0. 16.4152u 0.
total voltage source power dissipation= 14.5913u watts

```

Comment:

By observation, for NMOS that its body is grounded, the parameters calculated from small signal model related to g_m has large difference comparing to the simulation. Meanwhile, the NMOS that its body is connected to source has negligible difference between the parameters. This result can conclude that the existence of body effect will impact the small signal model especially g_m .

From calculation, I find out that g_m is the reason that causes the gain to be smaller and the input impedance to be larger, the small signal model of common gate amplifier with body effect should have adjustment on the g_m part where the total transconductance should be larger. This suggests that when there is body effect, body conductance should be considered as a factor of boosting total transconductance in common gate amplifier.

經過同學已知有了 Body effect 後的 small signal parameter

$$A_v = (g_m + g_{mb} + g_{ds}) (R_D \parallel r_o) = (99.2682 + 15.165 + 2.1205) \times 10^{-6} (98.5 \times 10^3 \Omega \parallel 471586.89 \Omega) = 9.4969$$

$$\text{relative error} \left| \frac{9.4969 - 9.4951}{9.4951} \right| = 0.019\% \Rightarrow \text{becomes identical}$$

$$R_{in} = \frac{r_o + R_D}{(g_m + g_{mb}) r_o + 1} = \frac{471586.89 + 98500}{1 + (99.2682 + 15.165) \times 10^{-6} \times 471586.89} = 10371.78$$

$$\text{relative error} \left| \frac{10371.78 - 10373.7}{10373.7} \right| = 0.019\% \Rightarrow \text{becomes identical}$$

Comment and Discussion

At first, I use aspect ratio $\frac{W}{L} = \frac{0.36 \mu m}{0.18 \mu m}$ and a large resistor first, since I need a large gain. Then I had drain current of $12 \mu A$, but the gain is only around 3.

| First Trial | | | | | |
|-------------|---------|-----------|-----------|-----------|--|
| W/L | RD | VB | | | |
| 0.36u/0.18u | 75k | 0.8 | | | |
| ID | gds | beta | gm | Vth | |
| 12.1364 | 5.6269u | 726.2551u | 108.5494u | 450.3757m | |

Then I think that I have to increase r_o so that the output resistance will be dominated by the drain resistor. I shift the same ratio but larger L, since from last homework a larger channel length gives smaller output conductance which makes r_o become larger and the gain got closer

| third Trial | | | | | |
|-------------|---------|-----------|----------|-----------|-----------------|
| W/L | RD | VB | | | |
| 1.2u/0.6u | 89k | 0.81 | | | |
| ID | gds | beta | gm | Vth | |
| 10.2188u | 1.4825u | 636.5166u | 97.9919u | 437.0727m | |
| | | | | | gain vds |
| | | | | | 7.8198 690.5309 |

But still the gain is not over the expected value, so I think that I have to increase drain resistor and decrease drain current, but after trying lowering down the channel width and increasing drain resistance, I still can't achieve the gain.

So I think that I have to boost up g_m , but I still need small drain current, then it reminded me that the drain current is affected by V_{TH} by order of 2 but g_m is only affected by order of one, so I can increase the aspect ratio and increase V_{TH} , so that I get a great boost of g_m but a less boost of drain current to sustain the $I_D R_D$ at around 0.9 V. After some trials I achieved the goal.

| sixth Trial | | | | | |
|-------------|---------|-----------|-----------|-----------|-----------------|
| W/L | RD | VB | | | |
| 1.1u/0.4u | 96k | 0.8 | | | |
| ID | gds | beta | gm | Vth | |
| 9.3793u | 2.1864u | 902.9562u | 109.5748u | 474.4421m | |
| | | | | | gain vds |
| | | | | | 8.8659 699.5858 |


Then, I find out that the requirement for the homework is to keep the body of NMOS to ground, which I connected to the source at first, switching body voltage to ground causes V_{SB} become larger. Therefore, V_{TH} rises. This gives me some space to shift up the gate voltage, and then I can use this opportunity to size down my device. Eventually, I stick for $V_B = 0.85 V$, $\frac{W}{L} = \frac{0.9 \mu m}{0.4 \mu m}$, $R_D = 98.5 k\Omega$ where it meets the SPEC.

My design to me is still considered large since the channel length is 5 times of $0.18 \mu m$. The resistance of drain resistor is quite large, this could cause more noise to the device, leakage current will also affect the output. But the good thing is my drain current is low, so the power consumption is low.

Common gate design let me find out that meeting an ideal SPEC often leads me to extreme value, in this case is large resistor and small drain current, but in real life, both should be avoided to create a dependable machine.

Part 3 - Source Follower

(1) DC sweep

 

Comment:

As input DC voltage becomes larger, the derivative of V_{out} with respect to V_{in} becomes larger, this indicates that the change of small signal input creates larger output change when the input DC voltage is biased at higher voltage. So, my design for smaller DC biased stage doesn't display the use for source follower where we need a unity gain. Also, the derivative growth become less steep after the input voltage is larger than 1.4V, we need the input bias stage to be larger than this voltage to make sure that the gain remains a constant.

(2) TF Analysis

```
****      small-signal transfer characteristics

v(vout)/vin          = 821.1060m
input resistance at   vin      = 1.000e+20
output resistance at v(vout)    = 9.5953k
```

(3) Hand Calculation and Discussion

**** mosfets

```

subckt
element 0:md
model 0:n_18.1
region Saturation
id 7.3234u
ibs -97.3412a
ibd -194.5047a
vgs 699.2234m
vds 899.2234m
vbs -900.7766m
vth 587.4121m
vdsat 156.1147m
vod 111.8113m
beta 683.9145u
gam eff 528.3134m
gm 85.6094u
gds 2.8915u
gmb 7.6268u
cdtot 670.5263a
cgtot 1.0629f
cstot 1.3954f
cbtot 1.1668f
cgs 801.9791a
cgd 178.2385a

```

**** resistors

```

subckt
element 0:rs
r value 123.0000k
v drop 900.7766m
current 7.3234u
power 6.5967u

```

TABLE III

SOURCE FOLLOWER PERFORMANCE TABLE

| Working Item | SPEC | Your Design | Hand Calculation |
|--------------|-----------------|--------------------------------------|------------------|
| V_{DD} | 1.8V | 1.8V | 1.8V |
| $V_{in,DC}$ | 1.6V | 1.6V | 1.6V |
| $V_{out,DC}$ | 0.9V | 0.90078 V | 0.90078 V |
| Gain A_V | > 0.8 (V/V) | 0.8211 V/V | 0.8859 V/V |
| R_S | < 150K Ω | 123 k Ω | - |
| I_D | < 30 μ A | 7.3234 μ A | - |
| M_d W/L, m | - | $\frac{0.5 \mu m}{0.25 \mu m}$, m=1 | - |

From .lis file, $g_{ds} = 2.8915 \mu S$ indicating that $r_o = \frac{1}{2.8915 \times 10^{-6}}$
 $= 345841.26 \Omega$

DC Gain

DC gain for source follower is $A_v = \frac{r_o || R_S}{\frac{1}{g_m} + r_o || R_S} = 0.885942 \text{ V/V}$

The relative error of DC gain between hand calculation and design is

$$\left| \frac{0.885942 - 0.8211060}{0.8211060} \right| = 7.89\% \text{, which exists a significant difference where}$$

the hand calculated value is unexpectedly larger.

$V_{out,DC}$

$$V_{out,DC} = I_D R_S = 7.3234 \times 10^{-6} \times 1230000 = 0.9007782 \text{ V}$$

The relative error between hand calculation and design is

$$\left| \frac{0.9007782 - 0.9007766}{0.9007766} \right| = -1.776 \times 10^{-4}\% \text{. Which is almost identical.}$$

Output Impedence

R_{out} for source follower is $\frac{1}{g_m} || r_o || R_S =$

$$\frac{1}{85.6094 \times 10^{-6} + 2.8915 \times 10^{-6} + \frac{1}{123000}} = 10348.65 \Omega$$

The relative error between hand calculation and design is

$$\left| \frac{10348.65 - 9595.3}{9595.3} \right| = 7.85\% \text{ which exists a difference just like the DC}$$

gain where it is unexpectedly larger where the relative error is around 8%.

With body voltage connected to source voltage(一開始做錯)

**** mosfets

```
subckt
element 0:md
model 0:n_18.1
region Saturation
id 11.2505u
ibs -5.057e-21
ibd -97.2445a
vgs 699.9589m
vds 899.9589m
vbs 0.
vth 471.9536m
vdsat 222.3949m
vod 228.0053m
beta 405.2284u
gam eff 507.4472m
gm 82.1898u
gds 1.7514u
gmb 14.0114u
cdtot 749.4013a
cgtot 1.5168f
cstot 2.0429f
cbtot 1.5749f
cgs 1.2087f
cgd 180.7153a
```

**** resistors

```
subckt
element 0:rs
r value 80.0000k
v drop 900.0411m
current 11.2505u
power 10.1259u
```

TABLE III

SOURCE FOLLOWER PERFORMANCE TABLE

| Working Item | SPEC | Your Design | Hand Calculation |
|--------------|-----------------|----------------------------------|------------------|
| V_{DD} | 1.8V | 1.8V | 1.8V |
| $V_{in,DC}$ | 1.6V | 1.6V | 1.6V |
| $V_{out,DC}$ | 0.9V | 0.90004 V | 0.90004 V |
| Gain A_V | > 0.8 (V/V) | 0.8522 V/V | 0.8522 V/V |
| R_S | < 150K Ω | 80 k Ω | - |
| I_D | < 30 μ A | 11.2505 k Ω | - |
| M_d W/L, m | - | $\frac{0.5\mu A}{0.4\mu A}, m=1$ | - |

From .lis file, $g_{ds} = 1.7514 \mu S$ indicating that $r_o = \frac{1}{1.7514 \times 10^{-6}}$

= 570971.794 Ω

DC Gain

DC gain for source follower is $A_v = \frac{r_o || R_S}{\frac{1}{g_m} + r_o || R_S} = 0.8522271 V/V$

The relative error of DC gain between hand calculation and design is

$$\left| \frac{0.8522271 - 0.8521810}{0.8521810} \right| = 0.11\%. \text{ which is almost identical}$$

$V_{out,DC}$

$$V_{out,DC} = I_D R_S = 11.2505 \times 10^{-6} \times 80000 = 0.90004 V$$

The relative error between hand calculation and design is

$$\left| \frac{0.90004 - 0.9000411}{0.9000411} \right| = -1.2222 \times 10^{-6}. \text{ Which is almost identical too.}$$

Output Impedance

R_{out} for source follower is $\frac{1}{g_m} || r_o || R_S =$

$$\frac{1}{82.1898 \times 10^{-6} + 1.7514 \times 10^{-6} + \frac{1}{80000}} = 10369.01 \Omega$$

The relative error between hand calculation and design is

$$\left| \frac{10369.01 - 10372.8}{10372.8} \right| = 0.04\%. \text{ Which is almost identical too.}$$

Other operating point information

```

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vdd    = 1.8000  0:vin  = 1.6000  0:vout  = 900.7766m
+0:vss    = 0.

maximum nodal capacitance= 1.395E-15      on node      0:vout
nodal capacitance table
node      = cap      node      = cap      node      = cap
+0:vdd    = 670.5263a 0:vin  = 1.0629f 0:vout  = 1.3954f
+0:vss    = 0.

**** voltage sources
subckt
element 0:vin 0:vdd 0:vss
volts 1.6000 1.8000 0.
current 0. -7.3234u -2.7011p
power 0. 13.1821u 0.

total voltage source power dissipation= 13.1821u watts

```

Comment:

The same difference can be observed between NMOS that its body is connected to source and the one that doesn't, the difference between parameters from small signal model is negligible if there is no body effect, but an observable difference when there is body effect.

From the calculation, the gain is overvalued comparing to the simulation, this tells that $\frac{1}{g_m}$ is undervalued, which leads to g_m is overvalued in the model, so this means that g_m in the small signal model of source follower with body effect has to be adjusted to a smaller value. This suggest that the body conductance should be considered when there is body effect in source follower that it lowers the total transconductance.

經過同學已知有了 Body effect 後的 small signal parameter

$$A_v = \frac{\frac{g_m r_o R_s}{r_o}}{1 + \frac{(g_m + g_{mb}) r_o R_s}{r_o}} = \frac{85.6094 \times 10^{-6} \times 123 \times 10^3}{1 + (85.6094 \times 10^{-6} + 7.6268 \times 10^{-6}) \times 123 \times 10^3} = 0.8446 \text{ V/V}$$

$$\text{relative error} \left| \frac{0.8446 - 0.8211}{0.8211} \right| = 2.86\% \Rightarrow \text{becomes closer if considering } g_{mb}$$

$$R_{out} = \frac{1}{\frac{1}{R_s} + g_m + \frac{1}{r_o} + g_{mb}} = \frac{1}{\frac{1}{123 \times 10^3} + 85.6094 \times 10^{-6} + 2.8915 \times 10^{-6} + 7.6268 \times 10^{-6}} = 9323.33 \Omega$$

$$\text{relative error} \left| \frac{9323.33 - 9595.3}{9595.3} \right| = 2.83\% \Rightarrow \text{becomes closer if considering } g_{mb}$$

Comment and Discussion

To achieved a good performance of source follower, $A_v = \frac{r_o || R_s}{\frac{1}{g_m} + r_o || R_s}$, I think I have to increase g_m so that it affects the output resistance less, but then after some trials I find out that since I need the $I_D R_s$ to be around 0.9V so that the source resistance is limited, I find out that this is not a good tradeoff, because the gain performance still relies on source resistor more.

So I set the aspect ratio close to 1 and a larger source resistance. after adjusting g_m and R_s for performance, I have reached the goal and I set for the fourth trial.

| Third Trial | | | | | | Dropping the W/L ratio | | | | | |
|-------------|------------|----------|-------------|-------------|-------------|------------------------|--|--|--|--|--|
| W/L | RS | | | | | | | | | | |
| 0.3u/0.3u | 85000 | | | | | | | | | | |
| ID | gds | beta | gm | Vth | | | | | | | |
| 11.312 | 2.1701E-06 | 330.3597 | 7.15409E-05 | 456.9426 | | | | | | | |
| vds | gain | | ro | ro // rd | 1/gm | gain by divider | | | | | |
| 895.1463 | 836.9044m | | 460808.2577 | 71762.75066 | 13978.01817 | 0.836973492 | | | | | |

| Fourth Trial | | | | | | Increasing the W/L ratio | | | | | |
|--------------|------------|-----------|-------------|-------------|-------------|--------------------------|--|--|--|--|--|
| W/L | RS | | | | | | | | | | |
| 0.5/0.4 | 80000 | | | | | | | | | | |
| ID | gds | beta | gm | Vth | | | | | | | |
| 11.2505u | 1.7514E-06 | 405.2284u | 8.21898E-05 | 471.9536m | | | | | | | |
| vds | gain | | ro | ro // rs | 1/gm | gain by divider | | | | | |
| 899.9589m | 852.1810m | | 570971.794 | 70168.54484 | 12166.95989 | 0.852227056 | | | | | |

But same as last part, I originally connected the body to source, so I have to switch it to ground. But the original source is projected to be around 0.9V, so this is a significant drop, this gives me chance to size down the device, I drop down the channel length, which makes drain current larger. I made some adjustment to the source resistor, making it larger. Then I stick to $R_s = 123 \text{ k}\Omega$, $\frac{W}{L} = \frac{0.5\mu\text{m}}{0.25\mu\text{m}}$ which meet the SPEC.

My device has same issue as the CG stage, my source resistor is large which it can cause large noise and the unstable output if leakage current occurs. But I think that the drain current and device is size is acceptable, power consumption is low. Last but not least, regardless of the conditions above, the desired good performance of the source follower is to remain the gain approaching to unity, but what I designed is about 0.82 V/V. This isn't considered a great performance especially I didn't make my device small enough, but since I made NMOS body connected to source accidentally, with lower resistance and length increase for

$\frac{0.4-0.25}{0.25} = 60\%$, gain of 0.85 V/V is acquired. But considering the fact that 60% of length increase only

boost up the gain a little bit, if the device is not asking unity gain for priority, then the device of body connecting to ground that I designed is an overall better one than the device body connected to the source.