

# 110 Fall EE3235 Analog Integrated Circuit Analysis and Design I

## Homework 7 Common Mode Feedback

Due date:2021.01.05 (Wed.) 13:20 pm (upload to eeclass System)

This homework is for you to design a fully-differential amplifier with/without common mode feedback. The problem sets include HSPICE simulations and hand calculations. The SPICE model is cic018.1. Please use the parameters from HSPICE simulation results for hand calculations.

In this homework, please use  $V_{DD}=1.5V$ , temperature= $25^{\circ}C$ .

Also, please set **measdgt** higher than 15 and **numdgt** higher than 7.

**Note that the minimum channel length and width step is  $0.01\mu m$  in this homework.**

Please note that:

1. **No delay allowed.**
2. Please hand in your report using eeclass system.
3. Please generate your report in **pdf** format, name your report as **HWX\_studentID\_name.pdf**.
4. Please hand in the spice code file (.sp) for each work. Do not include the output file.
5. Please print waveform with **white background**, and make sure the X, and Y labels are clear.
6. Please do not zip your report.

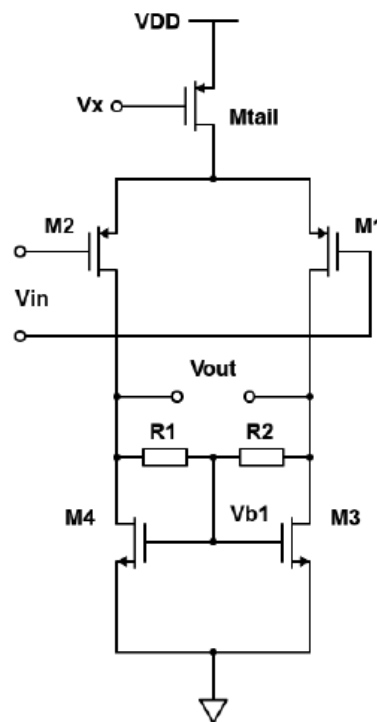



Fig. 1. Differential amplifier with CMFB.

In Fig. 1, please design your  $M_{tail}$  and its bias voltage  $V_x$  to generate the tail current  $5\mu A$ .

(a) Please design your amplifier and input common mode level to achieve differential mode DC gain ( $V_{out}/V_{in}$ ) of 20 and the output common mode level of 0.7V.
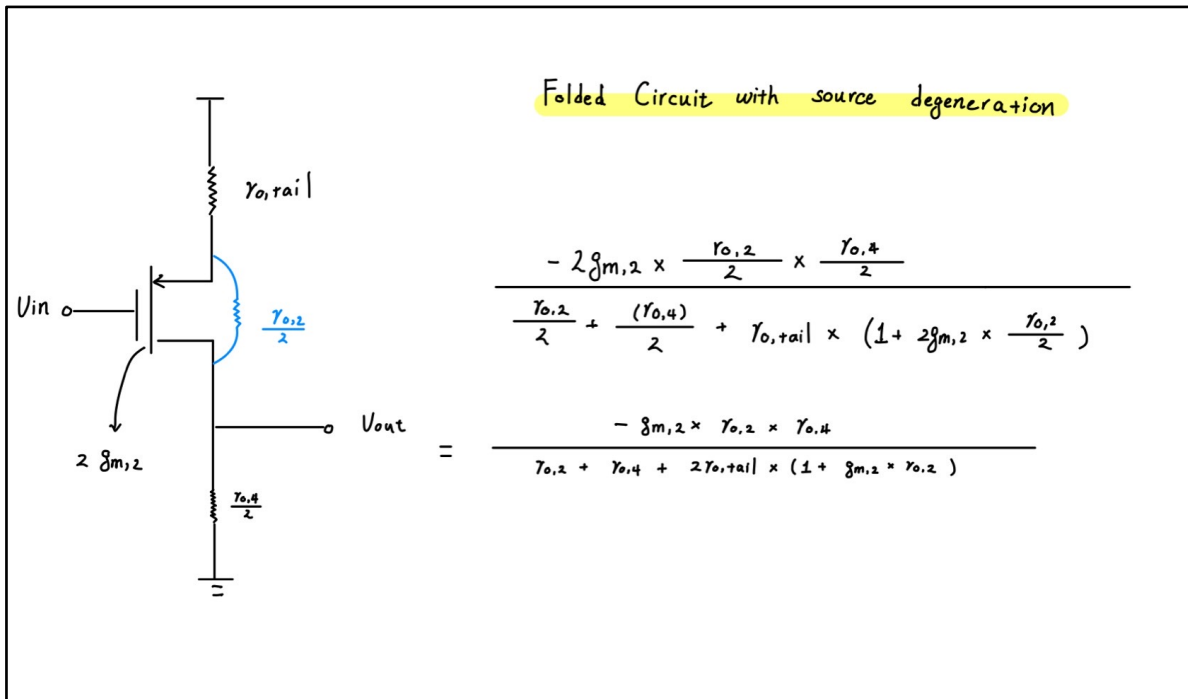
### Design Flow:

The first trial is a mess without considering through the model so that my common mode gain is not strongly suppressed even with common mode feedback system. Thus, I remove the resistor pair and calculated the common mode gain without considering body effect to see what parameters should I set stage for.



From above formula, I observed that the if the  $r_o$  of  $M_{1(2)}$  and the tail MOS is larger compared to the  $r_o$  of the  $M_4$  then the denominator of the above formula can be simplified to  $2 \times r_{o,tail} \times (g_{m,2} \times r_{o,2})$  where since the multiplied value of two resistance is high. Then calculated with the numerator, the common mode gain without feedback can approximated as  $V_{CM,no\ FB} \cong \frac{-r_{o,4}}{2 \times r_{o,tail}}$  so the main goal is to increase the  $r_o$  of  $M_2$  and  $M_{tail}$  while maintaining a smaller  $r_o$  of  $M_4$  for reaching output common level of 0.7 V.

There is another SPEC that I have to achieve, which is drain current of  $5\mu A$ . The relatively predictable is  $M_{3,4}$  since the gate and drain are in same voltage level and we want to set the level to 0.7V, thus through calculation  $\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.7 - V_{TH})^2 = 2.5 \times 10^{-6}$  and from previous homework that  $\mu_n C_{ox}$  can be

approximated by  $325 \mu\text{A}/\text{V}^2$ , so the equation can be rewritten as  $\frac{W}{L} \cong \frac{0.015}{(0.7 - V_{TH})^2}$  and the threshold voltage encountered for NMOS is typically 0.5~0.4V. so through the above approximation, I will expect to see that the size of the aspect ratio of NMOS is less than 1, use threshold voltage = 0.45V as approximation, I would have to start by using  $W/L = 1/5$  as a starting design size.

Starting with size of 0.3/1.5 for the NMOS where  $0.3\mu\text{m}$  is the minimum width for this manufacture. And then first set the input common level at 0.7 V where it is at the midpoint of the circuit. And then set the resistor of the feedback system to 100k where it is sufficiently large to serve a stable feedback. The NMOS part is partially deterministic, then I move the focus point to the Tail MOS.

From earlier analysis, I am looking for a large  $r_o$  for the tail MOS, so I will have to set a small aspect ratio and a large channel length to do that, thus I started to increase from  $5\mu\text{m}$  all the way to  $40\mu\text{m}$  for large tail resistance with aspect ratio slightly higher than 1. And the threshold voltage of the PMOS of is usually around 0.5 V so I set the bias level of the gate to 0.9 V where  $V_{SG} = 1.5 - 0.9 = 0.6\text{V}$  so that when  $V_{DD}$  drops to 1.425 V, the tail is still in saturation. But with the size constrain, the  $g_m$  is not high enough to increase to the drain current, the current by that time is slightly below  $1\mu\text{A}$ , so I set  $m=6$  to the tail MOS for higher drain current.

Also from the other part from earlier analysis,  $M_{1,2}$  has to have a large  $r_o$  also, so the channel length is also large with small aspect ratio where I set it to 2, about 2 times larger than the tail MOS, acknowledging that the bulk is connected to  $V_{DD}$  but the source isn't, so that the threshold voltage is larger than the tail MOS where it is around 0.55 V so that I decrease my input level from 0.7V to 0.6V. Same thing happens with  $M_{1,2}$  where the transconductance is not strong enough thus I have to increase the  $m$  of  $M_{1,2}$ .

Then I want my desired output level to be at 0.7 V, the output level was at 0.57V at the moment, the way to raise up the level is increasing the length of the NMOS where simultaneously decrease the aspect ratio which makes the  $V_{GS}$  increases so that it can sustain same drain current. From the drain current formula I can calculated that the aspect ratio has to be dropped from 1/5 to about 1/6 for the output common level to

raise up to 0.7V, so I switch from 0.3/1.5 to 0.3/1.75, but the output level is slightly lower, so then I increase the minimum step of 0.01 u to raise the point.

Then for the  $V_{DD}$  test, increasing to 1.575V has no hardship for 5 MOS to stay in the saturation region, but suppressing it to 1.425V, makes all  $V_s$  of NMOS to be suppressed, then  $M_{2(1)}$  is prone to entering subthreshold, which means I have to decrease the input common level making sure  $V_{SG}$  of the  $M_{2(1)}$  is large enough to stay in linear when  $V_{DD}$  is suppressed, so I have to drop m for the PMOS and then readjusted the W/L to match the drain current while making sure that the output common level is at the 0.7V.

Eventually, I reach the SPEC with slightly higher  $M_4$  channel length and slightly smaller  $M_2$  width for the MOS to be less prone to enter subthreshold when  $V_{DD}$  is altered. The final part is to design the differential gain with the support of the resistor of the common mode feedback system. The differential gain can be calculated by  $g_{m,2} \times (r_{o,2} \parallel r_{o,4} \parallel R_1)$ . Since the gain is adjusted after the stage is set, I then have the first 3 parameters.

利用excel 的目標搜尋，找到 $R_1 = 585110 \Omega$  時會讓 differential gain 變成近乎20 V/V

Differential gain	gm2 (S)	ro2 ( $\Omega$ )	ro4 ( $\Omega$ )	R1 ( $\Omega$ )
19.99998382	3.79376E-05	35860349.43	6253402.497	585110.0658

I set the resistance to 585 k  $\Omega$  to reach the SPEC.

(b) Print out the small-signal parameters using .op command.

```
***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vb1    = 700.20231486m 0:vcm_in = 500.00000000m 0:vdd      = 1.50000000
+0:vin     = 0.            0:vin_left= 500.00000000m 0:vin_right= 500.00000000m
+0:vout_left= 700.20231527m 0:vout_right= 700.20231445m 0:vp      = 1.14085707
+0:vss     = 0.            0:vx      = 900.00000000m

**** mosfets

subckt
element      0:mtail      0:m1      0:m2      0:m3
model        0:p_18.1      0:p_18.1      0:p_18.1      0:n_18.1
region       Saturation   Saturation   Saturation   Saturation
id           -5.00375401u  -2.50187883u  -2.50187883u  2.50188240u
ibs          4.6559651e-22  1.32033605f  1.32033605f  -1.6297974e-21
ibd          4.33791741f    2.94033758f  2.94033758f  -65.78657886a
vgs          -600.00000000m -640.85707497m -640.85707497m 700.20231486m
vds          -359.14292503m -440.65476052m -440.65475970m 700.20231445m
vbs          0.            359.14292503m 359.14292503m 0.
vth          -457.19064737m -562.82792429m -562.82792429m 356.68486015m
vdsat        -141.95818482m -104.81385791m -104.81385791m 294.97371197m
vod          -142.80935263m -78.02915068m  -78.02915068m 343.51745472m
beta         490.38179660u  547.84928067u  547.84928067u  48.42213491u
gam_eff      557.08465667m  554.67912047m  554.67912047m 507.44640053m
gm           56.21882891u   37.93751514u   37.93751514u   13.68655442u
gds          86.70041054n   27.90780250n   27.90780250n   159.88838139n
gmb          17.30681156u   10.04865690u   10.04865690u   2.54868331u
cdtot        710.35523701f  95.42951902f   95.42951906f   518.45197988a
cgtot        68.25367796p    4.75370482p    4.75370482p    3.63188690f
cstot        76.14530686p    5.10513622p    5.10513622p    4.05278893f
cbtot        24.30919161p    1.61298214p    1.61298214p    1.75627593f
cgs          62.09174329p    4.27952759p    4.27952759p    3.24809789f
cgd          273.92067225f    31.41398601f   31.41398602f   106.51673223a
cgd          106.51673221a
```

```
**** resistors

subckt
element      0:r1      0:r2
r value      585.00000000k 585.00000000k
v drop       409.60723702p -409.60779213p
current      700.18331114a -700.18426005a
power        2.8680015e-25 2.8680093e-25
```

(c) Please use .tf command to simulate the differential and common mode gain, and print out the results.

Differential mode gain

```
**** small-signal transfer characteristics


v(vout_left,vout_right)/vin = -19.9967
input resistance at vin = 1.000e+20
output resistance at v(vout_left,vout_right) = 1.0542k
```

Common mode gain

```
**** small-signal transfer characteristics


v(vout_left)/vcm_in = -2.4724m
input resistance at vcm_in = 1.000e+20
output resistance at v(vout_left) = 299.6622k
```

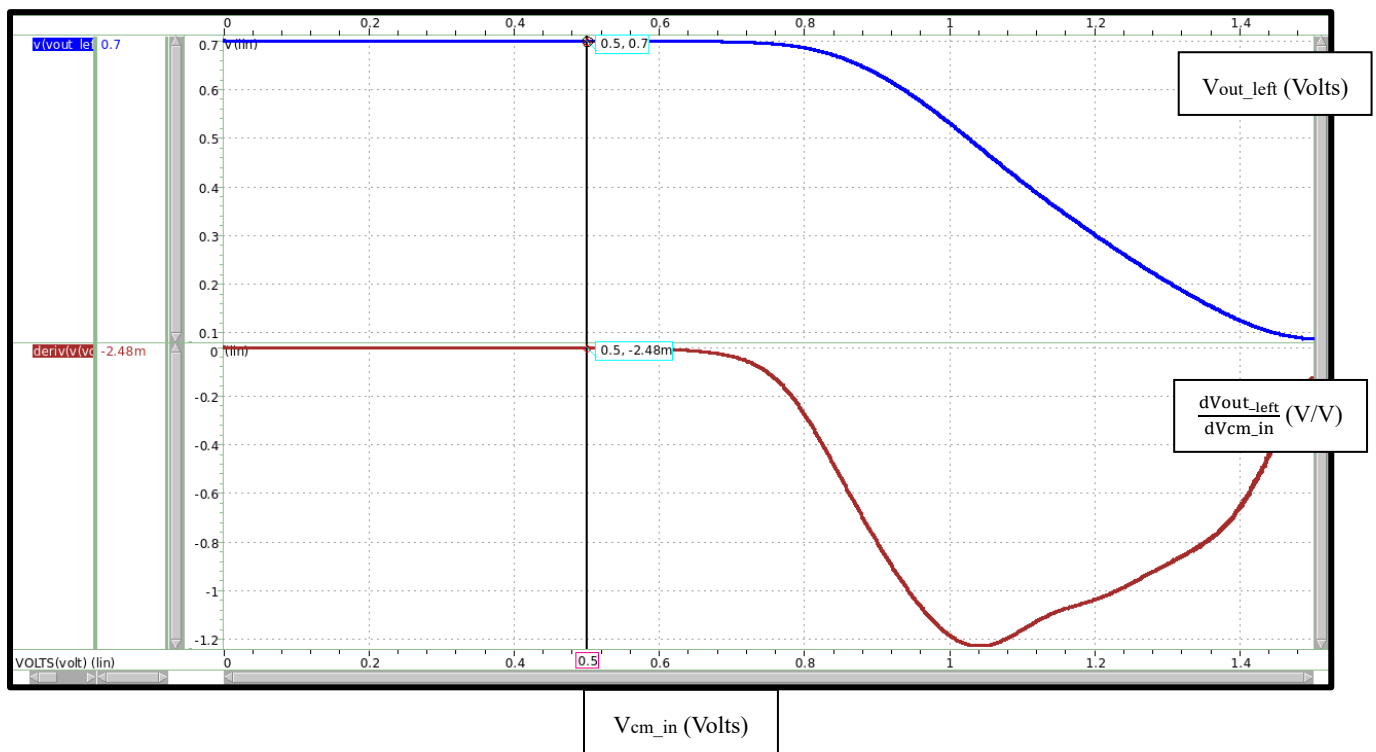(d) Please sweep the input common mode voltage from 0V to  $V_{DD}$ , probe the output common mode voltage and its slope. Mark the bias point on the figures and explain what happens when the input common mode voltage increases.




Comment:

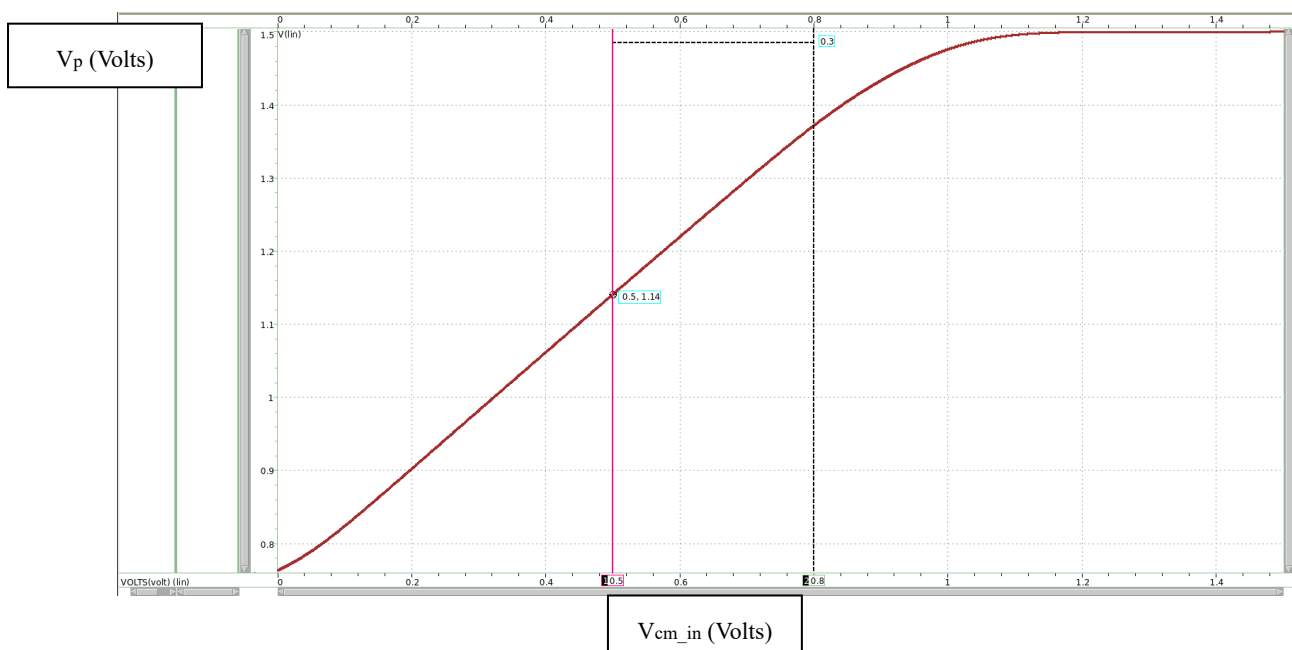
The common mode gain started to increase and the output common level starts to fall when  $V_{cm\_in}$  is approaching 0.8V. From the graph below, we see that the PMOS wants to sustain the same drain current thus the voltage of its source and the tail MOS' drain (denoted as  $V_p$ ) is then raised to a higher level since the gate of  $M_{1,2}$  is increasing.



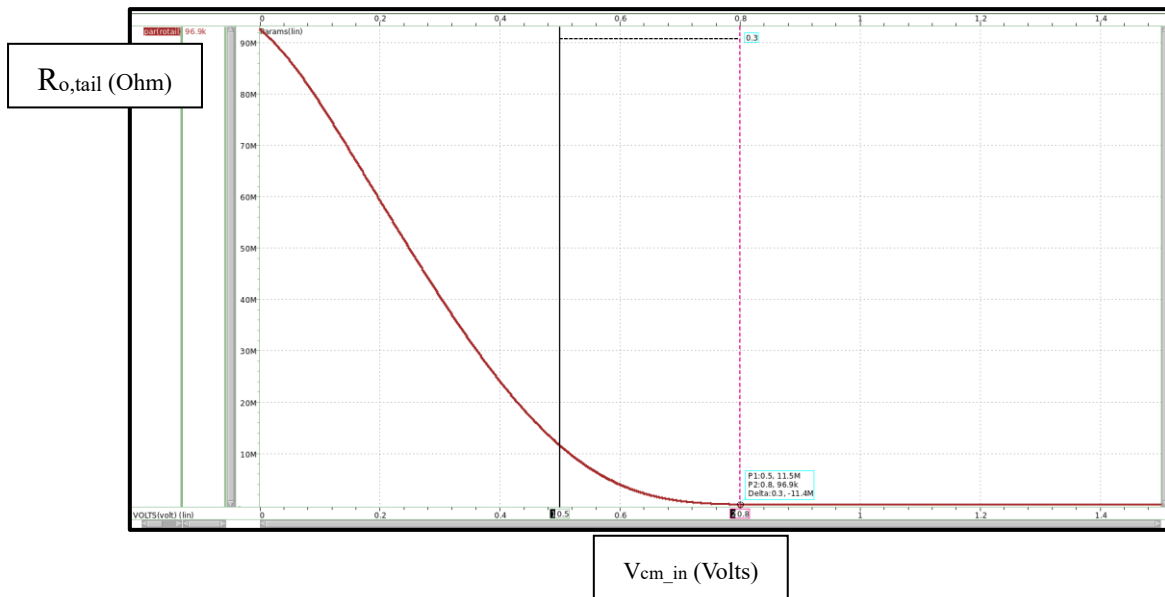Then, while  $V_p$  is increasing, the  $V_{DD}$  remains the same. The  $V_{SD}$  of the tail MOS decreases which leads the tail MOS into linear region, then the drain current started to decrease and the output resistance of the tail MOS starts to decrease, thus the effect of degeneration is not strong enough to suppress the common mode gain, causing the common mode gain started to increase.



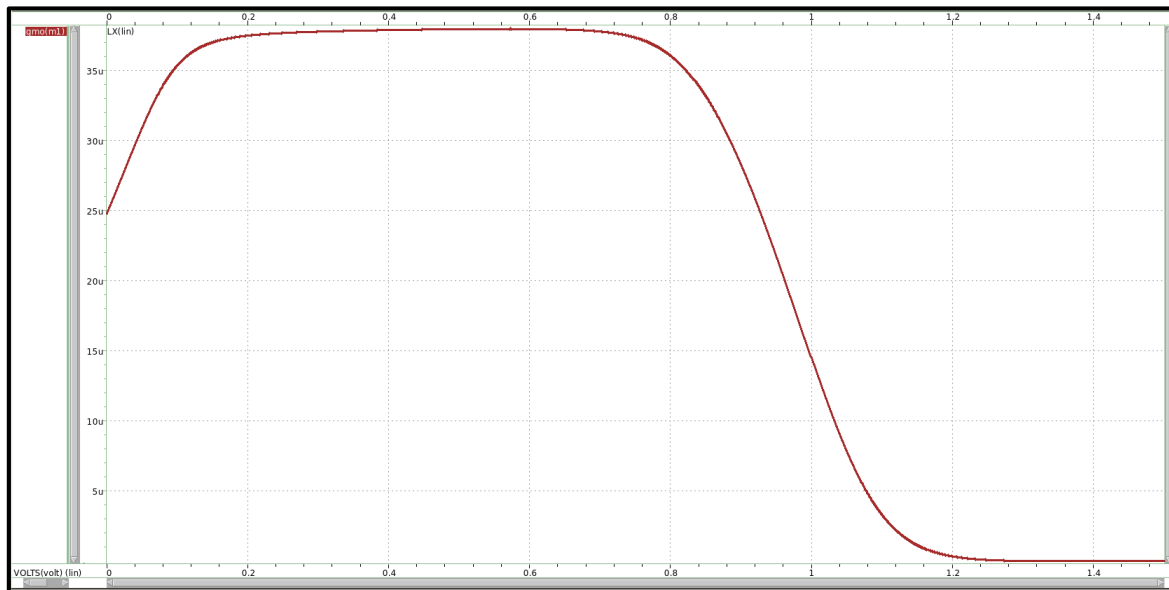
But when the  $V_{cm,in}$  keeps increasing,  $M_{1,2}$  started to fall into subthreshold region then the transconductance started to fall, causing the common mode gain then again becomes smaller.



As a result, I observe that the common mode gain started to increase as  $V_{cm,in}$  increases because the tail MOS falls into linear region so it's  $r_o$  drops. Then  $V_{cm,in}$  increases to an extent that  $M_1$  falls into subthreshold which the transconductance drops rapidly, which causes the common mode gain then again drops. This matches the slope graph.

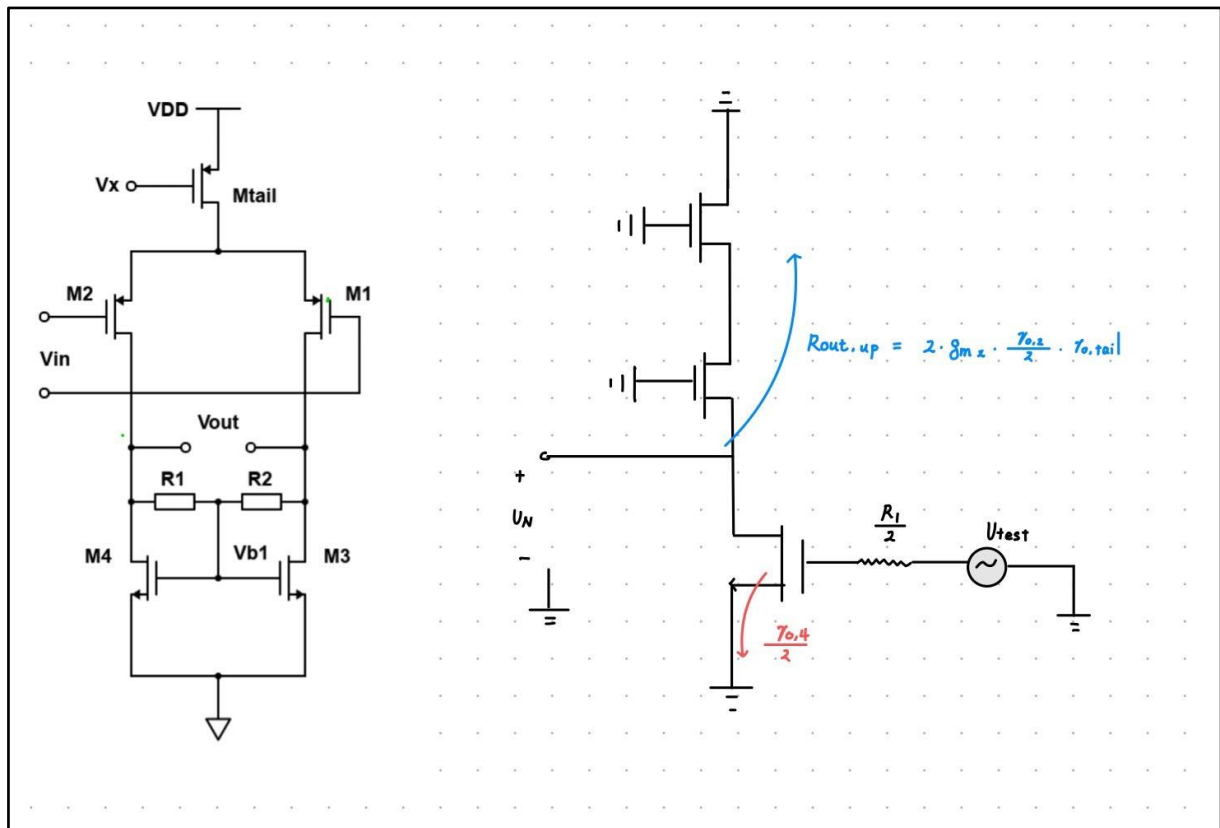(e) The common mode feedback system can be illustrated by the concept shown in Fig. 2. Please simplify Fig. 2 based on Fig. 1. Calculate the common mode gain with the small-signal parameters and the block diagram you draw.

First, calculate the loop gain of this common mode feedback of the system. By breaking up the loop at the common output node, where I use a test voltage  $V_{Test}$  to go into the path of the feedback system. Then folds the circuit, where the output resistance looking up is  $2 \times g_{m,2} \times \frac{r_{o,2}}{2} \times r_{o,tail}$  and output resistance looking down is  $\frac{r_{o,4}}{2}$




Thus, the loop gain is  $\frac{V_N}{V_{Test}} = 2 \times g_{m,4} \times (\frac{r_{o,4}}{2} \parallel 2 \times g_{m,2} \times \frac{r_{o,2}}{2} \times r_{o,tail})$

gm2 (S)	ro2 (Ω)	ro4 (Ω)	gm4 (S)	ro,tail (Ω)
3.79375E-05	35832272.96	6254363.146	1.36866E-05	11533970.76

$$\text{loop gain} = -85.5836 \text{ (V/V)}$$

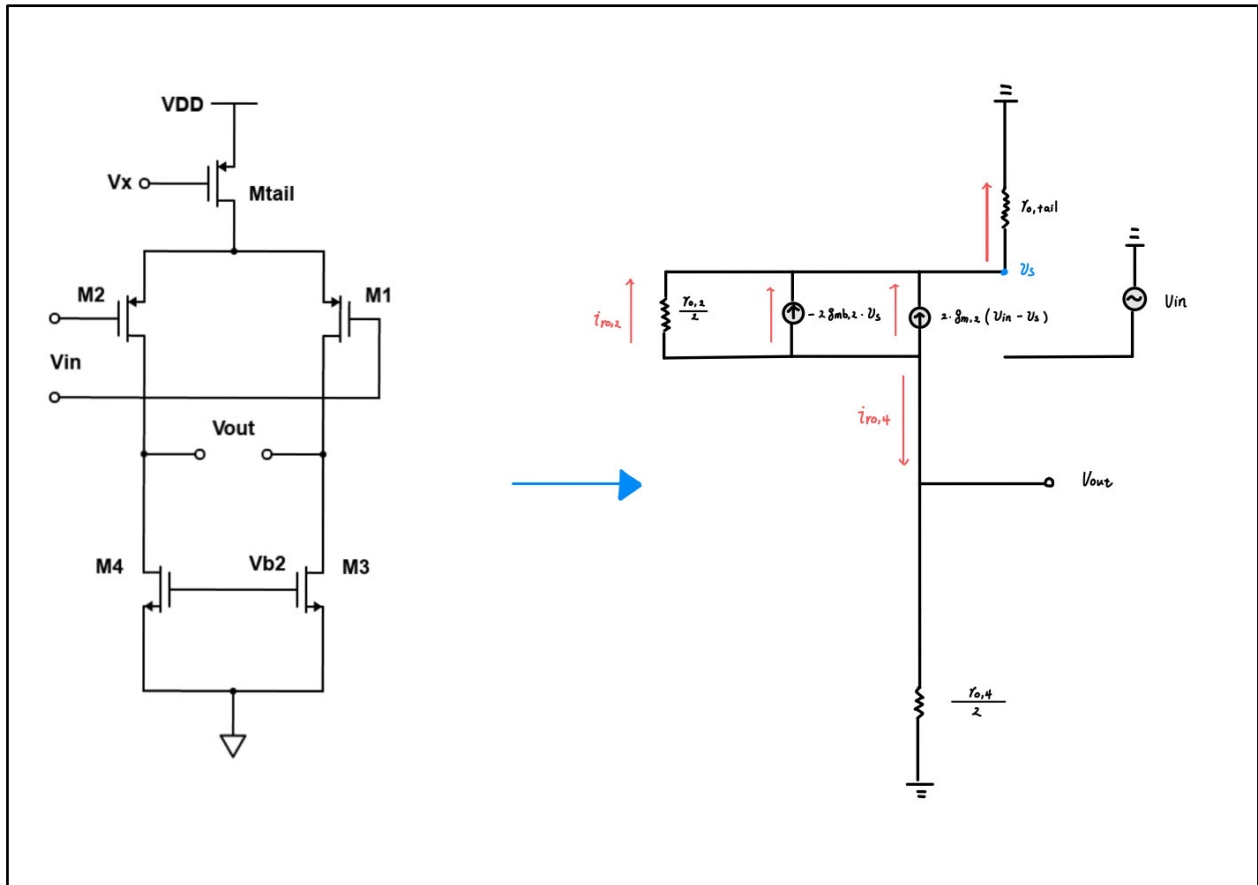Then calculate the open-loop gain for the system without the common mode feedback using folded circuit method.





$$\begin{cases} \frac{2 V_{out}}{r_{o,4}} + \frac{2 (V_{out} - V_s)}{r_{o,2}} - 2 \cdot g_{m,2} V_s + 2 \cdot g_{m,2} (V_{in} - V_s) = 0 \\ \left[ 2 \frac{(V_{out} - V_s)}{r_{o,2}} - 2 \cdot g_{m,2} V_s + 2 \cdot g_{m,2} (V_{in} - V_s) \right] \cdot r_{o,tail} = V_s \end{cases}$$

$$\frac{2 V_{out}}{r_{o,2}} \times r_{o,tail} + 2 \cdot g_{m,2} V_{in} \cdot r_{o,tail} = (1 + 2 \cdot g_{m,2} \cdot r_{o,tail} + 2 \frac{r_{o,tail}}{r_{o,2}} + 2 \cdot g_{m,2} \cdot r_{o,tail}) V_s$$

$$V_s = \frac{\frac{2 V_{out}}{r_{o,2}} \times r_{o,tail} + 2 \cdot g_{m,2} V_{in} \cdot r_{o,tail}}{1 + 2 \cdot g_{m,2} \cdot r_{o,tail} + 2 \cdot g_{m,2} \cdot r_{o,tail} + 2 \frac{r_{o,tail}}{r_{o,2}}}$$


$$\frac{2 V_{out}}{r_{o,4}} + \frac{2 V_{out}}{r_{o,2}} + 2 \cdot g_{m,2} V_{in} = \left( \frac{2}{r_{o,2}} + 2 \cdot g_{m,2} + 2 \cdot g_{m,2} \right) \frac{\frac{2 r_{o,tail}}{r_{o,2}} \times V_{out} + 2 \cdot g_{m,2} V_{in} \cdot r_{o,tail}}{1 + 2 \cdot g_{m,2} \cdot r_{o,tail} + 2 \cdot g_{m,2} \cdot r_{o,tail} + 2 \frac{r_{o,tail}}{r_{o,2}}}$$

$$A_{CM} = \frac{2 \cdot g_{m,2} (1 - \tau \cdot r_{o,tail})}{\left( \frac{2 \tau \cdot r_{o,tail}}{r_{o,2}} - \frac{2}{r_{o,4}} - \frac{2}{r_{o,2}} \right)}$$

gmb2 (S)	gm2 (S)	ro2 (Ω)	ro4 (Ω)	ro,tail (Ω)	τ
1.00487E-05	3.79375E-05	35832272.96	6254363.146	11533970.76	8.66222E-08

$$A_{CM,opened-loop} = -0.214000219 \text{ (V/V)}$$

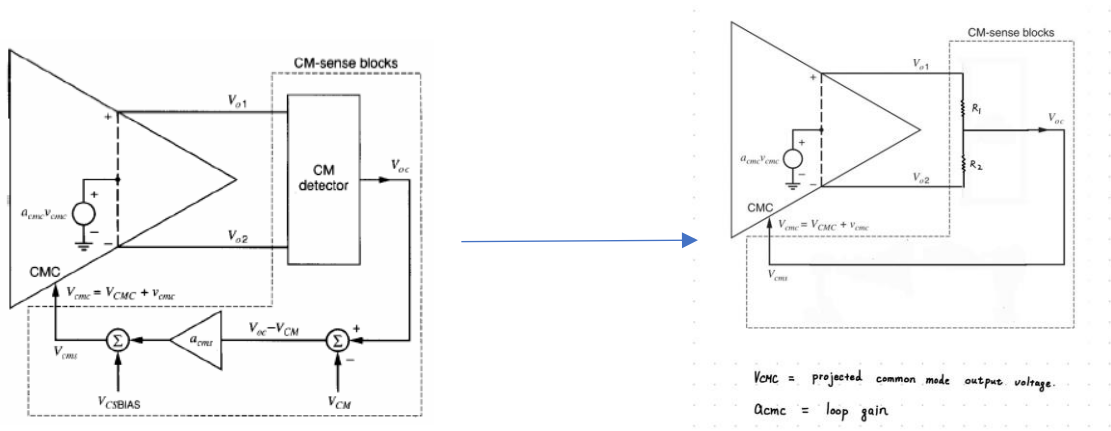The below left figure can be simplified to the below right figure



Where the  $(a_{cm} \times a_{cms})$  product is the calculated loop gain and  $a_{cms}$  is 1,  $V_{CMC}$  equals to the projected common mode output voltage.

Then, referenced from “Analysis and Design of Analog Integrated Circuits 4th Edition”, Paul R. Gray, Paul J. Hurst, Stephen H. Lewis, Robert G. Meyer.

$a'_{cm} = \frac{a_{cm}}{1 + a_{cms}(-a_{cmc})}$  where  $a'_{cm}$  is the common mode gain with CMFB, and  $a_{cm}$  is the common mode gain without CMFB and  $a_{cms}(a_{cmc})$  is the loop gain calculated earlier.

$$a'_{cm} = \frac{a_{cm}}{1 + a_{cms}(-a_{cmc})} = \frac{-0.214000219}{1 + 1 \times (85.58361202)} = -0.002471602 \text{ (V/V)}$$

ACM with CMFB (calculated)	Acm with CMFB (simulation)	error	loop gain
-0.002471602	-0.0024724	-0.032%	-85.58361202

Comment:

The calculated value is identical to the simulation value, which tells that the loop simplified is correct.


(f) In Fig. 3, based on your design in (a), please remove R1 and R2, design the bias voltage  $V_{b2}$  to achieve the output common mode level of 0.7V.

Design Flow:

Originally, I use the drain current formula to find the  $V_{b2}$   $V_{b2} = \sqrt{\frac{2 \times 2.50188240 \times 10^{-6}}{48.42213491 \times 10^{-6}}} + 0.356684860515 = 0.6781445173 \text{ V}$


This value is too inaccurate since square law isn't an accurate method. So instead of calculating for it, observe how the output common voltage changes with  $V_{b2}$ .

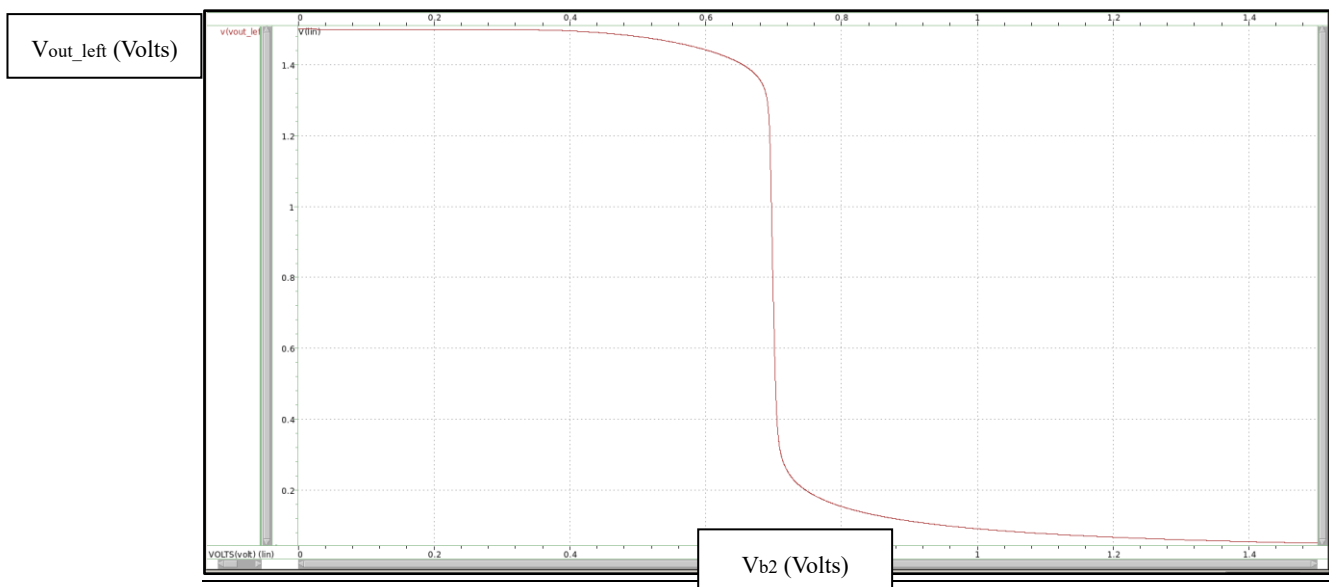First use DC sweep to see how the output common level changes when  $V_{b2}$  changes.



I observe that there is a steep change when  $V_{b2}$  approaches to 0.7 V from both sides and the output level = 0.7 V is in the range in between the steep slope.

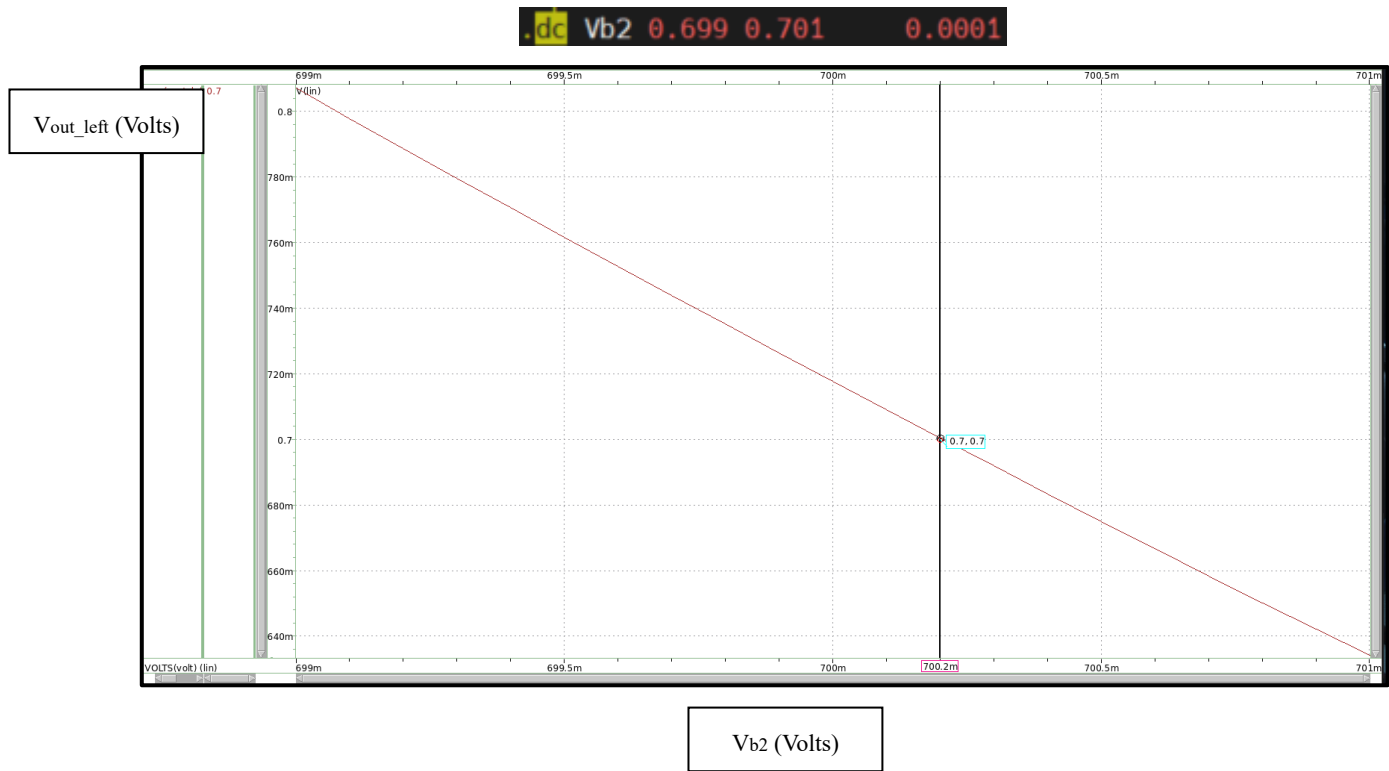Then, use DC sweep around the region of 0.699 V to 0.701 V with 0.0001V/ step to find the point to estimate the input  $V_{b2}$  where the output common level is 0.7 V, I found out that when  $V_{b2}$  is 0.7002 mV the output level is about 0.7 V, but the figure rounding is rough in waveview, thus more significant digit needs to be added to 0.7002 mV to achieve more accurate output level.



Then  $V_{b2}$  is set to 700.2046 mV for the output level to be 700.00680174 mV, the result is in the below figure.

```

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vb2     = 700.20460000m 0:vcm_in = 500.00000000m 0:vdd      = 1.50000000
+0:vin     = 0.          0:vin_left= 500.00000000m 0:vin_righ= 500.00000000m
+0:vout_lef= 700.00680174m 0:vout_rig= 700.00680174m 0:vp       = 1.14085696
+0:vss     = 0.          0:vx      = 900.00000000m

```

(g) Please compare the feedback voltage  $V_{b1}$  in Fig. 1 with the bias voltage  $V_{b2}$  in Fig. 3.

$V_{b1}$ (mV)	$V_{b2}$ (mV)
700.2023149	700.2046

Comment:

The  $V_{b2}$  is the same  $V_{b2}$  until the 6<sup>th</sup> significant digit after the decimal point (in V). Meaning that almost the same value of bias voltage applied to the gate of the NMOS gives the same common output level.

(h) Please use .tf command to simulate the differential and common mode gain, and print out the results.

### Differential mode gain

```

****      small-signal transfer characteristics

v(vout_left,vout_right)/vin      = -202.0202
input resistance at vin          = 1.000e+20
output resistance at v(vout_left,vout_right) = 10.6502x
  
```

### Common mode gain

```


****      small-signal transfer characteristics

v(vout_left)/vcm_in              = -214.0315m
input resistance at vcm_in       = 1.000e+20
output resistance at v(vout_left) = 5.7890x
  
```

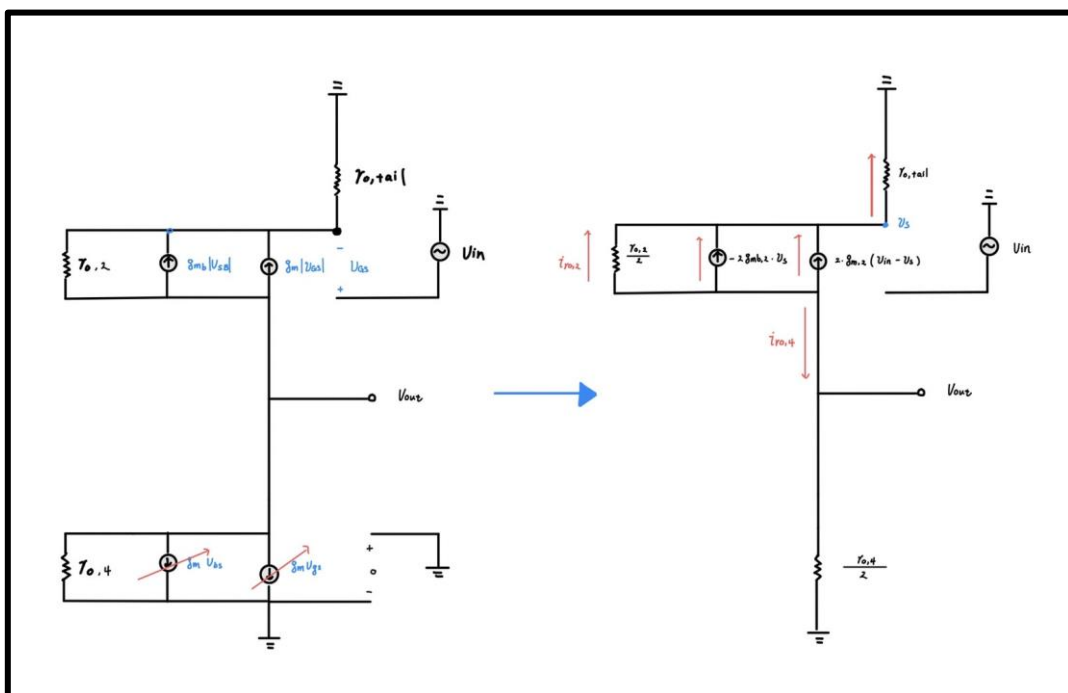(i) Please calculate the common mode gain with the small-signal parameters.

```

**** mosfets
subckt
element      0:m1      0:m2      0:m3
model        0:p_18.1  0:p_18.1  0:p_18.1
region       Saturation Saturation Saturation Saturation
id           -5.00375402u -2.50187884u -2.50187884u 2.50188242u
ibs          4.6559651e-22 1.32033647f 1.32033647f -1.6297974e-21
ibd          4.33791878f 2.94105636f 2.94105636f -65.76820927a
vgs          -600.00000000m -640.85696155m -640.85696155m 700.20460000m
vds          -359.14303845m -440.85015981m -440.85015981m 700.00680174m
vbs          0. 359.14303845m 359.14303845m 0.
vth          -457.19064737m -562.82795375m -562.82795375m 356.68588325m
vdsat        -141.95818482m -104.81376930m -104.81376930m 294.97467160m
vod          -142.80935263m -78.02900780m -78.02900780m 343.51871675m
beta         490.38179660u 547.84928754u 547.84928754u 48.42213593u
gam_eff      557.08465667m 554.67911977m 554.67911977m 507.44640053m
gm            56.21882909u 37.93755188u 37.93755188u 13.68650233u
gds          86.70030129n 27.88497944n 27.88497944n 159.91406317n
gmb          17.30681161u 10.04866619u 10.04866619u 2.54868515u
cdtot        710.35480689f 95.41860549f 95.41860549f 518.47879693a
cgtot        68.25367770p 4.75369525p 4.75369525p 3.63189093f
cstot        76.14530696p 5.10513915p 5.10513915p 4.05279021f
cbtot        24.30919157p 1.61297823p 1.61297823p 1.75629417f
cgs          62.09174315p 4.27951939p 4.27951939p 3.24810150f
cgd          273.92047671f 31.41019830f 31.41019830f 106.52038570a
  
```



$$\left\{ \begin{array}{l} \frac{2 V_{out}}{r_{o,4}} + \frac{2 (V_{out} - V_s)}{r_{o,2}} - 2 \cdot g_{m,2} V_s + 2 \cdot g_{m,2} (V_{in} - V_s) = 0 \\ \left[ 2 \frac{(V_{out} - V_s)}{r_{o,2}} - 2 g_{m,2} V_s + 2 g_{m,2} (V_{in} - V_s) \right] \cdot r_{o,tail} = V_s \end{array} \right.$$

$$\frac{2 V_{out}}{r_{o,2}} \times r_{o,tail} + 2 g_{m,2} V_{in} \cdot r_{o,tail} = (1 + 2 g_{m,2} \cdot r_{o,tail} + 2 \frac{r_{o,tail}}{r_{o,2}} + 2 g_{m,2} \cdot r_{o,tail}) V_s$$

$$V_s = \frac{\frac{2 V_{out}}{r_{o,2}} \times r_{o,tail} + 2 g_{m,2} V_{in} \cdot r_{o,tail}}{1 + 2 g_{m,2} \cdot r_{o,tail} + 2 g_{m,2} \cdot r_{o,tail} + 2 \frac{r_{o,tail}}{r_{o,2}}}$$

$$\frac{2 V_{out}}{r_{o,4}} + \frac{2 V_{out}}{r_{o,2}} + 2 g_{m,2} V_{in} = \left( \frac{2}{r_{o,2}} + 2 g_{m,2} + 2 g_{m,2} \right) \frac{\frac{2 r_{o,tail}}{r_{o,2}} \times V_{out} + 2 g_{m,2} V_{in} \cdot r_{o,tail}}{1 + 2 g_{m,2} \cdot r_{o,tail} + 2 g_{m,2} \cdot r_{o,tail} + 2 \frac{r_{o,tail}}{r_{o,2}}}$$

$$A_{CM} = \frac{2 \cdot g_{m,2} (1 - \tau \cdot r_{o,tail})}{\left( \frac{2 \tau \cdot r_{o,tail}}{r_{o,2}} - \frac{2}{r_{o,4}} - \frac{2}{r_{o,2}} \right)}$$

gmb2 (S)	gm2 (S)	ro2 (Ω)	ro4 (Ω)	ro,tail (Ω)	τ
1.00487E-05	3.79376E-05	35861600.76	6253358.711	11533985.29	8.66221E-08

Acm calculated (V/V)	Acm simulation (V/V)	error
-0.213965719	-0.2140315	-0.03%

### Comment:

The common mode gain calculated identical to the simulation result. This also proves that from previous two homework of neglecting body effect is the reason that causes large error when calculating the gain.

## Discussions:

(j) Please discuss the precision requirement for the bias voltage  $V_{b2}$ .

### Comment:

From part (f) and (g), I observe that output voltage changes drastically when  $V_{b2}$  is altered through 0.7V, so that more precision value have to be considered to make the output common level to be 0.7V, this can be viewed as the 3 PMOS serves as a deterministic current source, and we are now altering the gate voltage of the NMOS below, if small changes deviates from the original feedback gate voltage will breakdown the configuration I built in part A. So  $V_{b2}$  given has to be at least 6<sup>th</sup> digit same as the original gate voltage ( $V_{b1}$ ) with feedback system. And the reason that it breakdown so drastically is that, since there is no support of CMFB, thus changes of  $V_{b2}$  has no pathway to balance and feedback the whole circuit stage to hold stability, so that's why we have to use extremely precise value of  $V_{b2}$ .

(k) For both Fig. 1 and Fig. 3, please compare and discuss the common mode voltage with  $\pm 5\%$   $V_{DD}$  variation.

### With Common Mode Feedback

$V_{DD} = 1.5V$

```
***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vb1     = 700.20231486m 0:vcm_in = 500.00000000m 0:vdd      = 1.50000000
+0:vin      = 0.          0:vin_left= 500.00000000m 0:vin_right= 500.00000000m
+0:vout_lef= 700.20231527m 0:vout_rig= 700.20231445m 0:vp       = 1.14085707
+0:vss      = 0.          0:vx      = 900.00000000m
```

\*\*\*\* mosfets

subckt	0:mtail	0:m1	0:m2	0:m3	element	0:m4
model	0:p_18.1	0:p_18.1	0:p_18.1	0:n_18.1	model	0:n_18.1
region	Saturation	Saturation	Saturation	Saturation	region	Saturation
id	-5.00375401u	-2.50187883u	-2.50187883u	2.50188240u	id	2.50188240u
ibs	4.6559651e-22	1.32033605f	1.32033605f	-1.6297974e-21	ibs	-1.6297974e-21
ibd	4.33791741f	2.94033758f	2.94033758f	-65.78657886a	ibd	-65.78657894a
vgs	-600.00000000m	-640.85707497m	-640.85707497m	700.20231486m	vgs	700.20231486m
vds	-359.14292503m	-440.65476052m	-440.65475970m	700.20231445m	vds	700.20231527m
vbs	0.	359.14292503m	359.14292503m	0.	vbs	0.
vth	-457.19064737m	-562.82792429m	-562.82792429m	356.68486015m	vth	356.68486014m
vdsat	-141.95818482m	-104.81385791m	-104.81385791m	294.97371197m	vdsat	294.97371197m
vod	-142.80935263m	-78.02915068m	-78.02915068m	343.51745472m	vod	343.51745472m
beta	490.38179660u	547.84928067u	547.84928067u	48.42213491u	beta	48.42213491u
gam_eff	557.08465667m	554.67912047m	554.67912047m	507.44640053m	gam_eff	507.44640053m
gm	56.21882891u	37.93751514u	37.93751514u	13.68655442u	gm	13.68655442u
gds	86.70041054n	27.90780250n	27.90780259n	159.88838139n	gds	159.88838129n
gmb	17.30681156u	10.04865690u	10.04865690u	2.54868331u	gmb	2.54868331u
cdtot	710.35523701f	95.42951902f	95.42951906f	518.45197988a	cdtot	518.45197977a
cgtot	68.25367796p	4.75370482p	4.75370482p	3.63188690f	cgtot	3.63188690f
cstot	76.14530686p	5.10513622p	5.10513622p	4.05278893f	cstot	4.05278893f
cbtot	24.30919161p	1.61298214p	1.61298214p	1.75627593f	cbtot	1.75627593f
cgs	62.09174329p	4.27952759p	4.27952759p	3.24809789f	cgs	3.24809789f
cgd	273.92067225f	31.41398601f	31.41398602f	106.51673223a	cgd	106.51673221a

\*\*\*\* resistors

subckt	0:r1	0:r2
element		
r value	585.00000000k	585.00000000k
v drop	409.60723702p	-409.60779213p
current	700.18331114a	-700.18426005a
power	2.8680015e-25	2.8680093e-25



VDD = 1.425V

'v = 1.425v'

\*\*\*\*\* operating point information tnom= 25.000 temp= 25.000 \*\*\*\*\*

\*\*\*\*\* operating point status is all simulation time is 0.

node	=voltage	node	=voltage	node	=voltage
------	----------	------	----------	------	----------

+0:vb1	= 556.15243924m	0:vcm_in	= 500.00000000m	0:vdd	= 1.42500000
+0:vin	= 0.	0:vin_left	= 500.00000000m	0:vin_right	= 500.00000000m
+0:vout_lef	= 556.15243884m	0:vout_rig	= 556.15243963m	0:vp	= 1.07888627
+0:vss	= 0.	0:vx	= 900.00000000m		

\*\*\*\* mosfets

subckt	element	0:mtail	0:m1	0:m2	0:m3	element	0:m4
model		0:p_18.1	0:p_18.1	0:p_18.1	0:n_18.1	model	0:n_18.1
region	Saturation	Saturation	Saturation	Saturation	region	Saturation	
id	-1.82262924u	-911.31599532n	-911.31599533n	911.32045411n	id	911.32045404n	
ibs	1.6959475e-22	1.27243600f	1.27243600f	-5.9366027e-22	ibs	-5.9366027e-22	
ibd	4.18054426f	3.19418938f	3.19418938f	-52.25326496a	ibd	-52.25326488a	
vgs	-525.00000000m	-578.88626616m	-578.88626616m	556.15243924m	vgs	556.15243924m	
vds	-346.11373384m	-522.73382653m	-522.73382731m	556.15243963m	vds	556.15243884m	
vbs	0.	346.11373384m	346.11373384m	0.	vbs	0.	
vth	-457.19063988m	-559.43557405m	-559.43557405m	357.43623459m	vth	357.43623460m	
vdsat	-93.44714137m	-72.66000244m	-72.66000244m	186.06314819m	vdsat	186.06314819m	
vod	-67.80936012m	-19.45069211m	-19.45069211m	198.71620464m	vod	198.71620464m	
beta	499.72742007u	555.71312851u	555.71312851u	48.14578314u	beta	48.14578314u	
gam eff	557.08465685m	554.75992096m	554.75992096m	507.44609138m	gam eff	507.44609138m	
gm	29.02083637u	17.64822903u	17.64822903u	8.12749575u	gm	8.12749575u	
gds	22.59827590n	7.50806895n	7.50806893n	82.34888259n	gds	82.34888263n	
gmb	8.88051223u	4.68461672u	4.68461672u	1.56686967u	gmb	1.56686967u	
cdtot	471.98958077f	89.83988047f	89.83988045f	531.19784848a	cdtot	531.19784859a	
cgtot	63.21850808p	3.76011166p	3.76011166p	3.63496386f	cgtot	3.63496386f	
cstot	68.27356066p	3.63432283p	3.63432283p	4.05148114f	cstot	4.05148114f	
cbtot	24.24208971p	1.58406993p	1.58406993p	1.79338553f	cbtot	1.79338553f	
cgs	55.41457797p	3.01842198p	3.01842198p	3.23038171f	cgs	3.23038171f	
cgd	162.77551800f	29.24346059f	29.24346059f	105.91268575a	cgd	105.91268576a	

\*\*\*\* resistors

subckt	element	0:r1	0:r2
r value	585.00000000k	585.00000000k	
v drop	-392.48293504p	392.48626571p	
current	-670.91100007a	670.91669352a	
power	2.6332112e-25	2.6332559e-25	

$V_{DD} = 1.575V$

'v = 1.575v'

```
***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vb1     = 855.77693919m 0:vcm_in  = 500.00000000m 0:vdd      = 1.57500000
+0:vin     = 0.             0:vin_left= 500.00000000m 0:vin_righ= 500.00000000m
+0:vout_lef= 855.77693814m 0:vout_rig= 855.77694023m 0:vp      = 1.19894155
+0:vss     = 0.             0:vx      = 900.00000000m
```

\*\*\*\* mosfets

subckt	0:mtail	0:m1	0:m2	0:m3	element	0:m4
model	0:p_18.1	0:p_18.1	0:p_18.1	0:n_18.1	model	0:n_18.1
region	Saturation	Saturation	Saturation	Saturation	region	Saturation
id	-10.23896330u	-5.11948404u	-5.11948404u	5.11948659u	id	5.11948659u
ibs	9.5272961e-22	1.38252372f	1.38252372f	-3.3349788e-21	ibs	-3.3349788e-21
ibd	4.54223155f	2.64411664f	2.64411665f	-80.40204322a	ibd	-80.40204302a
vgs	-675.00000000m	-698.94155110m	-698.94155110m	855.77693919m	vgs	855.77693919m
vds	-376.05844890m	-343.16461087m	-343.16461296m	855.77694023m	vds	855.77693814m
vbs	0.	376.05844890m	376.05844890m	0.	vbs	0.
vth	-457.19065969m	-567.20697116m	-567.20697116m	355.87472252m	vth	355.87472253m
vdsat	-196.73441167m	-141.48112456m	-141.48112456m	414.84606798m	vdsat	414.84606797m
vod	-217.80934031m	-131.73457995m	-131.73457995m	499.90221667m	vod	499.90221666m
beta	480.34684560u	538.99087997u	538.99087997u	48.43646733u	beta	48.43646733u
gam_eff	557.08465637m	554.57483429m	554.57483429m	507.44690930m	gam_eff	507.44690930m
gm	82.90025796u	60.10512148u	60.10512148u	19.52541640u	gm	19.52541640u
gds	268.05164429n	134.18550945n	134.18550671n	255.80202674n	gds	255.80202720n
gmb	25.80744769u	15.93117147u	15.93117147u	3.56956253u	gmb	3.56956253u
cdtot	1.11127506p	119.49646649f	119.49646585f	505.38438047a	cdtot	505.38438073a
cgtot	68.98794552p	5.00047122p	5.00047121p	3.62780713f	cgtot	3.62780713f
cstot	77.08841134p	5.43990241p	5.43990241p	4.05156287f	cstot	4.05156287f
cbtot	24.10511524p	1.60807746p	1.60807746p	1.71906216f	cbtot	1.71906216f
cgs	63.11534491p	4.58874302p	4.58874302p	3.26561907f	cgs	3.26561907f
cgd	460.66554261f	42.19734603f	42.19734574f	106.67711891a	cgd	106.67711895a

\*\*\*\* resistors

subckt	0:r1	0:r2
element	0:r1	0:r2
r value	585.00000000k	585.00000000k
v drop	-1.04503151n	1.04503184n
current	-1.78637864f	1.78637921f
power	1.8668220e-24	1.8668232e-24



## Without Common Mode Feedback

$V_{DD} = 1.5V$

```
***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vb2     = 700.20460000m 0:vcm_in  = 500.00000000m 0:vdd      = 1.50000000
+0:vin     = 0.           0:vin_left= 500.00000000m 0:vin_right= 500.00000000m
+0:vout_lef= 700.00680174m 0:vout_rig= 700.00680174m 0:vp       = 1.14085696
+0:vss     = 0.           0:vx      = 900.00000000m
```

\*\*\*\*\* mosfets

subckt	0:m1	0:m2	0:m3	0:m4
element	0:p_18.1	0:p_18.1	0:p_18.1	0:n_18.1
model	0:p_18.1	0:p_18.1	0:p_18.1	0:n_18.1
region	Saturation	Saturation	Saturation	Saturation
id	-5.00375402u	-2.50187884u	-2.50187884u	2.50188242u
ibs	4.6559651e-22	1.32033647f	1.32033647f	-1.6297974e-21
ibd	4.33791878f	2.94105636f	2.94105636f	-65.76820927a
vgs	-600.00000000m	-640.85696155m	-640.85696155m	700.20460000m
vds	-359.14303845m	-440.85015981m	-440.85015981m	700.00680174m
vbs	0.	359.14303845m	359.14303845m	0.
vth	-457.19064737m	-562.82795375m	-562.82795375m	356.68588325m
vdsat	-141.95818482m	-104.81376930m	-104.81376930m	294.97467160m
vod	-142.80935263m	-78.02900780m	-78.02900780m	343.51871675m
beta	490.38179660u	547.84928754u	547.84928754u	48.42213593u
gam eff	557.08465667m	554.67911977m	554.67911977m	507.44640053m
gm	56.21882909u	37.93755188u	37.93755188u	13.68650233u
gds	86.70030129n	27.88497944n	27.88497944n	159.91406317n
gmb	17.30681161u	10.04866619u	10.04866619u	2.54868515u
cdtot	710.35480689f	95.41860549f	95.41860549f	518.47879693a
cgtot	68.25367770p	4.75369525p	4.75369525p	3.63189093f
cstot	76.14530696p	5.10513915p	5.10513915p	4.05279021f
cbtot	24.30919157p	1.61297823p	1.61297823p	1.75629417f
cgs	62.09174315p	4.27951939p	4.27951939p	3.24810150f
cgd	273.92047671f	31.41019830f	31.41019830f	106.52038570a

VDD = 1.425V

```
'v = 1.425v'

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0. *****
node      =voltage      node      =voltage      node      =voltage
+0:vb2     = 700.20460000m 0:vcm_in  = 500.00000000m 0:vdd      = 1.42500000
+0:vin      = 0.          0:vin_left= 500.00000000m 0:vin_righ= 500.00000000m
+0:vout_lef= 64.80083982m 0:vout_rig= 64.80083982m 0:vp       = 1.07876159
+0:vss      = 0.          0:vx      = 900.00000000m
```

```
**** mosfets

subckt
element      0:mtail      0:m1      0:m2      0:m3      element      0:m4
model        0:p_18.1      0:p_18.1      0:p_18.1      0:n_18.1      model        0:n_18.1
region      Saturation      Saturation      Saturation      Linear      region      Linear
id          -1.82263206u -911.31543792n -911.31543792n 911.32481068n id          911.32481068n
ibs         1.6959501e-22 1.27289437f 1.27289437f -5.9366278e-22 ibs         -5.9366278e-22
ibd         4.18205021f 5.00057082f 5.00057082f -6.08783404a ibd         -6.08783404a
vgs         -525.00000000m -578.76158578m -578.76158578m 700.20460000m vgs         700.20460000m
vds         -346.23841422m -1.01396075 -1.01396075 64.80083982m vds         64.80083982m
vbs         0.          346.23841422m 346.23841422m 0.          vbs         0.
vth         -457.19063988m -559.46811730m -559.46811730m 360.00741409m vth         360.00741409m
vdsat       -93.44714137m -72.58939681m -72.58939681m 292.45774937m vdsat       292.45774937m
vod         -67.80936012m -19.29346848m -19.29346848m 340.19718591m vod         340.19718591m
beta        499.72742007u 555.71543179u 555.71543179u 48.41765219u beta        48.41765219u
gam_eff     557.08465685m 554.75914578m 554.75914578m 507.44609138m gam_eff     507.44609138m
gm          29.02089556u 17.65484019u 17.65484019u 3.08348449u gm          3.08348449u
gds         22.57146488n 4.77377778n 4.77377778n 12.24280206u gds         12.24280206u
gmb         8.88053001u 4.68638527u 4.68638527u 629.04519486n gmb         629.04519486n
cdtot       471.82075632f 83.19006383f 83.19006383f 4.43953835f cdtot       4.43953835f
cgtot       63.21836613p 3.75375288p 3.75375288p 4.44571096f cgtot       4.44571096f
cstot       68.27364068p 3.62989195p 3.62989195p 4.56175294f cstot       4.56175294f
cbtot       24.24205967p 1.57793452p 1.57793452p 1.96196400f cbtot       1.96196400f
cgs         55.41446772p 3.01088259p 3.01088259p 2.60050881f cgs         2.60050881f
cgd         162.70177602f 28.77244539f 28.77244539f 1.70646495f cgd         1.70646495f
```

VDD = 1.575V

```
'v = 1.575v'


***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage
+0:vb2     = 700.20460000m 0:vcm_in  = 500.00000000m 0:vdd      = 1.57500000
+0:vin     = 0.           0:vin_left= 500.00000000m 0:vin_righ= 500.00000000m
+0:vout_lef= 1.50174499  0:vout_rig= 1.50174499  0:vp       = 1.51170288
+0:vss     = 0.           0:vx      = 900.00000000m
```

\*\*\*\* mosfets

subckt	element	0:mtail	0:m1	0:m2	0:m3	element	0:m4
model	0:p_18.1	0:p_18.1	0:p_18.1	0:n_18.1	model	0:n_18.1	
region	Linear	Linear	Linear	Saturation	region	Saturation	
id	-5.23145945u	-2.61573031u	-2.61573031u	2.61572765u	id	2.61572765u	
ibs	4.8678420e-22	232.70273007a	232.70273007a	-1.7039599e-21	ibs	-1.7039599e-21	
ibd	764.53550457a	269.31095093a	269.31095096a	-141.09624836a	ibd	-141.09624836a	
vgs	-675.00000000m	-1.01170288	-1.01170288	700.20460000m	vgs	700.20460000m	
vds	-63.29711628m	-9.95789329m	-9.95789330m	1.50174499	vds	1.50174499	
vbs	0.	63.29711628m	63.29711628m	0.	vbs	0.	
vth	-457.19064790m	-481.04130492m	-481.04130492m	352.49062602m	vth	352.49062602m	
vdsat	-196.73444835m	-446.92435213m	-446.92435213m	298.16449454m	vdsat	298.16449454m	
vod	-217.80935210m	-530.66157880m	-530.66157880m	347.71397398m	vod	347.71397398m	
beta	480.34684261u	513.33494436u	513.33494436u	48.42761160u	beta	48.42761160u	
gam eff	557.08465665m	556.63015335m	556.63015335m	507.44642266m	gam eff	507.44642266m	
gm	27.56478229u	4.40079708u	4.40079708u	14.09495510u	gm	14.09495510u	
gds	66.15000982u	259.66010962u	259.66010961u	135.89046180n	gds	135.89046180n	
gmb	9.23090504u	1.79293138u	1.79293138u	2.57333193u	gmb	2.57333193u	
cdtot	61.87890982p	6.75928666p	6.75928666p	455.70146151a	cdtot	455.70146151a	
cgtot	85.99248186p	6.56195221p	6.56195221p	3.62782060f	cgtot	3.62782060f	
cstot	81.54616610p	6.53118344p	6.53118344p	4.04502710f	cstot	4.04502710f	
cbtot	26.63839300p	2.04888273p	2.04888273p	1.70042839f	cbtot	1.70042839f	
cgs	56.57680209p	3.51138917p	3.51138917p	3.23735181f	cgs	3.23735181f	
cgd	28.65885438p	3.06670869p	3.06670869p	103.41521844a	cgd	103.41521844a	




## Discussion:

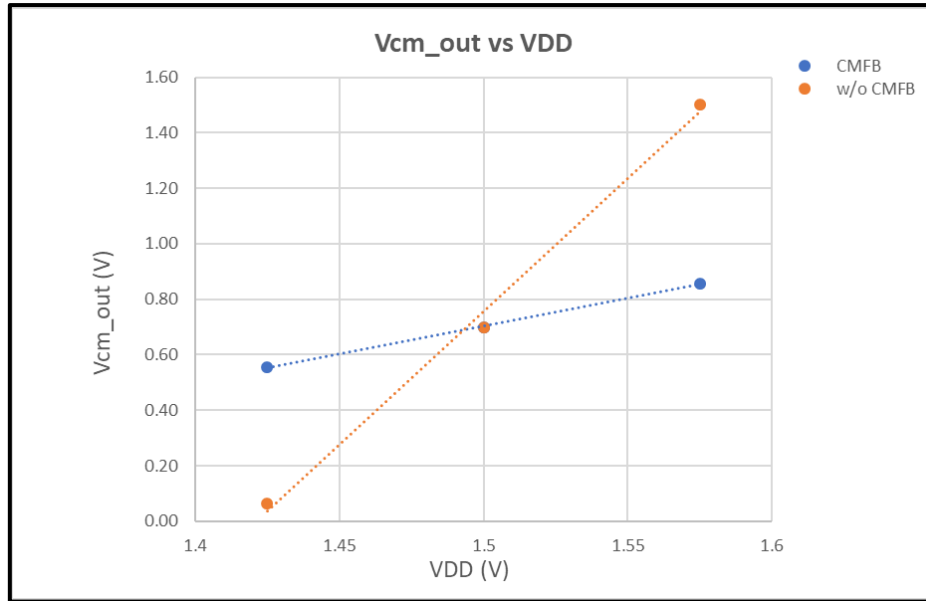

	VDD (V)	1.425	1.5	1.575
CMFB	Vcm_out (V)	0.55615243884	0.70020231445	0.85577694023
w/o CMFB	Vcm_out (V)	0.06480083982	0.70000680174	1.50174499000

Comment:

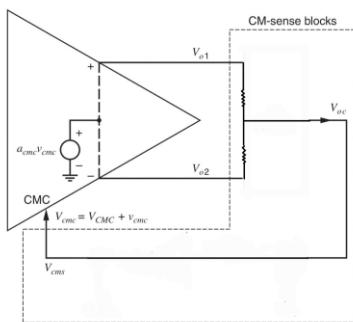For my design with CMFB, the bias voltage and size are set that it is less prone to leave saturation region with  $V_{DD}$  variation. By observing the output level when CMFB is in the system and without. I see that the output common level has relatively small variation. where we see that without the CMFB, either the output common level either falls to  $V_{SS}$  or raises to  $V_{DD}$ .



$V_{CMC}$  = projected common mode output voltage.

$A_{CMC}$  = loop gain.

With the support of the left figure CMFB loop, the system senses the variation and can compare with a projected  $V_{CMC}$  value, where if compare value exceeds 0, then with the negative loop gain, it then has negative feedback so that it suppresses the difference. In contrast, if the sensed value is below 0, then the feedback will raise the level up. Thus, the feedback system maintains a stable system and is less prone to change with changes of other voltage source.

But with no support of the feedback system, once we deviate from the original balanced state, then there is no detection and negative feedback to maintain the output level, the output voltage then will lean to either the highest voltage or the lowest voltage, with NMOS pair remains working and tail and PMOS pair off or vice versa.

(1) Fill up Tab. I.

Working Item	Specification	Simulation Result			Calculation
Supply VDD	1.5V±5%	1.575V	1.5V	1.425V	
Tail Current	5μA		5.00375401 μA		
With Common Mode Feedback					
Output Common mode	0.7V	0.85577693814 V	0.70020231527 V	0.55615243884V	
Differential voltage gain	20		-19.9967 V/V		
Common mode gain	<1		-2.4724mV		-2.471602 mV
Without Common Mode Feedback					
Output Common mode	0.7V	1.50174499 V	0.70000680174 V	0.06480083982 V	
Differential voltage gain	-		-202.0203 V		
Common mode gain	<1		-214.0330 mV		-214.000219 mV
Vb2	V		0.7002045V		
Device Size					
Mtail (W/L ×m)	-		(45μm/40μm × 6)		
M1, M2 (W/L ×m)	-		(20μm/10μm × 4)		
M3, M4 (W/L ×m)	-		(0.3μm/1.81μm × 1)		
R1, R2	KΩ		585 KΩ		
Vx	V		0.9 V		