

# EE3235 Analog Integrated Circuit Analysis and Design I

## Homework 1

### Process Analysis

Due date: 2021.10.13 (Wed.) 13:20 (upload to eeclass system)

In this homework, you are to run HSPICE and evaluate the device performance with threshold voltage  $V_{th}$ , transconductance  $g_m$ , output conductance  $g_{ds}$ , saturation drain voltage  $V_{dsat}$ , intrinsic gain  $g_m r_O$ , power efficiency  $g_m/I_D$ , speed  $g_m/C_g$ , drain current  $I_D$ , and body effect as the benchmarks.

Suppose  $V_{DD}=1.8V$ , temperature=25°C, TT corner in this homework.


Please note that:

1. **No delay allowed.**
2. Please hand in your report using eeclass system.
3. Please generate your report with **pdf** format, name your report as [HWX\\_studentID\\_name.pdf](#).
4. Please hand in the spice code file (.sp) for each work. Do not include output file.
5. Please print waveform with [white background](#), and make sure the X, and Y labels are clear.
6. Please do not zip your report.

## Part 1. Analyze with Diode Connected Structure

### (1) Threshold Voltage $V_{th}$

Threshold voltage (V)

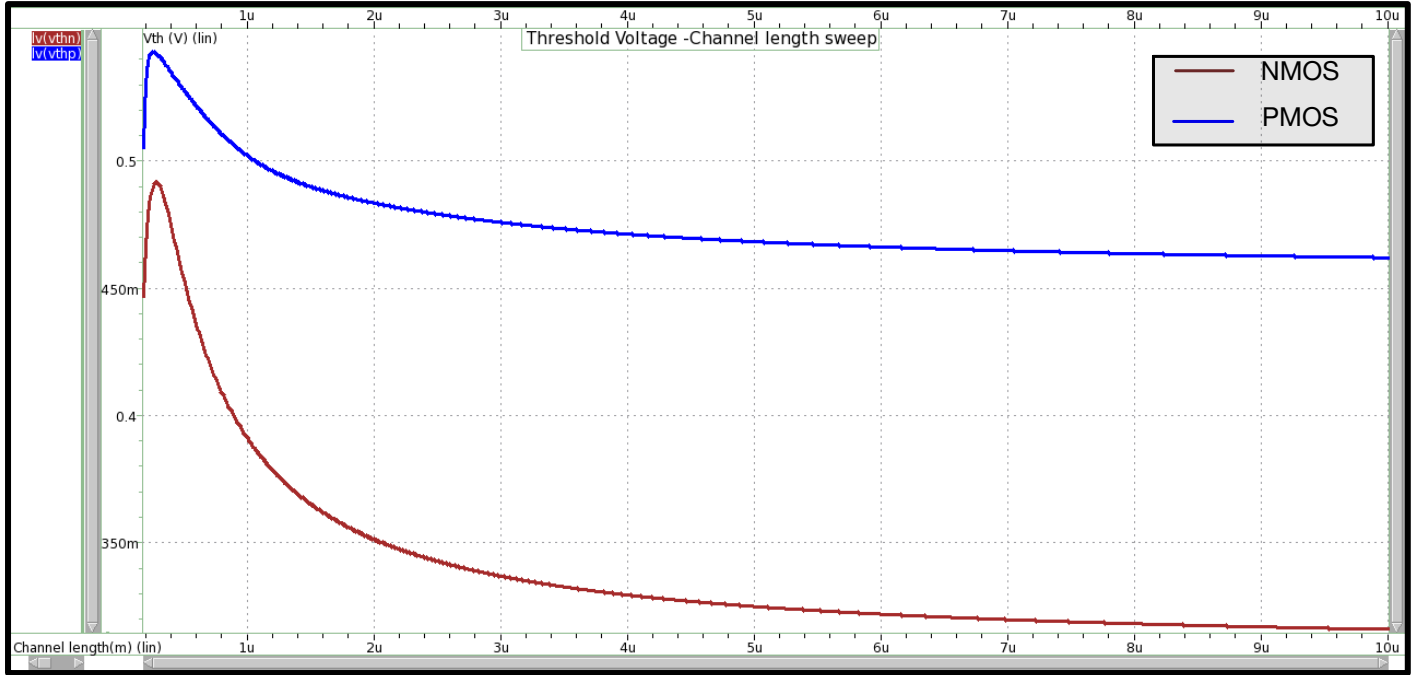

Channel length (m)

#### Comment:

With the sweeping channel length increasing in the (180nm – 300nm) region, the threshold voltage rises as the channel length increases for both diode-connected NMOS and PMOS with the W/L ratio stays at 2, but after that they hit a peak (491 mV for the NMOS and 543 mV for the PMOS) and began to drop as the channel length increases, even goes lower than the starting sweep length (0.18  $\mu\text{m}$ ) for both cases.

From the formula of the  $V_{TH}$  roll-off of short channel effect:

$$\Delta V_{TH} = \frac{-qN_A W_T}{C_{ox}} \frac{L-L'}{2L} \quad \text{where } L \text{ stands for upper channel length and } L' \text{ stands for lower channel length,}$$


this is more significant for shorter channel length since the relative difference between two lengths is larger, causing the threshold voltage rises when the channel length increases for short channel.

Also, when channel length is small with same  $V_{DS}$  and  $V_G$ , the inversion charge density is more concentrated at the channel so that less threshold voltage needs to be overcome to make the MOS be on, so in the region of 180nm – 300nm this can be observed.

But after that the threshold voltage decreases for increasing channel length, this is because there exists reverse short channel effect.

## (2) Transconductance $g_m$

### Transconductance (S)

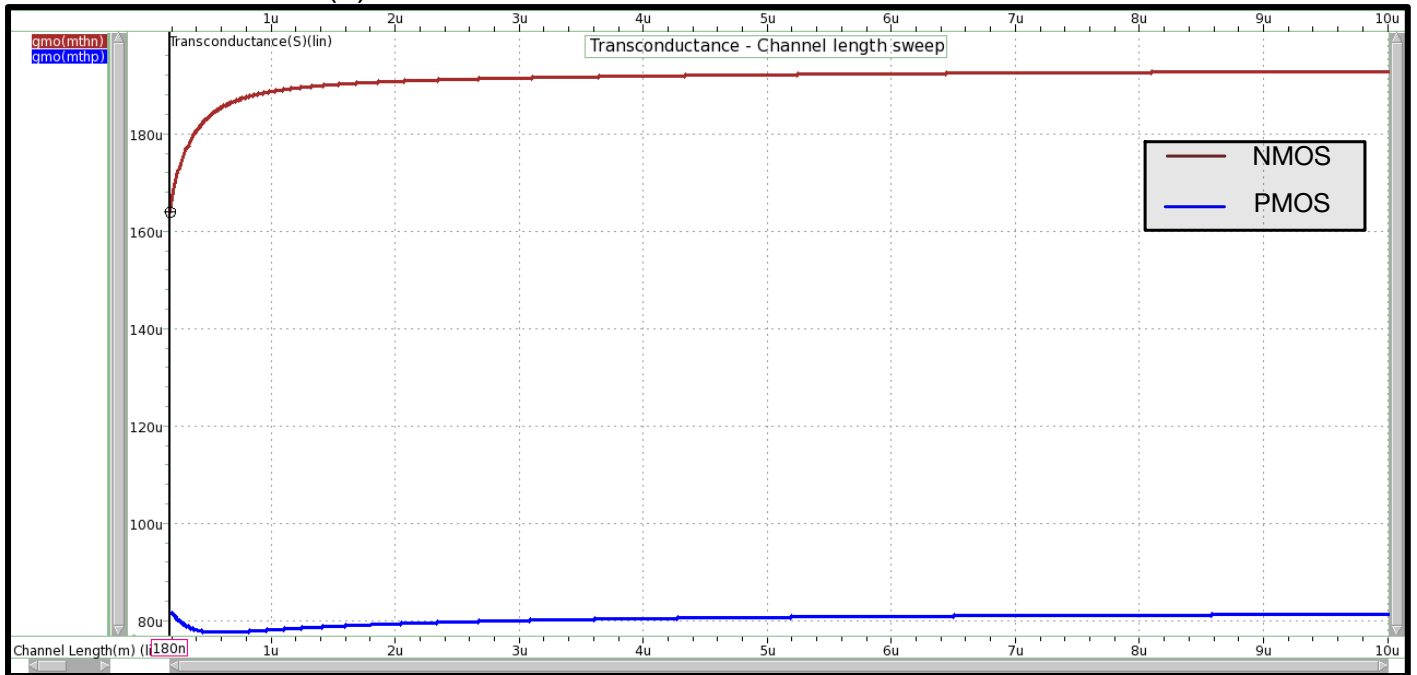

Channel length (m)

#### Comment:

From known formula:

$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$

$$g_m = \mu_{n(p)} C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)$$

The transconductance of the diode-connected NMOS has increased with the channel length as it increases and the slope has reduced and after 2um. Indicating that the drain current change rate with respect to  $V_{GS}$  will be less affected by channel length after it reaches 2um.


The transconductance of the diode-connected PMOS has a slight drop in the (180nm – 400nm) region and then start rising with a relatively small slope. The whole curve indicates that the transconductance of PMOS diode connected is less sensitive with respect to the channel length change comparing to the diode connected NMOS in the (180nm – 400nm) region.

Also, since the transconductance of the NMOS is larger than the PMOS in the graph, so it indicates that the change of drain current with respect to  $V_{GS}$  change is larger for NMOS than the PMOS throughout the sweeping length.

The transconductance supposedly should grow linearly with channel length increasing, because the previous simulation shows that  $|V_{TH}|$  decreases with channel lengths increases. After probing  $|V_{GS}|$ , I found out that  $|V_{GS}|$  has similar pattern parallel with  $|V_{TH}|$ ,  $|V_{GS}|$  first increases for increasing channel length for small channel, but after hitting a value,  $|V_{GS}|$  then drops. So that with  $|V_{GS}|$  and  $|V_{TH}|$  decreases together causing the transconductance doesn't grow linearly.

### (3) Output conductance $g_{ds}$

#### Output conductance (S)

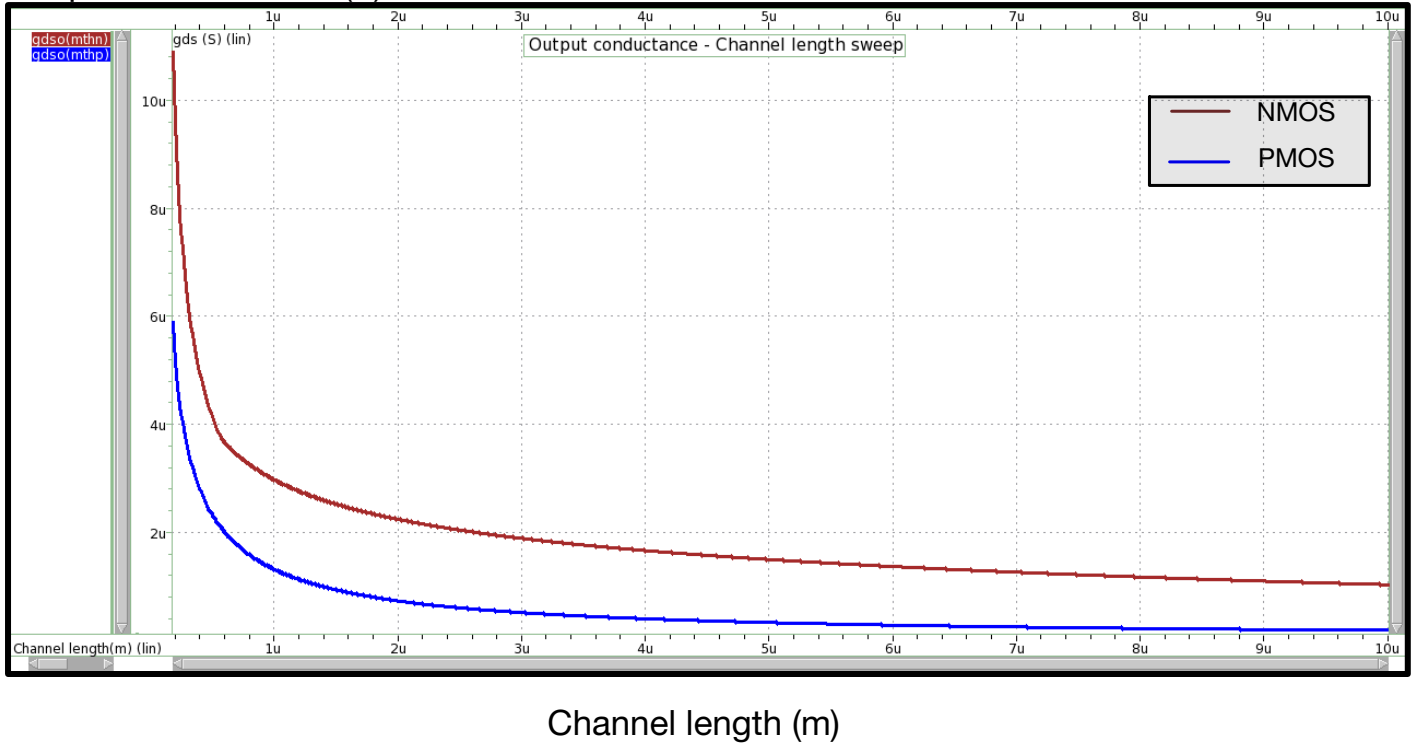

**Comment:**

From known formula:

$$r_o^{-1} = \frac{\partial I_D}{\partial V_{DS}} \quad \text{and} \quad r_o^{-1} = \frac{1}{2} \mu_n(p) C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 \times \lambda$$

The Output Conductance drops as channel lengths increases, and the drop in the (180nm – 1um) region is immense, and after that the slope decreases for both diode-connected PMOS and NMOS. Another thing to notice is that the output conductance of the NMOS remains higher than the PMOS throughout the sweep. The graph indicates that the drain current change with respect to the  $V_{DS}$  change is larger for the NMOS than the PMOS.

The output conductance is related to the channel length modulation effect, the effect is negligible for long channel length so that the output conductance decreases.

The decrease rate of the output conductance of the NMOS in the (180nm – 1um) region is

$$\frac{-9.67S \text{ (output conductance)}}{1\mu m \text{ (channel length)}}$$


The decrease rate of the output conductance of the PMOS in the (180nm – 1um) region is

$$\frac{-5.56S \text{ (output conductance)}}{1\mu m \text{ (channel length)}}$$

This also indicates that the change is more sensitive for NMOS with respect to the change of channel length comparing to PMOS in the (180nm – 1um) region.

#### (4) Saturation drain voltage $V_{dsat}$

##### Saturation drain voltage (V)

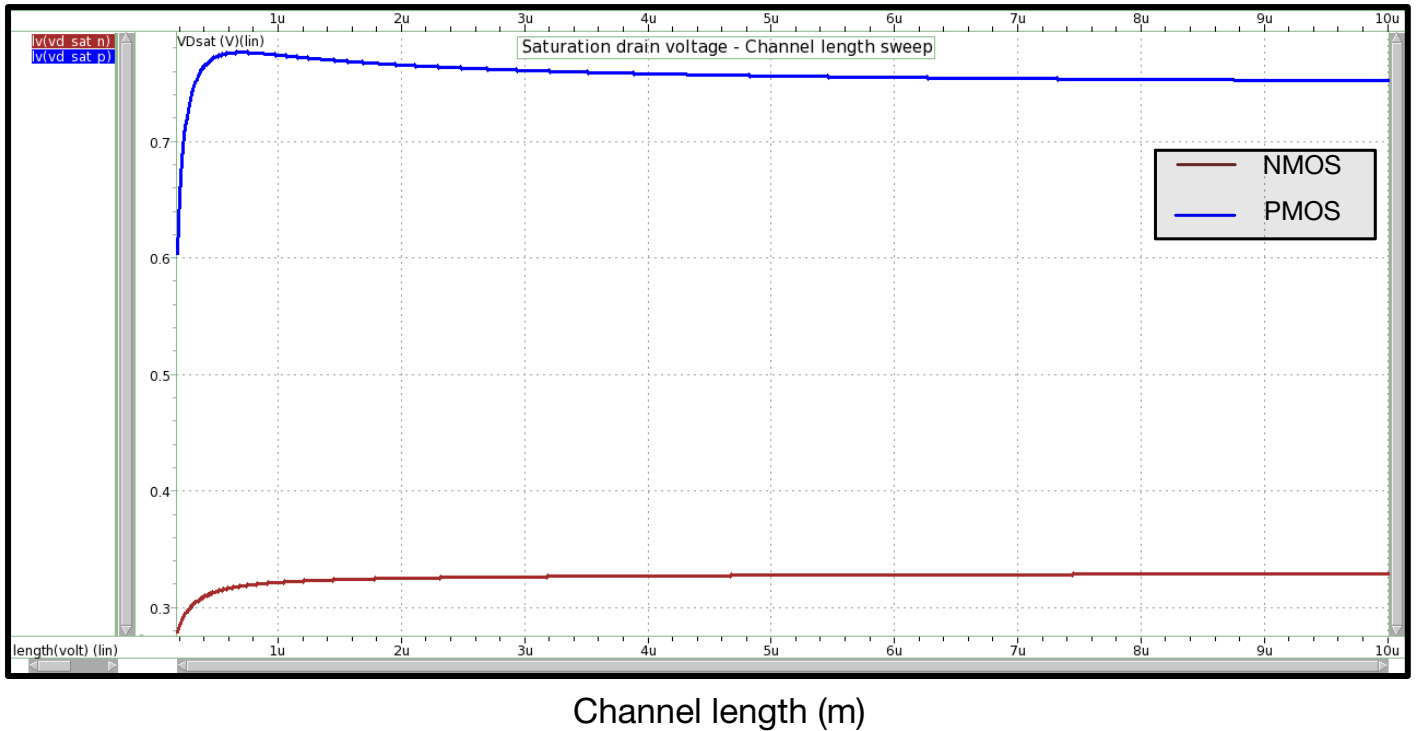

##### Comment:

The saturation voltage rises at first in the 180nm - 600nm of sweeping channel length for the diode-connected PMOS, and after that it has a slight drop and stay stable after the channel length is increased to 5 $\mu$ m.


In contrast to the diode-connected PMOS, the counterpart NMOS has no drop throughout the sweep and quickly converge to a near-constant saturation drain voltage after the length is increased to 2 $\mu$ m.

Both cases display that the saturation drain voltage becomes more channel length independent after the MOS' channel length has reached a certain length. But behaves different for smaller channel length.

Since  $V_{D,sat} = V_{GS} - V_{TH}$ , so the saturation drain voltage should rise if threshold voltage drops, the graph makes sense for the NMOS but acts differently for the PMOS, the saturation drain voltage acts parallel with the threshold voltage. So, there might be second order effect on saturation drain voltage if the channel length is increased that makes the  $V_{GS}$  changes parallel with threshold voltage also.

## (5) Intrinsic gain $g_m r_o$

Intrinsic gain (V/V)

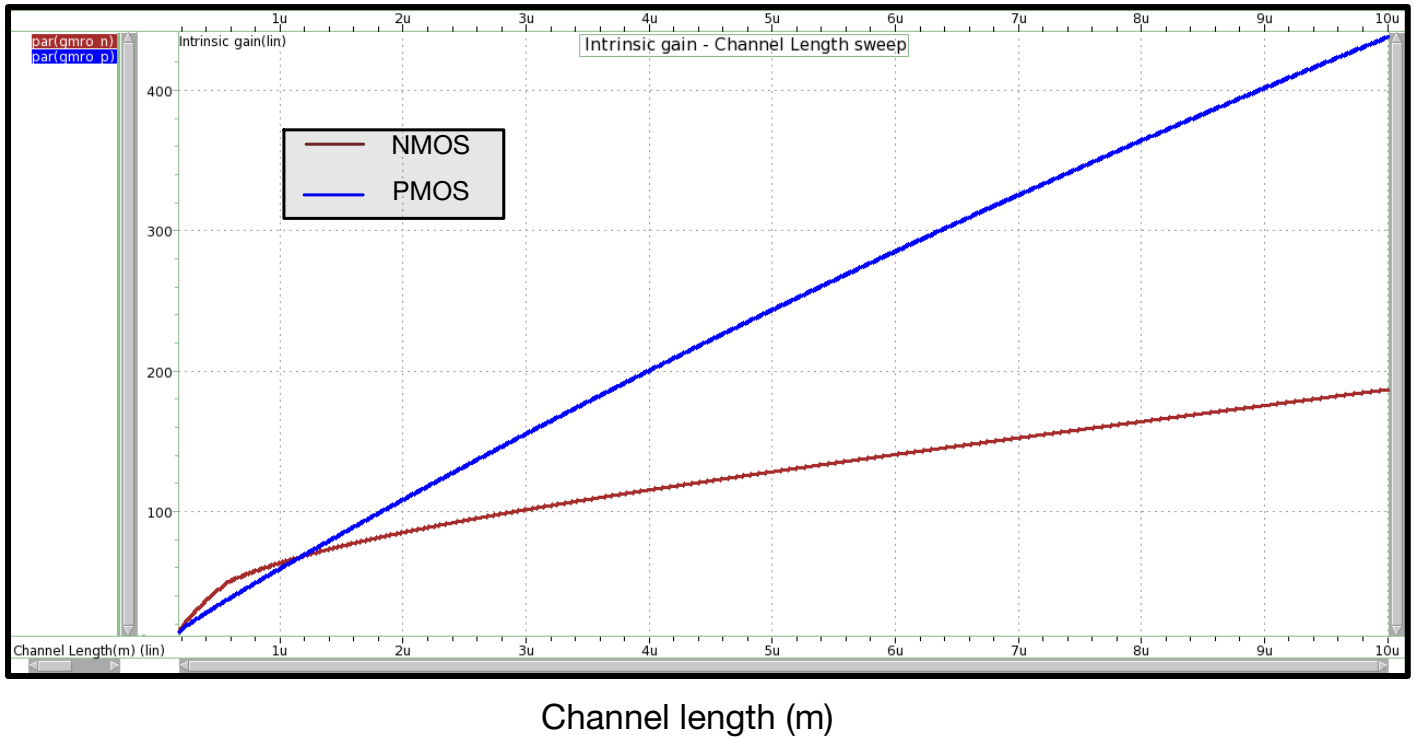

### Comment:

The intrinsic gain of the diode connected NMOS is higher than the diode-connected PMOS before the cross-point (channel length of 1.18  $\mu\text{m}$  where the intrinsic gain is 68.1 for both MOS). After that, the intrinsic gain of the diode-connected PMOS become larger than the diode connected NMOS, since it has a larger growing slope from the sweeping origin (0.18  $\mu\text{m}$ ).

The increase rate of the intrinsic gain of PMOS is  $\frac{41.92 \text{ (intrinsic gain)}}{1 \mu\text{m (channel length)}}$  after the cross-point


The increase rate of the intrinsic gain of NMOS is  $\frac{13.5 \text{ (intrinsic gain)}}{1 \mu\text{m (channel length)}}$  after the cross-point

It can be observed that there is a trade off between size of MOS and the intrinsic gain performance, with higher intrinsic gain acquired, more budget needs to be spent on the size.

And from the graph the intrinsic gain has a steady growing curve while the transconductance has a flat curve, so this means that the output resistance is growing with channel length increasing.

## (6) Power Efficiency $g_m/I_D$

Power efficiency (1/V)

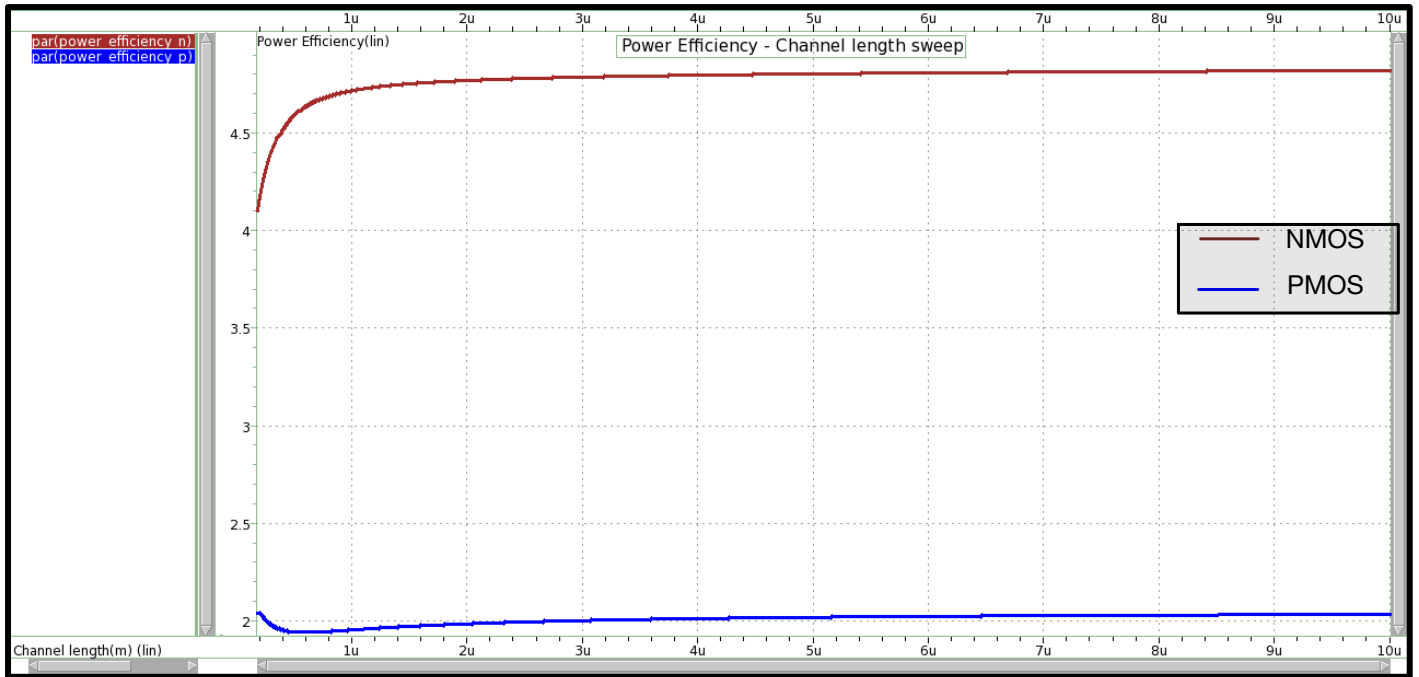

Channel length (m)


### Comment:

The power efficiency behaves parallel with the transconductance since Power efficiency is transconductance divided by Drain current, and since in saturation region the drain current of both MOS can be written as  $|I_D| = \frac{1}{2} \mu_{n(p)} C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 (1 + \lambda |V_{DS}|)$ , and everything remains constant throughout the sweep so that the power efficiency can show a parallel relationship with the transconductance.

Also, the intrinsic gain is  $g_m r_o$ , and is related to  $g_m$ , so we can see the power efficiency as a factor of how much gain we can attain for giving certain amount of drain current.

## (7) Speed $g_m/C_g$

Speed (rad/s)

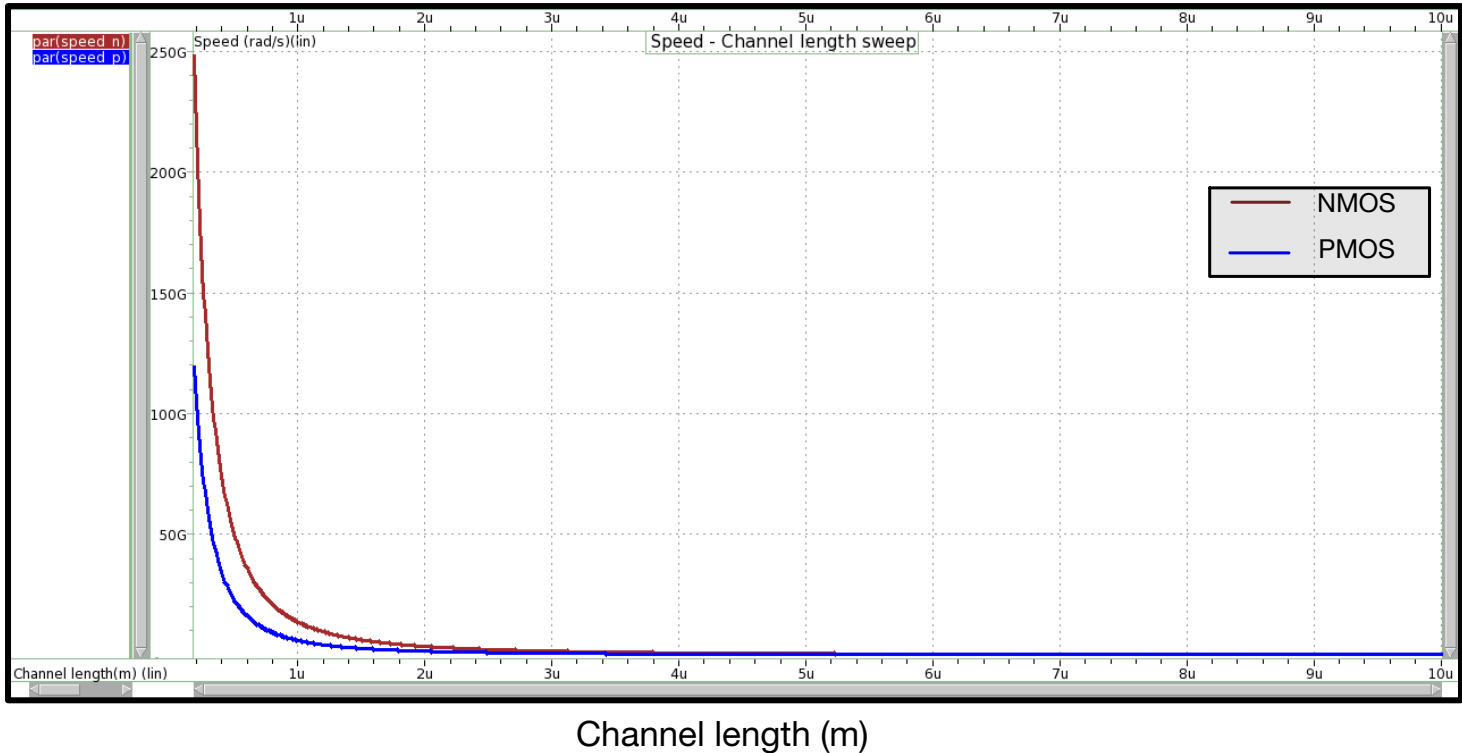

### Comment:

The speed of the diode-connected NMOS is higher than the diode-connected PMOS in the (180nm – 1μm) region, but after that the both speeds drops with a small slope as channel length increases. I also observe that the speed drops drastically in the previous mentioned region (180nm – 1μm) with a steep slope.

From known formula

$$C_{GS} = \frac{2}{3} C_{ox} \times W \times L_{eff} + WL_{ov} \times C_{ox}$$

$$C_{GD} = WL_{ov} \times C_{ox}$$

So that the gate capacitance increases as W and L increases, so the speed drops as the sweeping channel length increases, since the W/L is fixed at 2, so the total gate capacitance increases leading to the speed decreasing.

Since my past lecture hasn't covered about  $C_{GB}$  and further W/L modulation effect, but I think the reason that the speed is not decreasing that fast after 1μm might be because the gate capacitance of MOS will become W and L independent once the channel length approaches a value (in this simulation is 1μm).

(NMOS speed decrease rate:  $\frac{-285.7G}{1\mu m}$  PMOS speed decrease rate :  $\frac{-137.8G}{1\mu m}$ ) both for in the region


(180nm – 1μm)



## Part 2. Drain Current $I_D$

### (1) $I_D$ vs $V_G$ (NMOS)


Drain current (A)

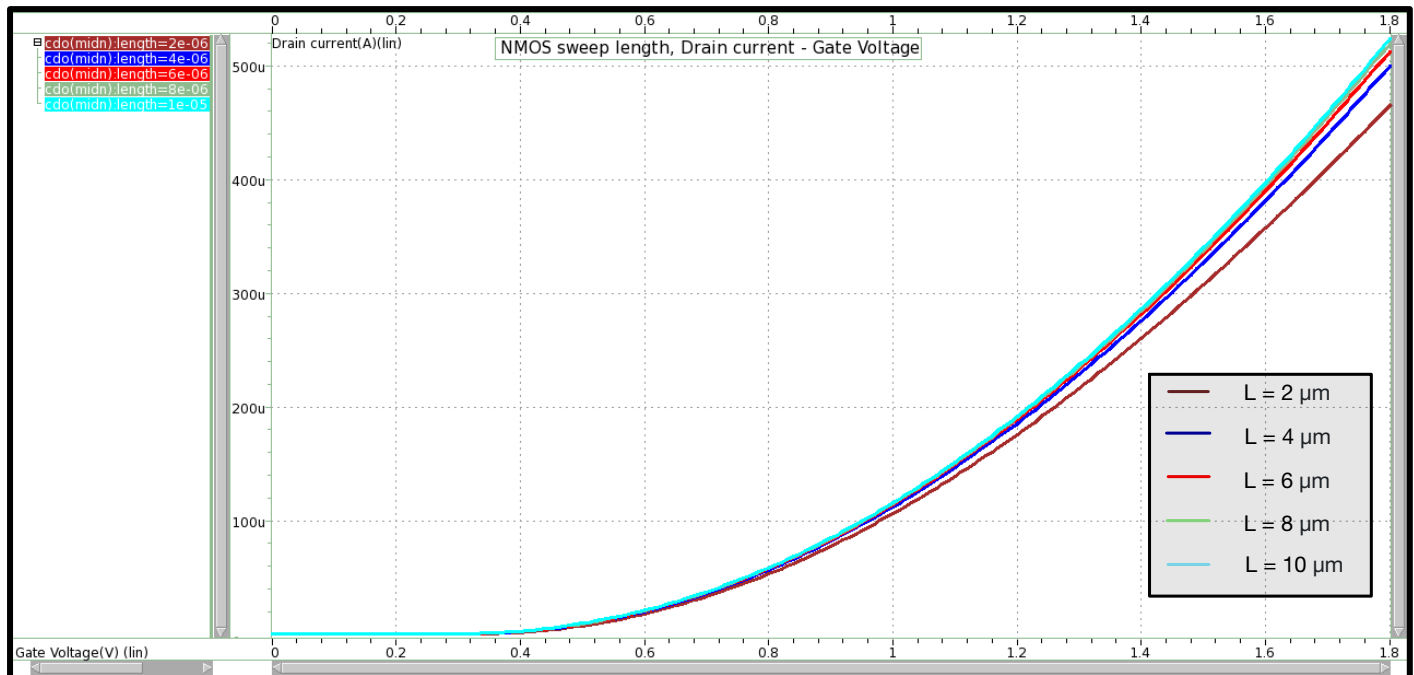

Gate voltage (V)

### (2) $I_D$ vs $V_G$ (PMOS)

Drain current (A)

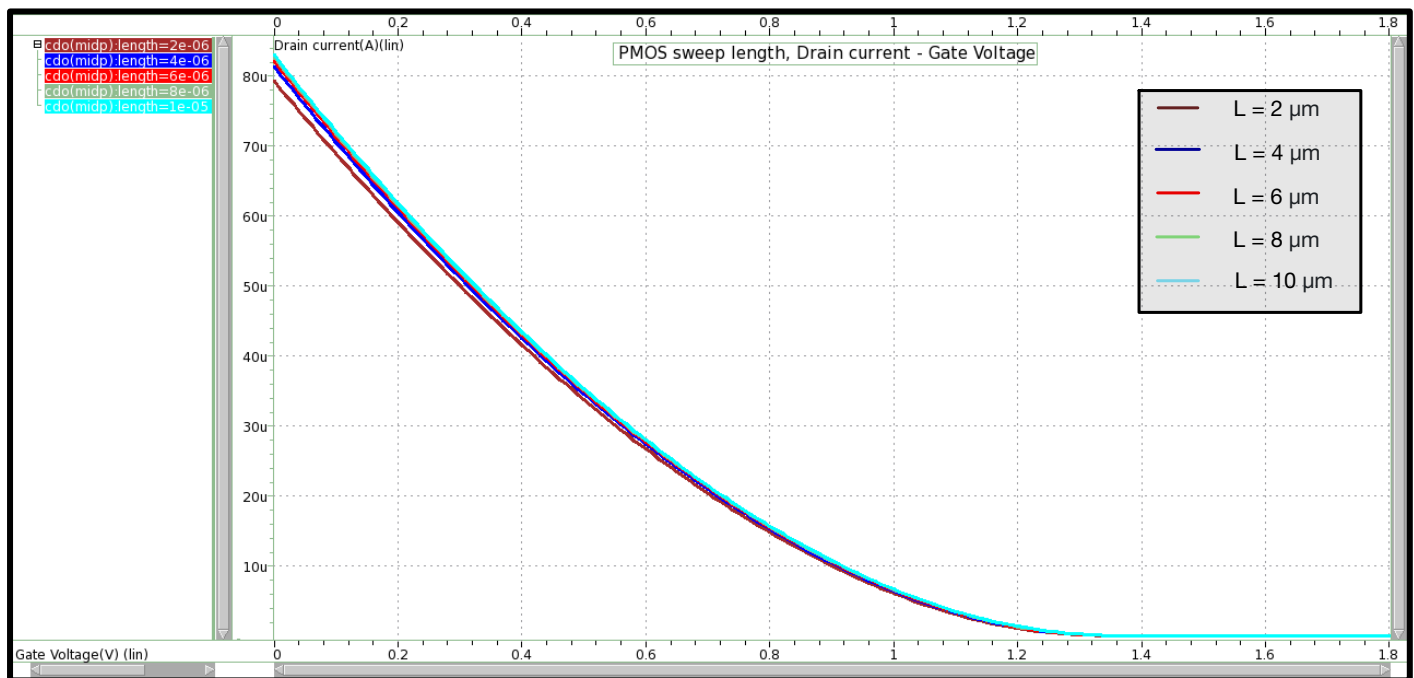

Gate voltage (V)

**Comment:**

In both NMOS and PMOS cases, I observed that the drain current doesn't vary much with its channel length, and both cases show that with the W/L ratio fixed at 2, the drain current is slightly increased as the channel length increases, this shows that increasing channel width has more impact on increasing the drain current than increasing the channel length on decreasing the drain current when the W/L ratio is fixed.

From known formula and concepts:

1.  $|V_{GS}|$  has to exceed some specific value of  $|V_{TH}|$  so that the MOS are on.
2. Drain current of MOS in saturation regions is  $|I_D| = \frac{1}{2} \mu_{n(p)} C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 (1 + \lambda |V_{DS}|)$ .


For the NMOS case, increasing the gate voltage until about 0.4V, then the NMOS started to provide drain current, indicating that the gate voltage has exceeded the built-in threshold voltage, and the NMOS are in saturation region since  $V_{GS}$  is always smaller than  $V_{DS}$  in the sweeping region (Where  $V_D$  is at 1.8V and  $V_G$  is sweeping from 0V to 1.8V) so that the drain currents grow in order of 2 after the gate voltage exceeds the threshold voltage.

For the PMOS case, increasing the gate voltage decreases the drain current, since the voltage difference between gate and voltage is getting smaller and is approaching to its threshold voltage (negative value). And when gate voltage is at around 1.2V, the PMOS is off. During the gate voltage region where PMOS is on, it is in saturation region since the drain is negative enough (using the source as reference point) contrast to  $(V_G - V_{TH})$ , and it shows that as gate voltage increases, the drain current falls as order of 2.

## Part 3. Body Effect

### (1) $V_{GS}$ vs $V_B$ (NMOS)


Gate-Source voltage (V)

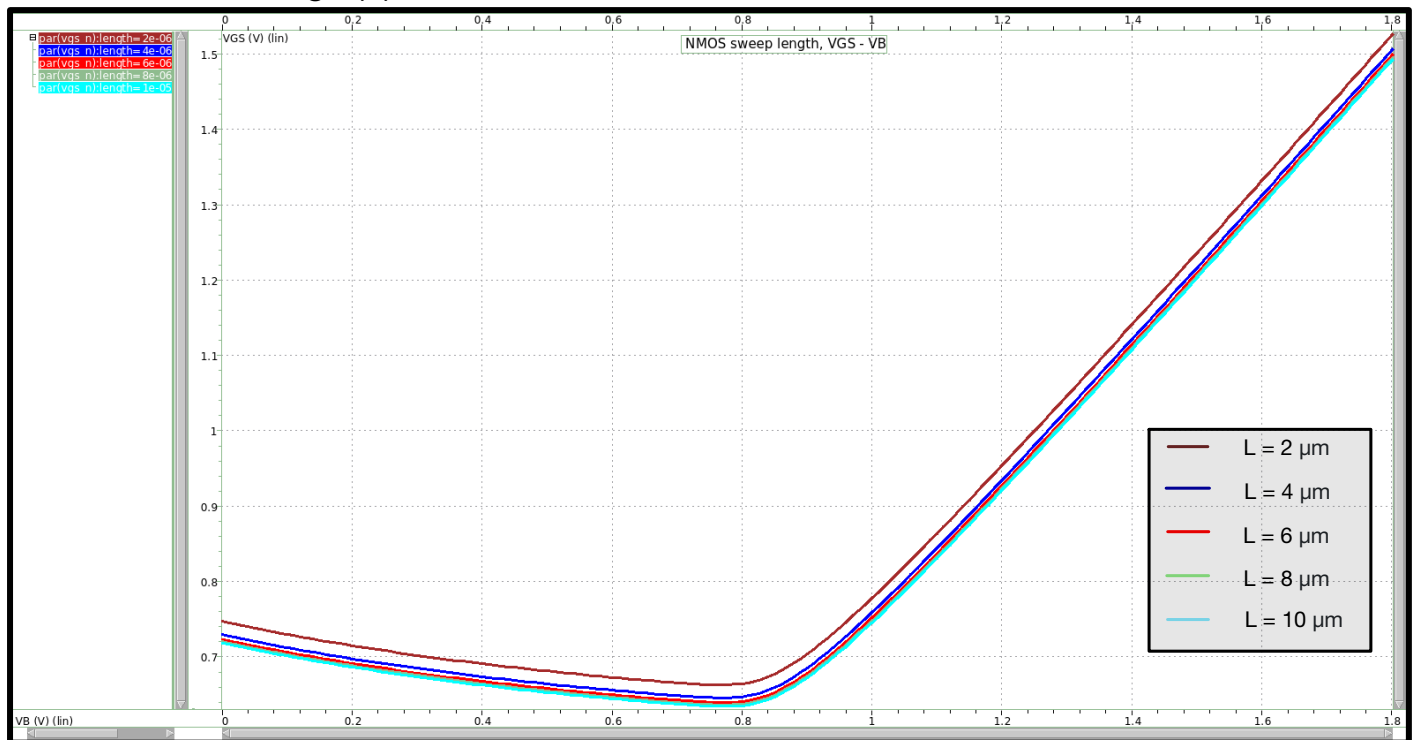

Bulk Voltage (V)

### (2) $V_{GS}$ vs $V_B$ (PMOS)

Gate-Source voltage (V)

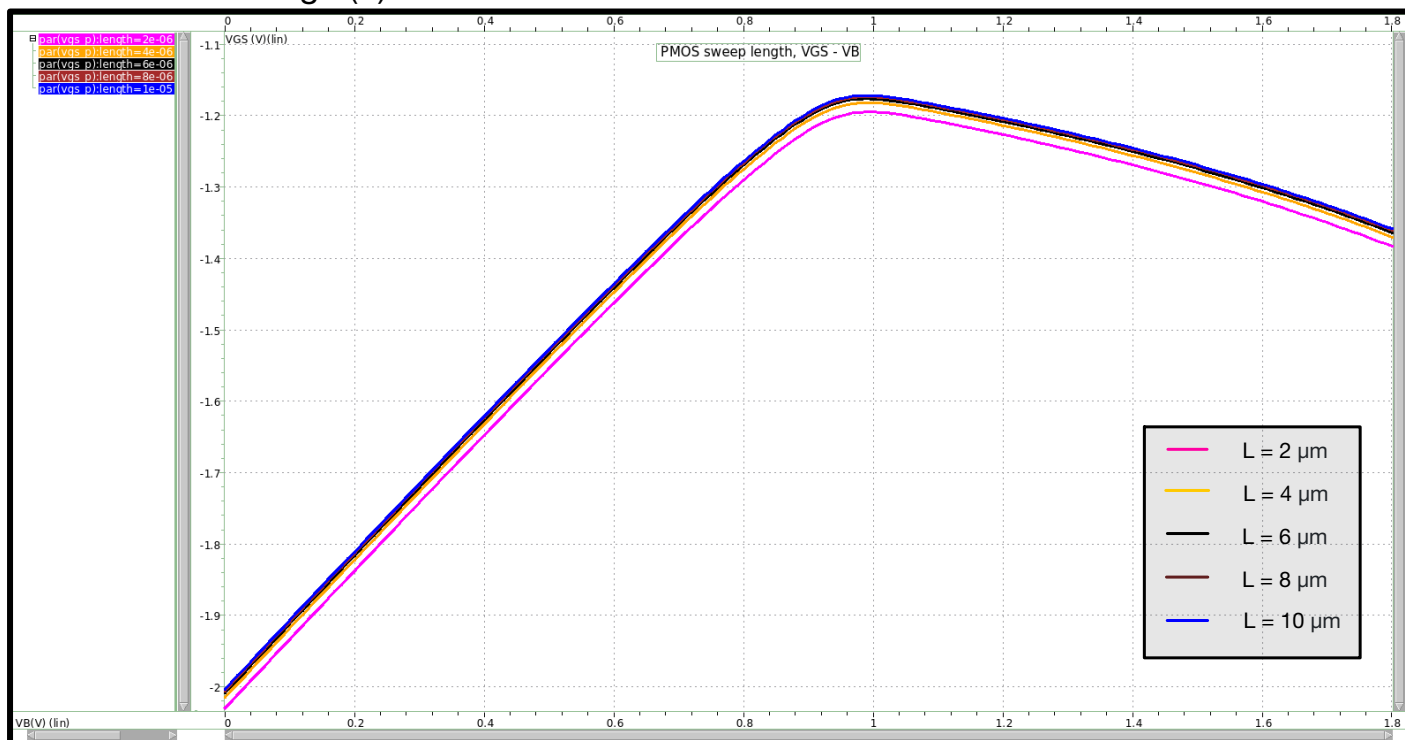

Bulk Voltage (V)

**Comment:**

In both NMOS and PMOS cases I observed that MOS with smaller channel length has larger  $|V_{GS}|$  throughout the sweeping  $V_B$ . The curves look like a boomerang, there is a turning point of the curve which the point is the minimum  $|V_{GS}|$  ( $V_B = 780$  mV for the NMOS and  $V_B = 994$  mV for the PMOS)

While sweeping  $V_B$  in  $0 - 0.8V$  for NMOS and  $1V - 1.8V$  for PMOS, both two region displays similar traits,  $|V_{GS}|$  drops as  $V_B$  approaches to turning point of each graph. This implies that either  $V_s$  increases or  $V_G$  decreases, but since the source is at the vicinity of the bulk so I think that the effect on the Source is the reason on this effect. More speculation will be that the source bulk junction tend to stay in reverse biased so that as bulk voltage increases, the source voltage reacts to it, causing  $|V_{GS}|$  to drop.

*Credits: The following part is contributed by brainstorming from EE23 108011244 王塘毅, after discussing with him, we both lead to a conclusion that the explanation makes sense.*


After both graphs hits the turning point,  $|V_{GS}|$  then starts to increase again, from research journal, after the bulk source junction is in forward bias, the phenomenon of leakage current is observed. So 王塘毅 made a conclusion and a hypothesis that  $|V_{GS}|$  increases to sustain the drain current. After probing the drain current of both MOS, I found out that both drain current are saturated to a constant value in each region after the turning point, so that the hypothesis makes even more sense.

**Reference:**

Noorfazila Kamal, Nadhira Mohamad Fauzi , “Effect Of Body Biasing On 0.13 Um CMOS Transistor”, in International Journal of Innovative Technology and Exploring Engineering (IJITEE), Dec.2019, <https://www.ijitee.org/wp-content/uploads/papers/v9i2/B7817129219.pdf>

### (3) $V_{TH}$ vs $V_B$ (NMOS)


Threshold voltage (V)

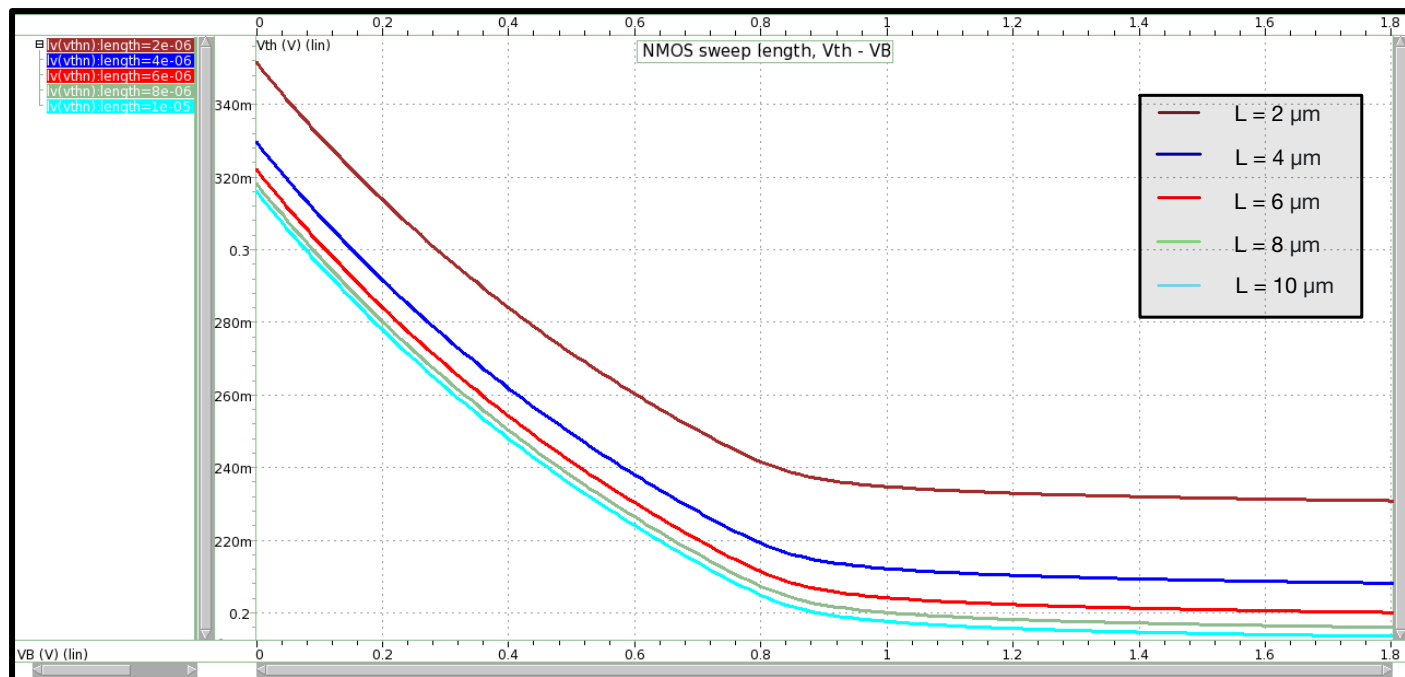

Bulk Voltage (V)

### (4) $V_{TH}$ vs $V_B$ (PMOS)

Threshold voltage (V)

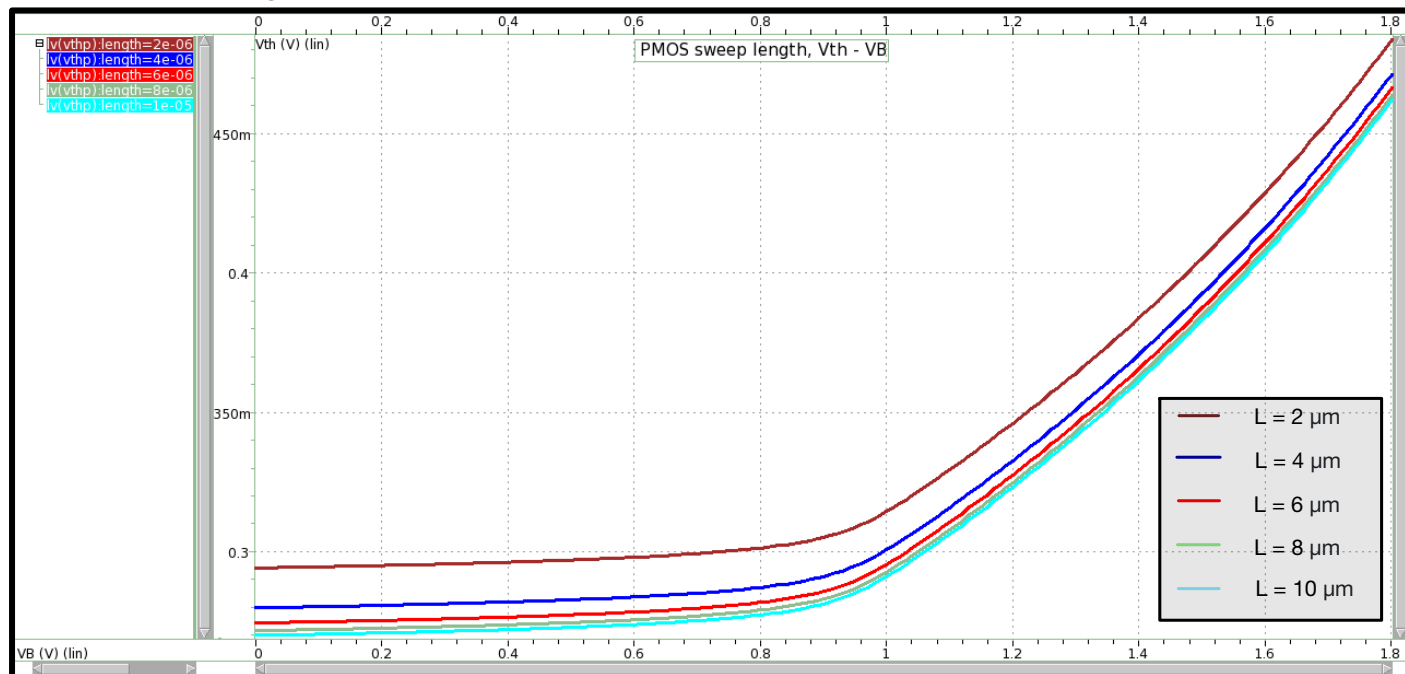

Bulk Voltage (V)

### Comment:

For both NMOS and PMOS cases, MOS with smaller channel length has larger absolute value of threshold voltage which corresponds to the (1) of part1 where the absolute value of threshold voltage drops as the channel length increases.

For known formula of body effect

$$\text{NMOS body effect: } V_{TH,N} = V_{TH0} + \gamma(\sqrt{|2\phi_f + V_{SB}|} - \sqrt{2\phi_f})$$

$$\text{PMOS body effect: } V_{TH,P} = V_{TH0} + \gamma(\sqrt{|2\phi_f + V_{BS}|} - \sqrt{2\phi_f})$$

From the formula, as the bulk voltage increases,  $V_{SB}$  decreases for NMOS, so the total threshold voltage drops, which we could see from the graph that the threshold voltage drops as bulk voltage increases.

Also, from the formula, as the bulk voltage increases,  $V_{BS}$  increases for PMOS, so the total threshold voltage rises, which we could also see from the graph that the threshold voltage rises as bulk voltage increase.


But one thing to notice is that NMOS doesn't keep a linear drop relation all along with increasing the bulk voltage, the body effect seems to be "saturated" after a specific bulk voltage. And for the PMOS, the threshold voltage doesn't increase immediately after adding the bulk voltage, instead it increases after the bulk voltage reaches a specific value.

For the NMOS case, the threshold voltage drops with an approximate rate of  $\frac{-137 \text{ mV } (V_{TH})}{1 \text{ V } (Bulk \text{ voltage})}$  as bulk voltage increases for all the 5 sweeping channel length, but after the bulk voltage approaches 0.8V, then the threshold voltage started to converge to a value. (5 different value for 5 distinct length respectively).

For the PMOS case, the threshold voltage remains the same (or without significant change) when bulk voltage is below 0.8V for all 5 of the sweeping channel lengths, but after bulk voltage is larger than 0.8 V, then the threshold voltage starts to increase with a rate of  $\frac{182 \text{ mV } (V_{TH})}{1 \text{ V } (Bulk \text{ voltage})}$ .

## Additional probe

$V_{GS}$  throughout the sweeping length

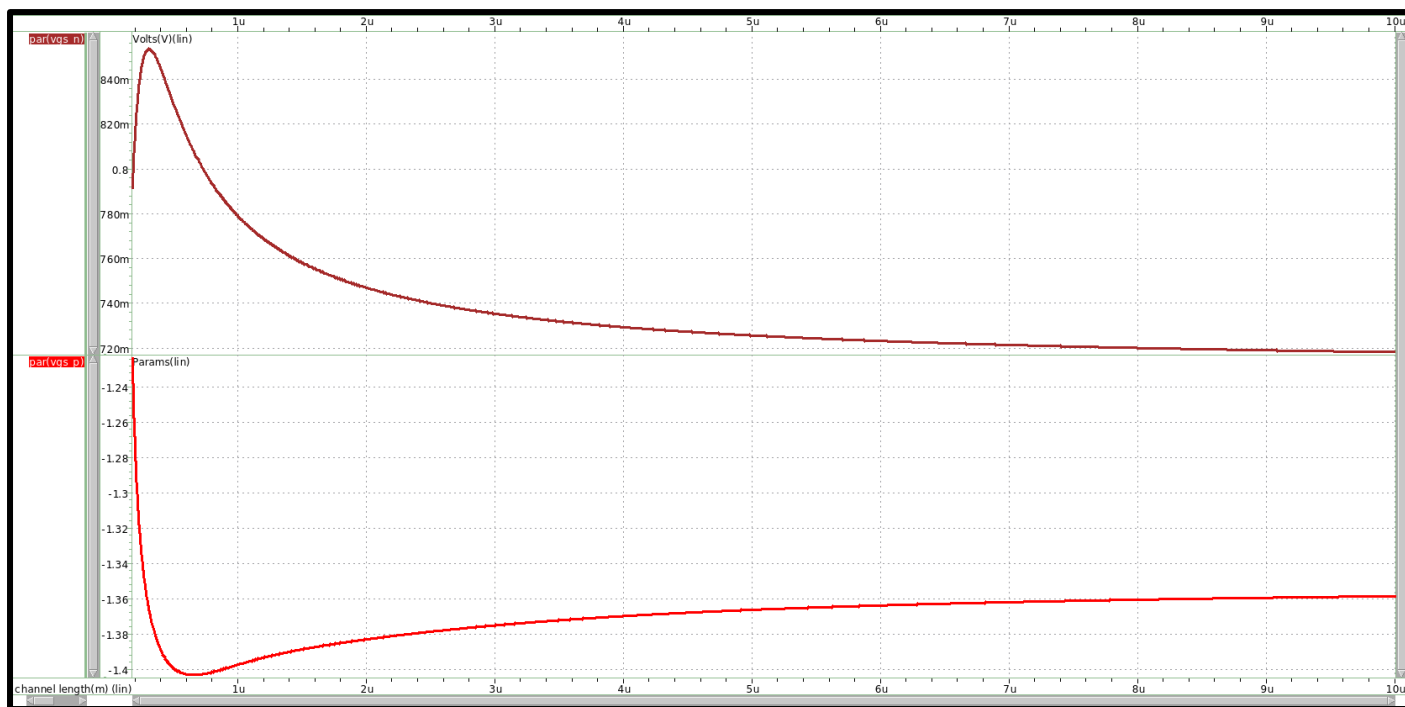

Drain current of diode connected MOS (sweep length,  $V_{GS}$ - $V_B$ )

